

1.

$V = 690\text{ V}$ ; tre symmetriska belastningar.

a) b)

	$P(\text{kW})$	$\cos \varphi$	$Q(\text{kVAr})$
I	78	0,64 kap	-93,65
II	95	0,90	46,00
III	22	1,0	0,00
$\Sigma$	195		-47,65

$$\underline{S} = 195,0 - j47,65 = 200,74 \angle -13,73^\circ \text{ (kVA)}$$

$$\underline{I}^* = \frac{\underline{S}}{3 \underline{V}_f} = 167,97 \angle -13,73^\circ \Rightarrow \underline{I} = 167,97 \angle 13,73^\circ \text{ (A)}$$

c)

$$\cos 13,73^\circ = 0,971$$

$$\cos \varphi = 0,971 \quad \text{kapacitiv karaktär}$$

d)

$$\underline{Z} = \frac{\underline{V}_f}{\underline{I}} = \frac{\frac{690}{\sqrt{3}} \angle 0^\circ}{167,97 \angle 13,73^\circ} = 2,37 \angle -13,73^\circ = 2,3 - j0,56 \text{ (}\Omega/\text{fas)}$$

$$S_n = 100 \text{ kVA} ; 6,6/0,4 \text{ kV}$$

a) Kortslutningsprov utfört från uppspänningssidan gav följande resultat:  $U_k = 265 \text{ V}$ ;  $P_k = 1,0 \text{ kW}$ ;  $I_k = I_{1n}$

$$I_{1n} = \frac{S_n}{\sqrt{3} U_{1n}} = \frac{100 \cdot 10^3}{\sqrt{3} \cdot 6,6 \cdot 10^3} = 8,75 \text{ A}$$

$$P_k = 3 \cdot R_k I_k^2 \Rightarrow R_k = \frac{1000}{3 \cdot 8,75^2} = 4,35 \text{ } \Omega/\text{fas}$$

$$U_k = \sqrt{3} I_k Z_k \Rightarrow Z_k = \frac{265}{\sqrt{3} \cdot 8,75} = 17,5 \text{ } \Omega/\text{fas}$$

$$X_k = \sqrt{Z_k^2 - R_k^2} = \sqrt{17,5^2 - 4,35^2} = 16,95 \text{ } \Omega/\text{fas}$$

Uppspänningssida:  $R_k = 4,35 \text{ } \Omega/\text{fas}$ ;  $X_k = 16,95 \text{ } \Omega/\text{fas}$

$$Z_k = (4,35 + j16,95) \text{ } \Omega/\text{fas}$$


Nedspänningssida:

$$Z_k = (4,35 + j16,95) \left( \frac{0,4}{6,6} \right)^2 = (0,016 + j0,062) \text{ } \Omega/\text{fas}$$

$$R_k = 0,016 \text{ } \Omega/\text{fas}; X_k = 0,062 \text{ } \Omega/\text{fas}$$

$$z_k = ? \quad z_k = \frac{Z_k}{Z_{\text{bas}}} = \frac{Z_k}{\frac{U_n^2}{S_n}} = \frac{17,5}{\frac{(6,6 \cdot 10^3)^2}{100 \cdot 10^3}} = 0,04 \Rightarrow z_k = 4\%$$

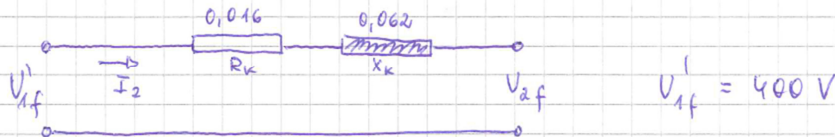b)  $I_2 = 100 \text{ A}$ ;  $\cos \varphi_2 = 0,8$ ;  $U_1 = 6,6 \text{ kV}$ ;  $U_2 = ?$



$$\Delta U = \sqrt{3} I_2 (R_k \cos \varphi_2 + X_k \sin \varphi_2) = \sqrt{3} \cdot 100 (0,016 \cdot 0,8 + 0,062 \cdot 0,6) = 8,66 \text{ V}$$

$$\underline{U_2 = 400 - 8,66 = 391,34 \text{ V}}$$

$$c) P_o = 800 \text{ W}; \quad \eta = ?$$

$$P_2 = \sqrt{3} \cdot U_2 \cdot I_2 \cdot \cos \varphi_2 = \sqrt{3} \cdot 391,34 \cdot 100 \cdot 0,8 = 54230 \text{ W}$$

$$P_{cu} = 3 R_k I_2^2 = 3 \cdot 0,016 \cdot 100^2 = 480 \text{ W}$$


$$\eta = \frac{P_2}{P_2 + P_o + P_{cu}} = \frac{54230}{54230 + 800 + 480} = 0,977$$

$$\underline{\underline{\eta = 97,7\%}}$$

3

$$AM; \quad U_n = 690 \text{ V}; \quad P_n = 500 \text{ kW}; \quad \cos \varphi = 0,92; \quad \eta = 0,95$$
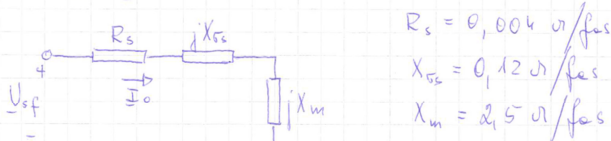
$$a) \text{ Tomgång: } s \approx 0 \Rightarrow$$



$$b) \underline{I}_o = \frac{U_{sf}}{R_s + j(X_{rs} + X_m)} = \frac{\frac{690}{\sqrt{3}} \angle 0^\circ}{0,004 + j2,62} = 152,05 \angle -89,9^\circ$$

$$\cos(-89,91^\circ) = 0,0016 = \cos \varphi_o$$

$$c) P_o = 3 U_{sf} I_o \cos \varphi_o = 285,44 \text{ W}$$

$$Q_o = 3 U_{sf} I_o \sin \varphi_o = 181,72 \text{ kVAR}$$

$$P_s = \frac{P_n}{\eta} = \frac{500}{0,95} = 526,32 \text{ kW}$$

$$\cos \varphi = 0,92 \Rightarrow Q_s = 224,21 \text{ kVAR}$$

$$d) Q_c = Q_o \quad (\text{f\"or att undvika \u00f6verkompensering})$$


$$X_c = \frac{3 U_c^2}{Q_c} \quad \text{om Y-kopplad} \quad U_c = U_{sf}$$

$$X_c = 2,62 \text{ } \Omega/\text{fas}$$

44

LM - separatmagnetiserad ;  $R_a = 0,5 \Omega$

$V_{a2} = ?$  vid 500 rpm

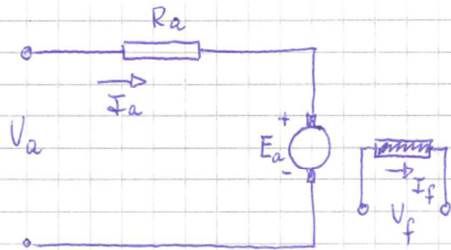

$V_{a1} = 440 \text{ V}$  ;  $I_{a1} = 40 \text{ A}$  ;  $n_1 = 1500 \text{ rpm}$

$V_{a2} = ?$  då  $n_2 = 500 \text{ rpm}$  ;  $T = \text{konst}$  ;  $I_f = \text{konst}$

$$V_{a1} = E_{a1} + R_a I_{a1} \Rightarrow E_{a1} = 440 - 0,5 \cdot 40 = 420 \text{ V}$$

$$E_a = k \omega I_f \Rightarrow$$


$$\frac{E_{a1}}{E_{a2}} = \frac{\omega_1}{\omega_2} = \frac{n_1}{n_2} \Rightarrow E_{a2} = E_{a1} \frac{n_2}{n_1} = 420 \frac{500}{1500} = 140 \text{ V}$$

Då  $T$  och  $I_f$  konst  $\Rightarrow I_a = \text{konst} \Rightarrow I_{a1} = I_{a2}$

$$V_{a2} = E_{a2} + R_a I_{a2} = 140 + 0,5 \cdot 40 = 160 \text{ V}$$

$$\underline{\underline{V_{a2} = 160 \text{ V}}}$$


5

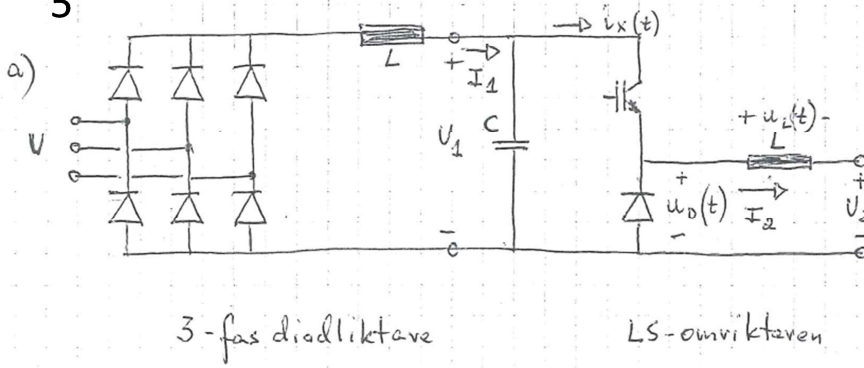


$$U = 400 \text{ V} \Rightarrow U_1 = 1,35 U = 540 \text{ V}$$

$$f = 50 \text{ kHz} \quad U_2 = 250 \text{ V} ; I_2 = 10 \text{ A}$$

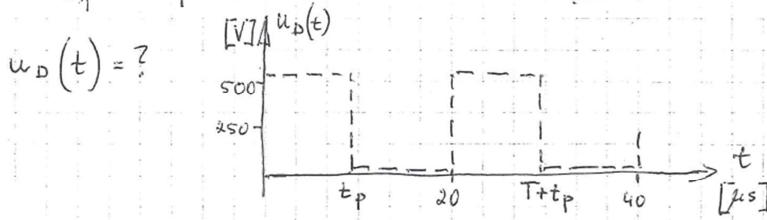b)  $\frac{U_2}{U_1} = \frac{t_p}{T} \quad T = \frac{1}{f} = 20 \cdot 10^{-6} \text{ s} ; t_p = \frac{U_2}{U_1} T = \frac{250}{540} \cdot 20 \cdot 10^{-6} = 9,3 \mu\text{s}$





c)  $u_L(t) = ?$

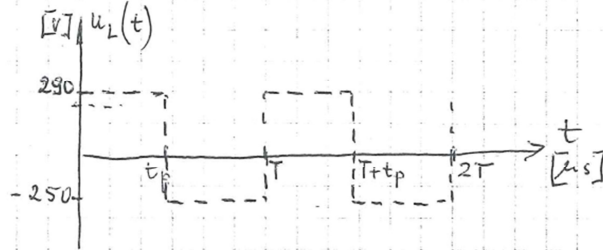

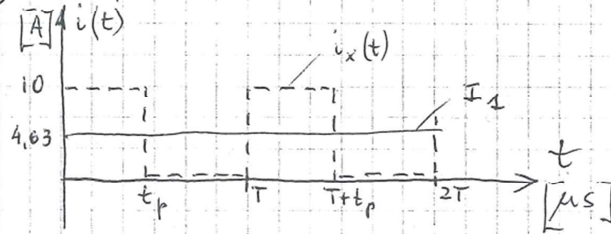d)  $U_1 I_1 = U_2 I_2$

$$I_1 = \frac{U_2}{U_1} I_2 = \frac{250}{540} \cdot 10 = 4,63 \text{ A}$$



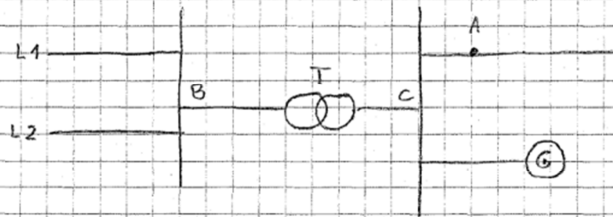

$$a) S_{KL1} = 300 \text{ MVA}$$

$$S_{KL2} = 200 \text{ MVA}$$

$$S_{KT} = \frac{S_n}{z_k} = \frac{20}{0,1} = 200 \text{ MVA}$$

$$S_{KG} = \frac{S_n}{x_d} = \frac{5}{0,25} = 20 \text{ MVA}$$

$$S_{KB} = S_{KL1} + S_{KL2} = 500 \text{ MVA}$$

$$S_{KC} = \frac{S_{KB} \cdot S_{KT}}{S_{KB} + S_{KT}} = \frac{500 \cdot 200}{700} = 142,86 \text{ MVA}$$

$$\underline{\underline{S_{KA} = S_{KC} + S_{KG} = 142,86 + 20 = 162,86 \text{ MVA}}}$$

$$b) \underline{\underline{I_{KA} = \frac{S_{KA}}{\sqrt{3} \cdot U} = \frac{162,86}{\sqrt{3} \cdot 10} = 9,4 \text{ kA}}}$$

$$\underline{\underline{I_s = 2,5 \cdot I_{KA} = 23,5 \text{ kA}}}$$