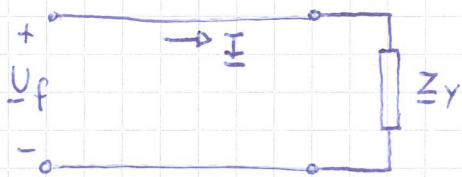


$$1/1 \quad Z_{\Delta} = (15 + j9) \Omega ; U = 400 \text{ V}$$

a) Ekv. Y-fas krets:



$$Z_Y = \frac{1}{3} Z_{\Delta} = (5 + j3) \Omega / \text{fas}$$

$$U_f = \frac{400}{\sqrt{3}} \angle 0^\circ = 230,94 \angle 0^\circ \text{ V}$$

referens

$$Z_Y = 5 + j3 = 5,83 \angle 31^\circ \Omega / \text{fas} \Rightarrow \underline{\underline{\cos \varphi = 0,857}}$$

$$\underline{I} = \frac{U_f}{Z_Y} = \frac{230,94 \angle 0^\circ}{5,83 \angle 31^\circ} = \underline{\underline{39,6 \angle -31^\circ \text{ A}}}$$


$$I_{\Delta} = \frac{I}{\sqrt{3}} = \underline{\underline{22,87 \text{ A}}}$$

$$\underline{S} = 3 U_f \underline{I}^* = 3 \cdot 230,94 \angle 0^\circ \cdot 39,6 \angle 31^\circ =$$

$$= \underline{\underline{27,44 \cdot 10^3 \angle 31^\circ = (23,52 \cdot 10^3 + j 14,13 \cdot 10^3) \text{ VA}}}$$

$$P = 23,52 \text{ kW} ; Q = 14,13 \text{ kVAR}$$

b) Ekv. Y-fas krets:

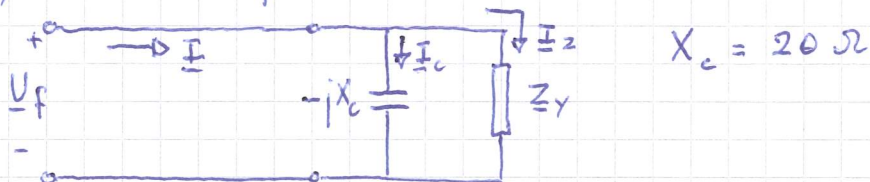

$$\underline{I}_2 = 39,6 \angle -31^\circ = (33,94 - j 20,4) \text{ A} \quad \text{enl. a)}$$

$$\underline{I}_c = \frac{U_f}{-jX_c} = j \frac{230,94 \angle 0^\circ}{20} = j 11,55 \text{ A}$$

$$\underline{I} = \underline{I}_c + \underline{I}_2 = 33,94 - j 20,4 + j 11,55 = 33,94 - j 8,85 =$$


$$= \underline{\underline{35,1 \angle -14,61^\circ \text{ A}}} \Rightarrow \underline{\underline{\cos \varphi = 0,968}}$$

$$\underline{\underline{S = 3 U_f \underline{I}^* = 24,32 \cdot 10^3 \angle 14,61^\circ = (23,52 \cdot 10^3 + j 6,13 \cdot 10^3) \text{ VA}}}$$


$$P = 23,52 \text{ kW} ; Q = 6,13 \text{ kVAR}$$

1/2

d) Visardisgram:

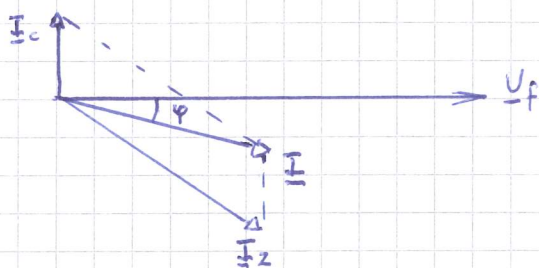

b) Anta att säkringar i fas b löser ut:

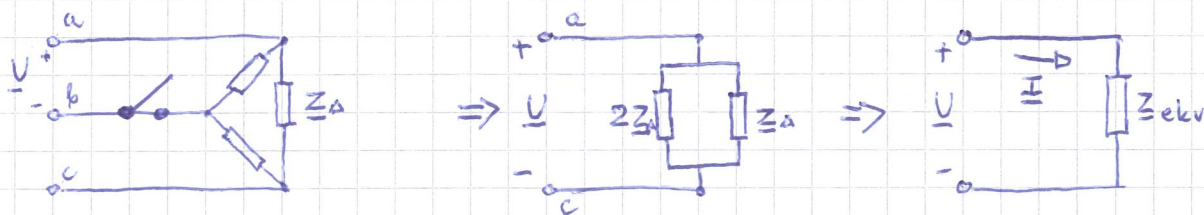

$$Z_{ekv} = 2Z_\Delta // Z_\Delta = \frac{2}{3} Z_\Delta = 11,66 / 31^\circ \Omega$$


$$I = \frac{U}{Z_{ekv}} = \frac{400 / 30^\circ}{11,66 / 31^\circ} = \underline{\underline{34,3 / -1^\circ}} \text{ A}$$

$$S = U I^* = 400 / 30^\circ \cdot 34,3 / 1^\circ = 13,72 \cdot 10^3 / 31^\circ =$$

$$= \left(\underset{\downarrow}{11,76 \cdot 10^3} + j \underset{\downarrow}{7,07 \cdot 10^3} \right) \text{ VA}$$

P Q

2.

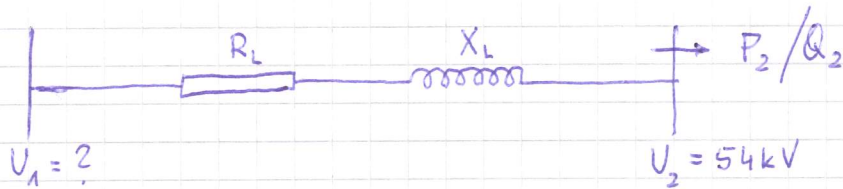

$$P_2 = 12 \text{ MW}; \cos \varphi = 0,6 \Rightarrow Q_2 = 16 \text{ MVAR}$$

$$\Rightarrow S_2 = 20 \text{ MVA}$$

Luftledning: $l = 50 \text{ km}; A = 200 \text{ mm}^2$

$$R_L = \rho \frac{l}{A} = 28,2 \cdot \frac{50}{200} = 7,05 \text{ } \Omega/\text{fas}$$

$$X_L = 0,4 \cdot 50 = 20,0 \text{ } \Omega/\text{fas}$$

a) $U_1 = ?$ visardiagramberäkningar; tvärsp.fallet försummas

$$U_{\text{längs}} = \frac{R_L \cdot P_2 + X_L Q_2}{U_2} = \frac{7,05 \cdot 12 + 20 \cdot 16}{54} = 7,5 \text{ kV}$$

$$\underline{\underline{U_1 \approx U_2 + U_{\text{längs}} \approx 61,5 \text{ kV}}}$$

b) förluster:

$$\underline{\underline{P_f = 3 R_L I^2 = 3 \cdot R_L \left(\frac{S_2}{\sqrt{3} U_2} \right)^2 = 3 \cdot 7,05 \cdot \left(\frac{20 \cdot 10^6}{\sqrt{3} \cdot 54 \cdot 10^3} \right)^2 = 967,1 \text{ kW}}}$$

$$\underline{\underline{Q_f = 3 X_L I^2 = 3 \cdot 20 \left(\frac{20 \cdot 10^6}{\sqrt{3} \cdot 54 \cdot 10^3} \right)^2 = 2,74 \text{ MVAR}}}$$

3

En 3-fas trafo: 690/400 V; $S_n = 2400 \text{ VA}$; $f = 50 \text{ Hz}$; $P_o = 20 \text{ W}$



$$r_k = 1,5\% ; z_k = 6,6\%$$

a) R_k och X_k hänförelse till 400 V-sidan?

$$R_k = r_k \cdot Z_{\text{bas}} = 0,015 \frac{400^2}{2400} = 1,0 \text{ } \Omega/\text{fas}$$

$$Z_k = z_k \cdot Z_{\text{bas}} = 0,066 \frac{400^2}{2400} = 4,4 \text{ } \Omega/\text{fas}$$
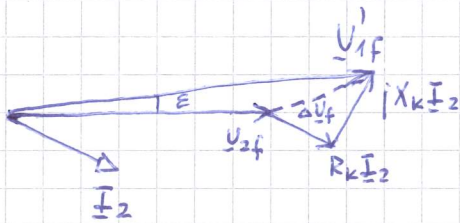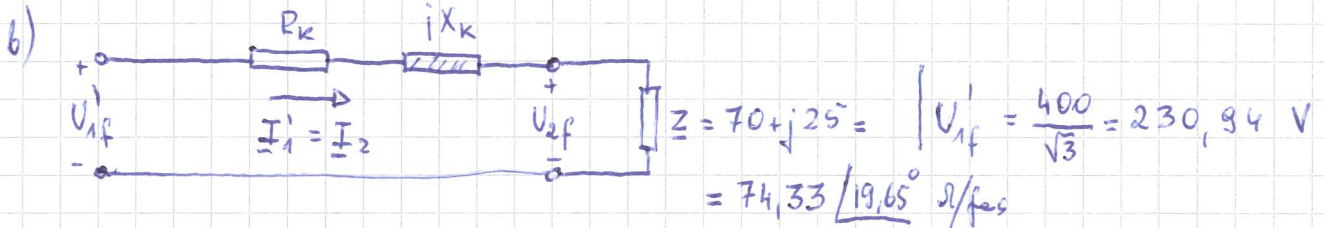
$$X_k = 4,28 \text{ } \Omega/\text{fas}$$



c)

$$\underline{I}_2 = \frac{U_{1f}'}{R_k + jX_k + Z} = \frac{230,94 \angle 0^\circ}{71 + j29,4} = \frac{230,94 \angle 0^\circ}{76,85 \angle 22,49^\circ} = \underline{\underline{3,0 \angle -22,49^\circ \text{ A}}}$$

$$U_{2f} = Z \cdot \underline{I}_2 = 74,33 \angle 19,65^\circ \cdot 3,0 \angle -22,49^\circ = 223,0 \angle -2,84^\circ \text{ V}$$

$$U_2 = 386,25 \text{ V}$$

d) Förluster:

$$P_{\text{cu}} = 3 R_k I_2^2 = 3 \cdot 1 \cdot 3^2 = 27,0 \text{ W} ; P_o = 20,0 \text{ W}$$

$$P_2 = \sqrt{3} U_2 I_2 \cos \varphi_2 = \sqrt{3} \cdot 386,25 \cdot 3 \cdot \cos 19,65^\circ = 1890 \text{ W}$$

$$\eta = \frac{P_2}{P_2 + P_{\text{cu}} + P_o} = \frac{1890}{1890 + 27 + 20} = 0,9757$$

$$\underline{\underline{\eta = 97,57\%}}$$

4/1

$$\text{AM} : P_n = 15 \text{ kW}; U_n = 400 \text{ V}; f = 50 \text{ Hz}$$

$$I_n = 32 \text{ A}; n_n = 970 \text{ rpm}; \cos \varphi = 0,81$$

Lasten

$$70 \text{ Nm vid } 750 \text{ rpm}$$

$$145 \text{ Nm vid } 1250 \text{ rpm}$$

a) $n = ?$

Lastens momentkaraktäristik kan approximeras med en rät linje

även AM-s momentkaraktäristik mellan tomgång och märkdrift kan approximeras med en rät linje

$$\text{AM} \quad T_n = \frac{P_n}{\omega_n} = \frac{15 \cdot 10^3}{\frac{2\pi \cdot 970}{60}} = 147,7 \text{ Nm}$$

$$\text{vid } n_s = 1000 \text{ rpm är } T = 0$$

$$T_{\text{AM}} - 0 = \frac{147,7 - 0}{970 - 1000} (n - 1000)$$

$$T_{\text{AM}} = 4920 - 4,92n$$

Lasten


$$T_L - 70 = \frac{145 - 70}{1250 - 750} (n - 750)$$

$$T_L = -42,5 + 0,15n$$

$$\text{Vid drift gäller: } T_{\text{AM}} = T_L$$

$$4920 - 4,92n = -42,5 + 0,15n$$

$$\underline{n = 978,8 \text{ rpm}}$$

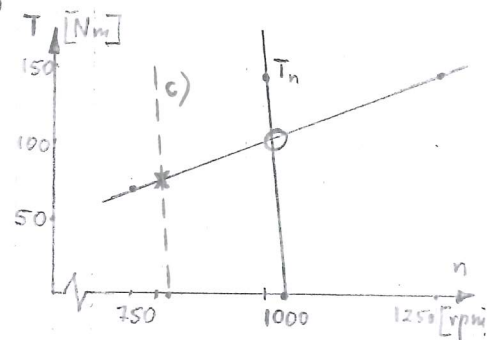b) $T = ?$

$$\underline{T = 4920 - 4,92 \cdot 978,8 = 104,3 \text{ Nm}}$$

4/2

c) d)

Lutningen på AM-s momentkurva i båda driftsfall skall vara lika

AM skall skapa vridmoment:

$$\text{eul. a)}: T_L = -42,5 + 0,15n = -42,5 + 0,15 \cdot 800 = \underline{\underline{77,5 \text{ Nm}}}$$

$$\frac{T_b}{n_a - n_{sa}} = \frac{T_d}{n_c - n_{sc}} \Rightarrow \frac{104,3}{978,8 - 1000} = \frac{77,5}{800 - n_{sc}}$$

$$n_{sc} = 815,75 \text{ rpm}$$

$$p = 3$$

$$n_{sc} = 60 \cdot \frac{f_c}{p} \Rightarrow \underline{\underline{f_c}} = \frac{p \cdot n_{sc}}{60} = \frac{3 \cdot 815,75}{60} = \underline{\underline{40,79 \text{ Hz}}}$$

För att AM-s luftgapsflöde skall hållas konstant:

$$\Rightarrow \frac{U}{f} = \text{konst} \quad \frac{400}{50} = 8 \Rightarrow U_c = 40,79 \cdot 8 = \underline{\underline{326,3 \text{ V}}}$$

e) $f_r = ?$

$$f_r = s_c \cdot f_c = \frac{815,75 - 800}{815,75} \cdot 40,79 = \underline{\underline{0,79 \text{ Hz}}}$$