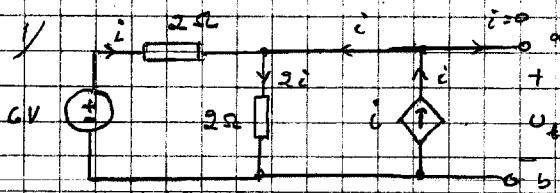


Lösningen till tentamen i Elektriska kretsen del  
signaler del 1 2002-12-20




1) Törnspanning  
söder ut ekvationer i  $i_1$ )

$$KVL: -6 + 2i + 2i \cdot 2 = 0$$

$$\Rightarrow i = 1$$

$$KVL: 2i \cdot 2 - u_k = 0 \Rightarrow u_k = 4 \cdot i = 4 \text{ V}$$


2) Kontrollektion

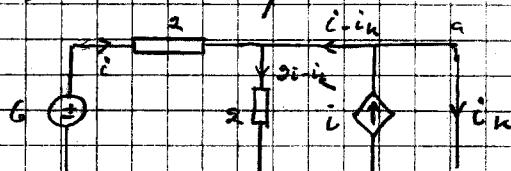

$$KVL: -6 + 2i = 0 \Rightarrow i = 3$$

$$KVL: (2i - i_k) \cdot 2 = 0 \Rightarrow i_k = 3i = 6 \text{ A}$$
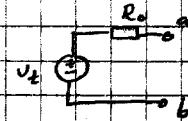
$$R_o = \frac{u_k}{i_k} = \frac{4}{3} \Omega$$



dämpning (full 1)


max effekt i  $R_L$  för  $R_L = \frac{2}{3} \Omega$

$$KVL: -4 + \frac{2}{3} i_L + R_L i_L = 0$$

$$\Rightarrow i_L = \frac{4}{\frac{2}{3} + R_L} = 3 \text{ A}$$


$$\text{Effekt i } R_L: P_{\text{max}} = R_L i_L^2 = 6 \text{ W}$$
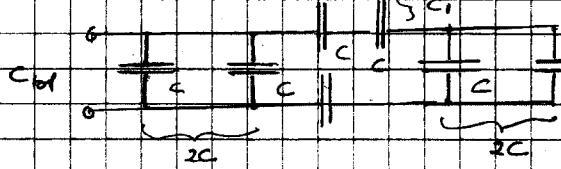
$$2c) C_0 = \sum C_k; \frac{1}{C_{\text{serie}}} = \sum \frac{1}{C_k}$$



$$\frac{1}{C_0} + \frac{1}{C} = \frac{1}{C_1}$$


$$\Rightarrow C_1 = C/2$$

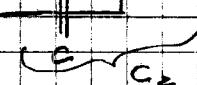

$$C_0 = 2C + C_1/2 = 2C + C/2 = \frac{5}{2} C \Rightarrow C_2 = 2C/7$$

$$\underline{\underline{C_{\text{tot}}} = 2C + C_2 = \frac{16}{7} C}$$

$$2b) \frac{I}{j\omega L}$$

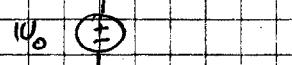

$$u_0 = j\omega L \bar{I}, \quad 100 e^{j0} = j\omega L \cdot 20 e^{j\alpha} =$$

$$= \omega L \cdot 20 e^{j(\frac{\pi}{2} + \alpha)}$$

Beloppen lika, vinkelnar lika  $\Rightarrow$

$$\left\{ \begin{array}{l} 100 = 90\omega L \\ 0 = \alpha + \frac{\pi}{2} \end{array} \right. \Rightarrow \underline{\underline{\frac{L}{\omega} = \frac{100}{90 \cdot 100\pi} = 15,9 \cdot 10^{-3} \text{ H}}}$$


$$\left\{ \begin{array}{l} 0 = \alpha + \frac{\pi}{2} \\ \alpha = -\frac{\pi}{2} \end{array} \right. \Rightarrow \underline{\underline{\alpha = -90^\circ}}$$

$$u_0 = 100 e^{j0}$$

$$I = 20 e^{j\alpha}$$

$$\omega = 90\pi \text{ rad/s} = 9\pi \cdot 50$$

3)

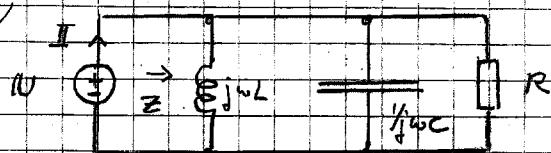

Parallel resonans neds

$$\frac{1}{Z} = Y = \frac{1}{jwL} + jwC + \frac{1}{R}$$

= 0 vid resonans  $\omega_0^2 = \frac{1}{LC}$ 


$$\Rightarrow Z(\omega_0) = R \quad \text{, } \frac{U}{I} = \frac{U_m e^{j\phi}}{I_m e^{j\phi}} = R$$

$$\Rightarrow R = \frac{10}{10^{-2}} = 10^3 \Omega \quad Q_{II} = \frac{R}{\omega_0 L}, \quad 1000 = \frac{10^3}{2 \cdot 10^3 L}$$

$$\Rightarrow L = 5 \cdot 10^{-3} H$$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow C = \frac{1}{\omega_0^2 L} = \frac{1}{4 \cdot 10^6 \cdot 5 \cdot 10^{-3}} = 50 \cdot 10^{-6} F$$

4)

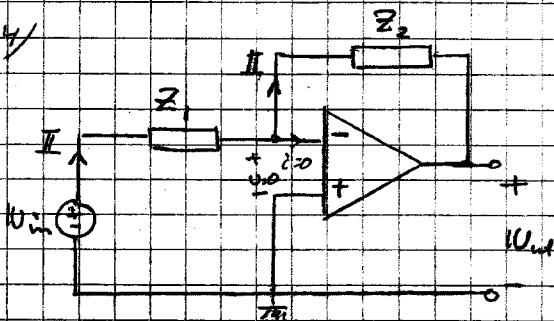

$$a) Impedansen Z_1 = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$Z_2 = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$KVL \text{ t.v. } -U_{in} + Z_1 I + 0 = 0$$

$$\text{t.h. } -0 + Z_2 I + U_{out} = 0$$

$$\Rightarrow U_{out} = -Z_2 I = -Z_2 \frac{U_{in}}{Z_1}$$

$$H(j\omega) = \frac{U_{out}}{U_{in}} = -\frac{Z_2}{Z_1}$$

$$= -\frac{R_2 (1 + j\omega R_1 C_1)}{R_1 (1 + j\omega R_2 C_2)}$$

$$1 + j\omega/\omega_1 \quad 1 + j\omega/\omega_2$$

$$\omega_1 = \frac{1}{R_1 C_1}, \quad \omega_2 = \frac{1}{R_2 C_2}$$


$$b) \omega_1 = \frac{1}{R_1 C_1} = 200 \quad \omega_2 = \frac{1}{R_2 C_2} = 2 \cdot 10^3$$

$$\omega < \omega_1 : H(j\omega) \approx -\frac{R_2}{R_1} = -10 \quad 20 \log 10 = 20 \text{ dB}$$


$$\omega_1 < \omega < \omega_2 : H(j\omega) \approx -\frac{R_2}{R_1} j\omega R_1 C_1 = -j\omega R_2 C_1 \quad |H| \text{ ökade med } 20 \text{ dB/decade}$$

$$\omega > \omega_2 : H(j\omega) \approx -\frac{R_2}{R_1} \frac{j\omega/\omega_2}{j\omega/\omega_2} = -\frac{R_2 \omega_2}{R_1 \omega_2} = -10 \cdot 10$$

$$20 \log (100) = 40 \text{ dB}$$

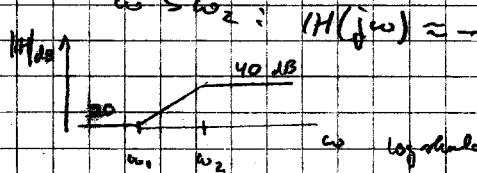

Gedda transformations ekv. + KVL

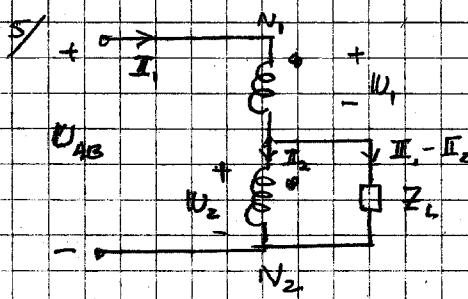

$$\frac{N_1}{N_1} = \frac{U_3}{N_2} \quad (1)$$

$$N_1 I_1 + N_2 I_2 = 0 \quad (2)$$

$$-U_{AB} + U_1 + U_2 = 0 \quad (3)$$

$$-U_2 + Z_L (I_1 - I_2) = 0 \quad (4)$$

$$\Rightarrow U_{AB} = \frac{(N_1 + N_3)^2}{N_3^2} Z_L I_1 \quad \Rightarrow Z_L = \frac{U_{AB}}{I_1} = \frac{(N_1 + N_3)^2}{N_3^2} Z_L$$