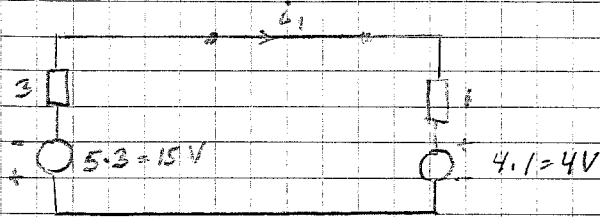



1/ $2\Omega // 2\Omega \rightarrow 1\Omega$ för Norton-Theorem omvandling



KVL $\Rightarrow +15 + 3i_1 + 4i_1 + 4 = 0$

$\Rightarrow i_1 = -\frac{19}{7} = -4,75 \text{ A}$

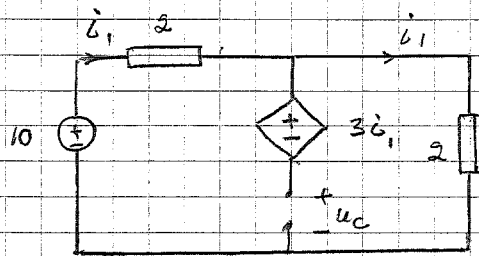2/ $t < 0$ stationär tillstånd: C utgör avbrott. Ingen ström i grenen med C. Teckna u_C !




KVL för slinga $-10 + 2i_1 + 2i_1 = 0$

$\Rightarrow i_1 = 2,5 \text{ A}$

KVL th $-u_C - 3i_1 + 2i_1 = 0$

$\Rightarrow u_C = -1 \cdot i_1 = -2,5 \text{ V} = u_C(0)$

$t \geq 0$

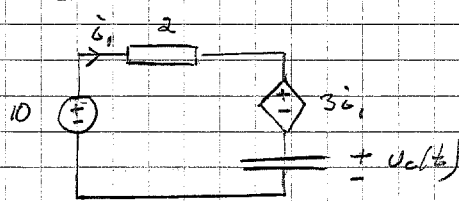

KVL $-10 + 2i_1 + 3i_1 + u_C(t) = 0$ (1)


$i_1 = C \frac{du_C}{dt}$ (2)

(2) i (1) $\Rightarrow \frac{d u_C}{dt} + \frac{1}{5C} u_C(t) = \frac{10}{5C}$

$C = 0,2 \Rightarrow \frac{d u_C}{dt} + u_C(t) = 10$ (3) med lösning $u_C(t) = k_1 + k_2 e^{-t/1}$ (4)

ins i (4) i (3) $\Rightarrow k_1 = 10$; $u_C(0) = k_1 + k_2 = -2,5 \Rightarrow k_2 = -12,5$

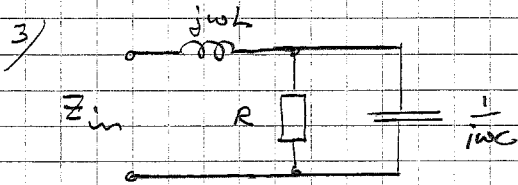alltså $u_C(t) = 10 - 12,5 e^{-t}$ ✓ [koll $t \rightarrow \infty$: $i_1 \rightarrow 0$ $u_C \rightarrow 10 \text{ V}$ OK]



$R // \frac{1}{j\omega C} = \frac{R}{1 + j\omega RC}$


$Z_{in} = j\omega L + \frac{R}{1 + j\omega RC} = j\omega L + \frac{R(1 - j\omega RC)}{1 + \omega^2 R^2 C^2}$

Z_{in} är reell för $\omega L = \frac{\omega R^2 C}{1 + \omega^2 R^2 C^2}$

1/ $\omega_r = 0 \Rightarrow Z_{in}(\omega=0) = R = 100 \Omega$

2/ $\omega_r^2 = \frac{1}{LC} - \frac{1}{R^2 C^2}$; $\Rightarrow \omega_r = 3 \cdot 10^5 \text{ rad/s} \Rightarrow Z_{in}(\omega_r) = \frac{L}{RC} = 64 \Omega$

4/a Tomgång: $U_k = Z$

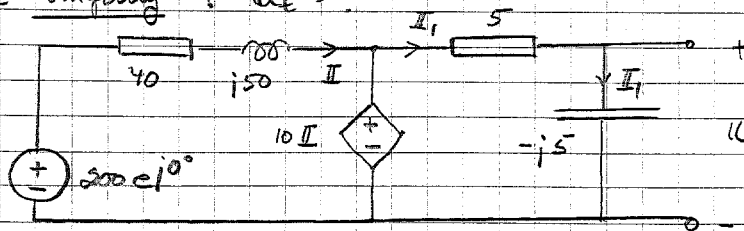

KVL tv


$$-200 + (40 + j50)I + 10I = 0$$

$$\Rightarrow I = \frac{200}{50(1+j)} = \frac{4}{1+j}$$

KVL th: $-10I + 5I - j5I = 0 \Rightarrow I_1 = \frac{10I}{5(1-j)} = \frac{2I}{1-j} = \dots = 4$

$$\Rightarrow U_k = -j5I_1 = -j20$$

Kortslutning

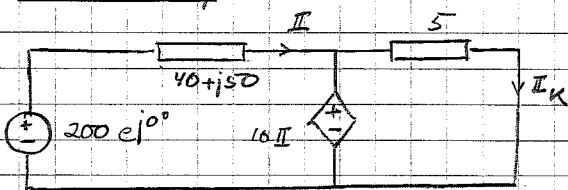


KVL tv: $-200 + (40 + j50)I + 10I = 0$

$$\Rightarrow I = \frac{4}{1+j}$$

KVL th: $-10I + 5I_k = 0$

$$\Rightarrow I_k = 2I = \frac{8}{1+j}$$
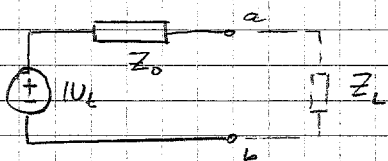
$$\Rightarrow Z_0 = \frac{U_k}{I_k} = \frac{-j20}{8} (1+j) = 2,5(1-j)$$



b) Effekten i Z_L är max för

$$\underline{Z_L = Z_0^* = 2,5(1+j) \Omega}$$

5/

Komplex effekt i de tre belastningarna:

$$S_1 = P_1 + jQ_1 = 3 \cdot 10^3 + j4 \cdot 10^3, \quad S_3 = P_3 = 1,5 \cdot 10^3$$



$$S_2 = P_2 + jQ_2 = S_2 \cos(\beta - \alpha) + jS_2 \sin(\beta - \alpha)$$

känd $\cos(\beta - \alpha) = 0,6 \Rightarrow \sin(\beta - \alpha) = 0,8$

(inlednings last $\Rightarrow \beta - \alpha > 0$)

$$\Rightarrow S_2 = 2,5 \cdot 10^3 (0,6 + j0,8) = 1,5 \cdot 10^3 + j2 \cdot 10^3$$
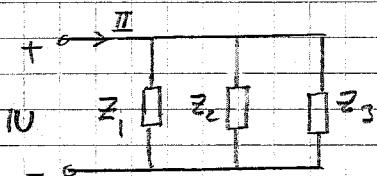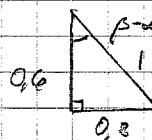
$$\Rightarrow \underline{S_{tot}} = S_1 + S_2 + S_3 = 6 \cdot 10^3 + j6 \cdot 10^3 \text{ VA}$$



$$S_{tot} = \frac{1}{2} UI^* = \frac{1}{2} 250 \sqrt{2} e^{j0} \cdot I_m e^{-j\alpha} =$$

$$= 6 \cdot 10^3 (1+j) = 6 \cdot 10^3 \sqrt{2} e^{j45^\circ}$$

$$\Rightarrow \alpha = -45^\circ, \quad \underline{I} = 48 \text{ A}$$

(ansatt $I = I_m e^{j\alpha}$)

$$\Rightarrow \text{Impedansen } \underline{Z_{tot}} = \frac{U}{I} = \frac{250 \sqrt{2} e^{j0}}{48 e^{-j45^\circ}} = 7,30 e^{j45^\circ} = \underline{5,21(1+j) \Omega}$$