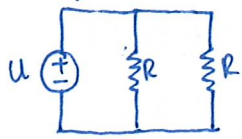


1)

a) C - Two speakers of 4Ω , $50W$ in parallel



$$R = 4\Omega$$

$$P_u = 100W @ 4\Omega$$

$$R_{eq} = R // R = 2\Omega$$

$$P_u = 100W = \frac{u^2}{4\Omega} \Rightarrow u = 20V$$


$$P_R = \frac{u^2}{R} = \frac{200^2}{4} = 100W \quad (> 50W \text{ load maximum!})$$

b) D - Two Non-Inverting Amplifiers followed by a Differential Amplifier

Non-inverting amplifiers on each differential input remove the need for impedance matching by making the input impedance nearly infinite.

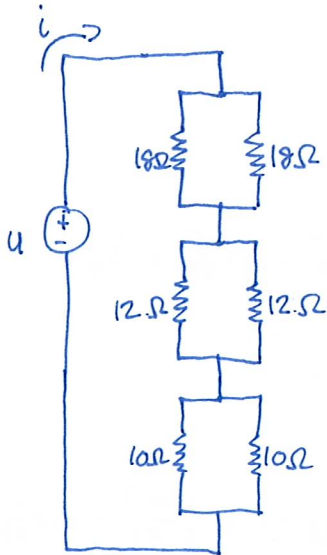c) There are many solutions. Example:

$$P_u = 2W @ 20\Omega \Rightarrow 2W = \frac{u^2}{20\Omega} \Rightarrow u = 2\sqrt{10}V$$



$$R_{eq} = (18 // 18) + (12 // 12) + (10 // 10) = 9 + 6 + 5 = \underline{20\Omega}$$


$$i = \frac{2\sqrt{10}}{20} = \frac{1}{\sqrt{10}} A$$

$$I_{18\Omega} = I_{12\Omega} = I_{10\Omega} = \frac{1}{2\sqrt{10}} A = \frac{i}{2}$$

$$P_{18\Omega} = I_{18\Omega}^2 \cdot 18\Omega = \frac{18}{40} = \underline{0.45W} < 0.5W$$

$$P_{12\Omega} = I_{12\Omega}^2 \cdot 12\Omega = \frac{12}{40} = \underline{0.30W} < 0.5W$$
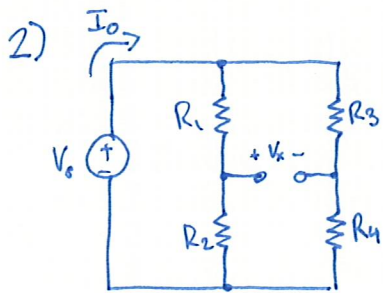
$$P_{10\Omega} = I_{10\Omega}^2 \cdot 10\Omega = \frac{10}{40} = \underline{0.25W} < 0.5W$$



$$\begin{aligned}
 V_0 &= 30\text{V} \\
 R_1 &= 5.0\text{k}\Omega \\
 R_2 &= 1.0\text{k}\Omega \\
 R_3 &= 60\text{k}\Omega \\
 R_4 &= 15\text{k}\Omega
 \end{aligned}$$

a) $V_{x^+} : V_0 \cdot \frac{R_2}{R_1 + R_2} = 30 \cdot \frac{1\text{k}\Omega}{1\text{k}\Omega + 5\text{k}\Omega} = 5\text{V}$

$$V_{x^-} : V_0 \cdot \frac{R_4}{R_3 + R_4} = 30 \cdot \frac{15\text{k}\Omega}{60\text{k}\Omega + 15\text{k}\Omega} = 6\text{V}$$

$$V_x = (V_{x^+}) - (V_{x^-}) = 5\text{V} - 6\text{V} = \boxed{-1\text{V}}$$


b) $R_{\text{eq}} = (R_1 + R_2) \parallel (R_3 + R_4)$

$$= 6\text{k}\Omega \parallel 75\text{k}\Omega = \frac{6\text{k}\Omega \cdot 75\text{k}\Omega}{6\text{k}\Omega + 75\text{k}\Omega}$$

$$R_{\text{eq}} \approx 5.6\text{k}\Omega$$

$$I_0 = \frac{V_0}{R_{\text{eq}}} = \frac{30}{5.6\text{k}} = 5.4 \cdot 10^{-3}\text{A} = \boxed{5.4\text{mA}}$$

3)

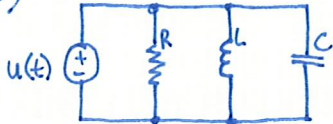

$$\begin{aligned}
 R &= 50\Omega \\
 L &= 0.50\text{H} \\
 C &= 10\mu\text{F}
 \end{aligned}$$

$$u(t) = 500\sqrt{2} \cdot \cos(\omega t)\text{V}$$

$$\omega = 377\text{ rad/s}$$

a) Average Power: $P_{\text{avg}} = S_R = \frac{1}{2} U I_R^* = \frac{1}{2} \frac{U U^*}{R^*} = \frac{1}{2} \frac{|U|^2}{R^*} = \frac{V_{\text{rms}}^2}{R}$

$$V_{\text{rms}} = \frac{500\sqrt{2}}{\sqrt{2}} = 500\text{V}$$

$$P_{\text{avg}} = \frac{500\text{V}^2}{50} = 5000\text{W} = \boxed{5\text{kW}}$$


b) Reactive Power: $P_{\text{rea}} = S_L + S_C = \frac{1}{2} U I_L^* + \frac{1}{2} U I_C^* = \frac{1}{2} \frac{|U|^2}{Z_L^*} + \frac{1}{2} \frac{|U|^2}{Z_C^*}$

$$Z_L^* = -j\omega L = -j377 \cdot 0.5$$

$$Z_C^* = j\frac{1}{\omega C} = \frac{j}{377 \cdot 10 \cdot 10^{-6}}$$

$$S_L + S_C = \frac{(500\sqrt{2})^2}{2} \left(\frac{1}{-j377 \cdot 0.5} - j377 \cdot 10 \cdot 10^{-6} \right) \approx j384 = jQ \Rightarrow \boxed{P_{\text{rea}} = 384\text{VAR}}$$

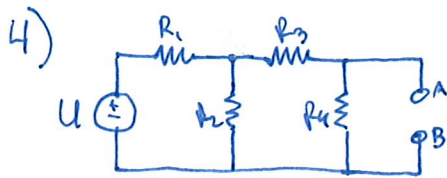
$$\text{Effective Power: } S = \sqrt{P_R^2 + Q^2} = \sqrt{5000^2 + 384^2} = \underline{\underline{5014\text{VA}}}$$




$$\begin{aligned}
 R_1 &= 200\Omega \\
 R_2 &= 300\Omega \\
 R_3 &= 60\Omega \\
 R_4 &= 220\Omega \\
 U &= 120V
 \end{aligned}$$

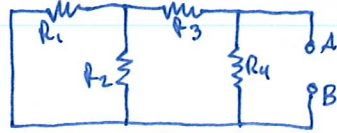a) Thevenin Equivalent:


$$R_{TH} = R_{eq} \text{ if sources } = \emptyset$$




$$R_{12} = R_1 // R_2 = 120\Omega$$

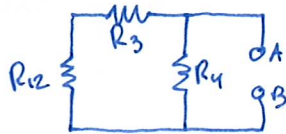

$$R_{123} = R_{12} + R_3 = 180\Omega$$

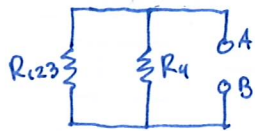
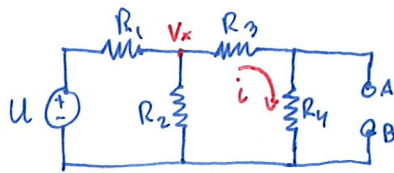
$$R_{1234} = R_{TH} = R_{123} // R_4 = \underline{99\Omega}$$



$$V_{oc} = V_{AB} = i \cdot R_4$$

$$V_x: \frac{U - V_x}{R_1} - \frac{V_x}{R_2} - \frac{V_x}{R_3 + R_4} = 0$$



$$\frac{30}{200} - \frac{V_x}{200} - \frac{V_x}{300} - \frac{V_x}{280} = 0$$

$$V_x = 50.4V$$

$$i = \frac{V_x}{R_3 + R_4} = \frac{50.4}{60 + 220} = 0.18A$$

$$V_{TH} = 0.18 \cdot 220 = \boxed{39.6V}$$


Answer:

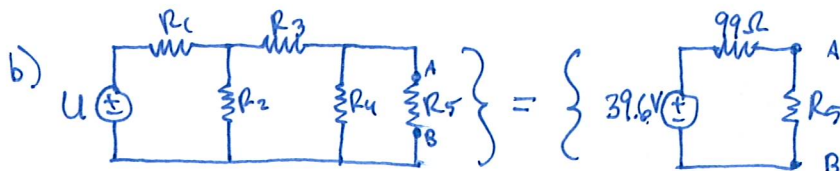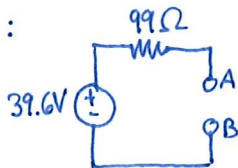

$$R_5 = 100\Omega. \text{ Find } V_{AB}$$

$$V_{AB} = 39.6V \cdot \frac{100\Omega}{99\Omega + 100\Omega} = \boxed{19.9V}$$

Voltage Divider

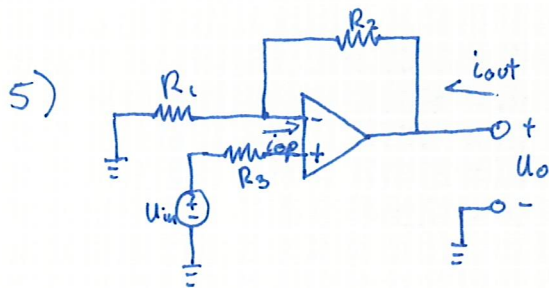

Ideal Op-Amp \Rightarrow

$$\begin{aligned} \varepsilon &= (V_-) - (V_+) = 0 \\ R_i &= \infty \Omega \Rightarrow i_{op} = 0 \text{ A} \\ R_o &= 0 \Omega \end{aligned}$$

a) Gain $\left(\frac{U_o}{U_{in}}\right)$: $(V_+) = U_{in}$, $(V_-) = U_{in}$

$$U_o \cdot \frac{R_1}{R_1 + R_2} = U_{in} \quad \left. \vphantom{U_o} \right\} \text{Voltage Divider}$$


$$\frac{U_o}{U_{in}} = \frac{R_1 + R_2}{R_1}$$

$$\boxed{\frac{U_o}{U_{in}} = 1 + R_2/R_1}$$

b) Input Resistance: $R_{in} = \frac{U_{in}}{i_{in}} = \frac{U_{in}}{0 \text{ A}} = \boxed{\infty \Omega}$

c) Output Resistance: $R_{out} = \left. \frac{U_o}{i_{out}} \right|_{U_{in}=0} = R_2 // R_o = R_2 // 0 \Omega = \boxed{0 \Omega}$

6a)

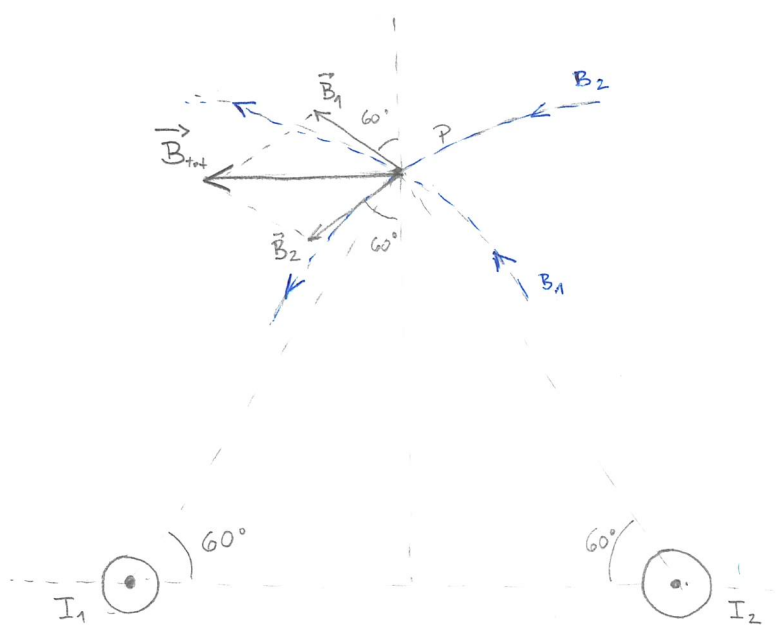

Bidragen \vec{B}_1 och \vec{B}_2 till flödestätheten ligger utefter tangenterna i P till respektive cirkelbågar och är lika stora:

$$|\vec{B}_1| = |\vec{B}_2| = \frac{\mu_0 I}{2\pi a} = 4 \mu T$$

Vi uttrycker \vec{B}_1 och \vec{B}_2 i polära koordinater och får då

$$\begin{aligned} \vec{B}_1 &= (4 \mu T, 150^\circ) & \text{i rektangulär form} & \vec{B}_1 = (-3,464; 2) \mu T \\ \vec{B}_2 &= (4 \mu T, -150^\circ) & \text{fören} & \vec{B}_2 = (-3,464; -2) \mu T \end{aligned}$$

$$\vec{B}_{Tot} = \vec{B}_1 + \vec{B}_2 = (-6,93; 0) \mu T$$

$$|\vec{B}_{Tot}| = \approx 6,93 \mu T$$

6b)

