

I) We are calculating the impedances related to an inductor and a capacitor. Which of the following is the correct?

- A) Inductive reactance translates into a positive imaginary impedance while capacitive reactance translates into a negative imaginary impedance.
- B) Both inductive and capacitive reactance translate into a positive imaginary impedance.
- C) It depends on the values of the inductor and the capacitor.
- D) Inductive reactance translates into a negative imaginary impedance while capacitive reactance translates into a positive imaginary impedance

II) Represent the following voltage sources in the phasor form.


- A) $u_{DC}(t) = 150 \text{ V} \rightarrow 150 \angle 0^\circ \text{ V}$
- B) $u_{s1}(t) = 120 \cos(100t + 45^\circ) \text{ V} \rightarrow 120 \angle 45^\circ \text{ V}$
- C) $u_{s2}(t) = 130 \sin(100t) \text{ V} \rightarrow 130 \angle -90^\circ \text{ V}$
- D) $u_{s3}(t) = 220 \sin(100 * 2\pi * t + 75^\circ) \text{ V} \rightarrow 220 \angle -15^\circ \text{ V}$

TIP: $\sin(\omega t) = \cos(\omega t - 90^\circ)$

III) What is the configuration of an instrumentational amplifier?

- A) Two inverting amplifiers follow by a differential amplifier
- B) Two buffer amplifiers follow by a non-inverting amplifier
- C) Two differential amplifiers follow by a buffer
- D) Two non-inverting amplifiers follow by a differential amplifier

①

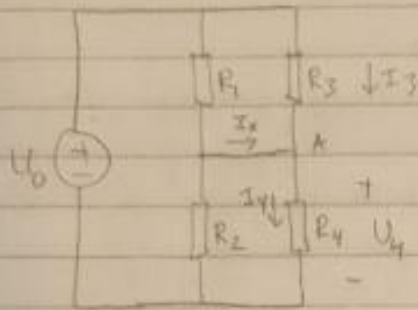

$$R_1 = 70 \Omega$$

$$R_2 = 20 \Omega$$

$$R_3 = 30 \Omega$$

$$R_4 = 5 \Omega$$

$$U_0 = 5 \text{ V}$$

Paralellkoppla $R_{13} = R_1 \parallel R_3 = \frac{70 \cdot 30}{70 + 30} = 21 \Omega$

$$R_{24} = R_2 \parallel R_4 = \frac{20 \cdot 5}{20 + 5} = 4 \Omega$$

Sp. delning

$$U_4 = U_0 \frac{R_{24}}{R_{24} + R_{13}} = 5 \cdot \frac{4}{4 + 21} = \frac{4}{5} \text{ V}$$

KCL i nod A $I_x + I_3 - I_4 = 0$

$$I_4 = \frac{U_4}{R_4} \quad ; \quad I_3 = \frac{U_0 - U_4}{R_3}$$

$$I_x = I_4 - I_3 = \frac{U_4}{R_4} - \frac{U_0 - U_4}{R_3} =$$


$$= \frac{4}{5 \cdot 5} - \frac{(5 - \frac{4}{5})}{30} = \frac{4}{25} - \frac{21}{5 \cdot 30} =$$

$$= \frac{1}{5} \left(\frac{4}{5} - \frac{7}{10} \right) = \frac{1}{5} \left(\frac{1}{10} \right) = \frac{1}{50} \text{ A}$$

Svar: $U_4 = \frac{4}{5} = 0,8 \text{ V}$

$$I_x = \frac{1}{50} = 0,02 \text{ A}$$

4. $j\omega$ -transformera kretsen

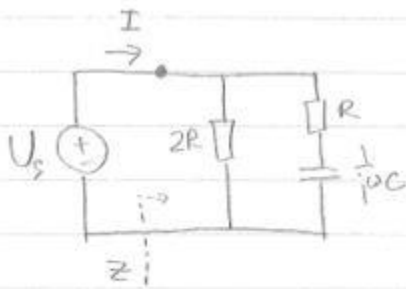

$$U_s(t) = 12 \cos(\omega t + 45^\circ) \text{ V}$$

$$\omega = 4000 \text{ rad/s}$$

$$R = 2.0 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{1}{4 \cdot 10^3 \cdot 250 \cdot 10^{-6}} = -j$$

$$Z = 2R \parallel \left(R + \frac{1}{j\omega C}\right) = \frac{2R(R + \frac{1}{j\omega C})}{2R + R + \frac{1}{j\omega C}} = \frac{4(2-j)}{6-j} =$$

$$= \frac{4(2-j)(6+j)}{(6-j)(6+j)} = \frac{4(12+1-16+j2)}{37} = \frac{4(13-j4)}{37}$$

Z mottager komplex effekt $S = P + jQ$


$$S = \frac{1}{2} U_s I^* = \frac{1}{2} U_s \left(\frac{U_s}{Z}\right)^* = \frac{1}{2} \frac{|U_s|^2}{Z^*} \cdot \frac{Z}{Z} =$$
$$= \frac{1}{2} \frac{|U_s|^2}{|Z|^2} Z$$

$$|Z| = \frac{4}{37} \sqrt{13^2 + 4^2} \approx 1.47$$

$$\text{Medel effekt } P = \text{Re}\{S\} = \frac{1}{2} \frac{|U_s|^2}{|Z|^2} \cdot \text{Re}\{Z\} =$$
$$= \frac{1}{2} \frac{12^2}{1.47^2} \cdot \frac{4}{37} \cdot 13 = 46.8 \text{ W}$$

Svar: $P = 46.8 \text{ W}$

2.

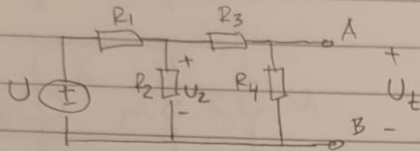

$$\begin{aligned} R_1 &= 200 \Omega \\ R_2 &= 300 \Omega \\ R_3 &= 60 \Omega \\ R_4 &= 220 \Omega \\ R_5 &= 100 \Omega \\ U &= 120 \text{ V} \end{aligned}$$

a) Tomgångsspänning U_t .

Sp. delning $U_2 = U \frac{R_2 \parallel (R_3 + R_4)}{R_1 + R_2 \parallel (R_3 + R_4)} =$

$$= U \frac{\frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}}{R_1 + \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}} = U \frac{1}{1 + \frac{R_1 (R_2 + R_3 + R_4)}{R_2 (R_3 + R_4)}}$$


$$= U \frac{1}{1 + \frac{200(300 + 60 + 220)}{300(60 + 220)}} = \frac{U}{1 + \frac{29}{21}} = 0,42 U = U_2$$

$$U_t = U_2 \frac{R_4}{R_3 + R_4} = \dots = 39,6 \text{ V}$$


Ekv. Resistans. (nollstätt U)

$$R_0 = R_4 \parallel \left(R_3 + R_1 \parallel R_2 \right) = \frac{R_4 \cdot \left(R_3 + \frac{R_1 R_2}{R_1 + R_2} \right)}{R_4 + R_3 + \frac{R_1 R_2}{R_1 + R_2}} = \dots = 99 \Omega$$

Svar a)

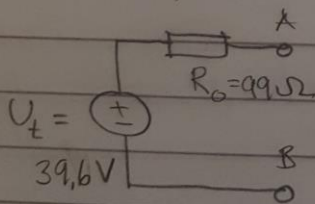

b)

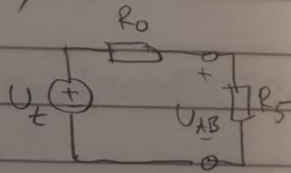


Sp. delning ger

$$U_{AB} = U_t \cdot \frac{R_5}{R_0 + R_5}$$

$$U_{AB} = 39,6 \cdot \frac{100}{99 + 100} = \underline{\underline{19,9 \text{ V}}}$$

5

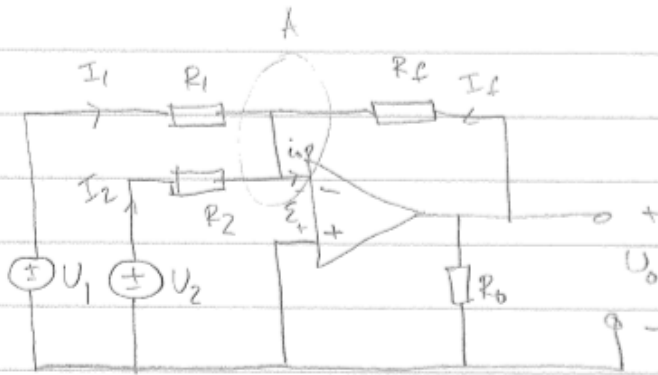

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 20 \text{ k}\Omega$$

$$R_f = 30 \text{ k}\Omega$$

$$R_0 = 10 \text{ k}\Omega$$

$$\left. \begin{array}{l} \text{Ideal op. först.} \\ \text{Neg. återkoppl.} \end{array} \right\} \Rightarrow \left\{ \begin{array}{l} \varepsilon = 0 \\ i_{op} = 0 \end{array} \right.$$

Summera strömmar i nod A (KCL)


$$I_1 + I_2 + I_f = 0$$

$$\frac{U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_o}{R_f} = 0$$

$$U_o = -U_1 \frac{R_f}{R_1} - U_2 \frac{R_f}{R_2} =$$

$$= -U_1 \frac{30}{10} - U_2 \frac{30}{20} = -3 \left(U_1 + \frac{1}{2} U_2 \right) \text{ V}$$

| U_1 [V] | U_2 [V] | $U_o = -3 \left(U_1 + \frac{1}{2} U_2 \right)$ [V] |
|-----------|-----------|--|
| 1 | 1 | -4.5 |
| 1 | -1 | -1.5 |
| 0 | -2 | 3 |
| -2 | 4 | 0 |

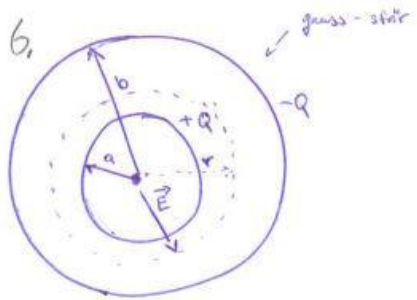

a) $r < a$ $\vec{E} = 0$ Laddningen innesluten i en Gauss-sfär med radie r är 0

$a < r < b$

$$\oiint \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0}$$

$$E \cdot 4\pi r^2 = \frac{Q}{\epsilon_0}$$

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

riktningen: radiellt utåt

$$\vec{E} = \frac{Q}{4\pi\epsilon_0 r^2} \hat{r}$$

$r > b$ $\vec{E} = 0$

b)

