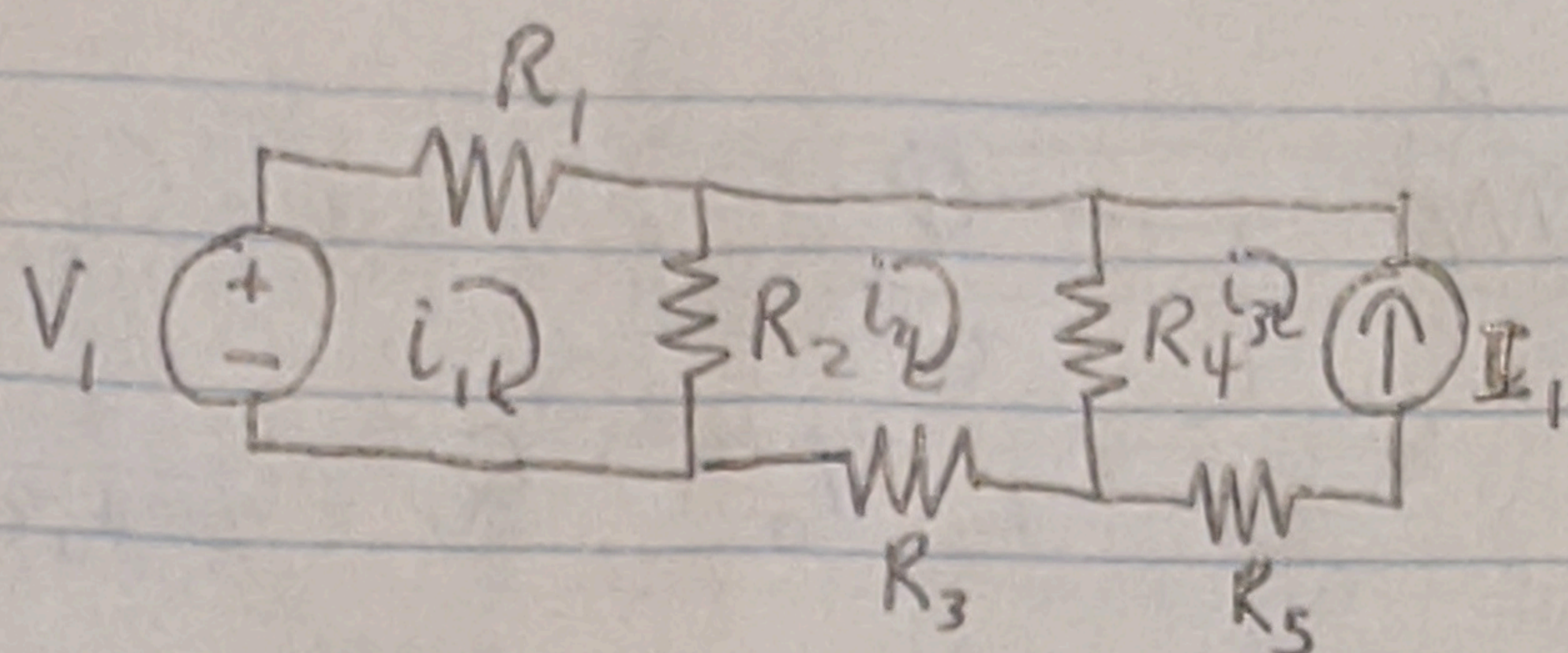


1.1)



$$-V_1 + R_1 i_1 + R_2 (i_1 - i_2) = 0$$

$$R_2 (i_2 - i_1) + R_4 (i_2 - i_3) + R_3 i_2 = 0$$

$$i_3 = -I_1$$

$$i_1 (R_1 + R_2) - i_2 (R_2) = V_1$$

$$-i_1 (R_2) + i_2 (R_2 + R_4 + R_3) = -I_1 R_4$$

$$i_1 (4.0 \text{ k}\Omega) - i_2 (2.7 \text{ k}\Omega) = 15 \text{ V}$$

$$-i_1 (2.7 \text{ k}\Omega) + i_2 (11.7 \text{ k}\Omega) = (-10 \text{ mA})(4.3 \text{ k}\Omega)$$

$$i_1 = 1.50 \text{ mA} \quad i_2 = -8.333 \text{ mA}$$


$$V_2 = (i_1 - i_2) R_2 = (4.83 \text{ mA})(2.7 \text{ k}\Omega) = \boxed{13.04 \text{ V}}$$

$$i_4 = i_2 - i_3 = \boxed{-6.6 \text{ mA}}$$

$$P = VI = (IR)I = I^2 R$$

$$P_{\text{tot}} = (i_1)^2 R_1 + (i_1 - i_2)^2 R_2 + (i_2)^2 R_3 + (i_2 - i_3)^2 R_4 + i_3^2 R_5 = \boxed{529 \text{ mW}}$$

1.2)

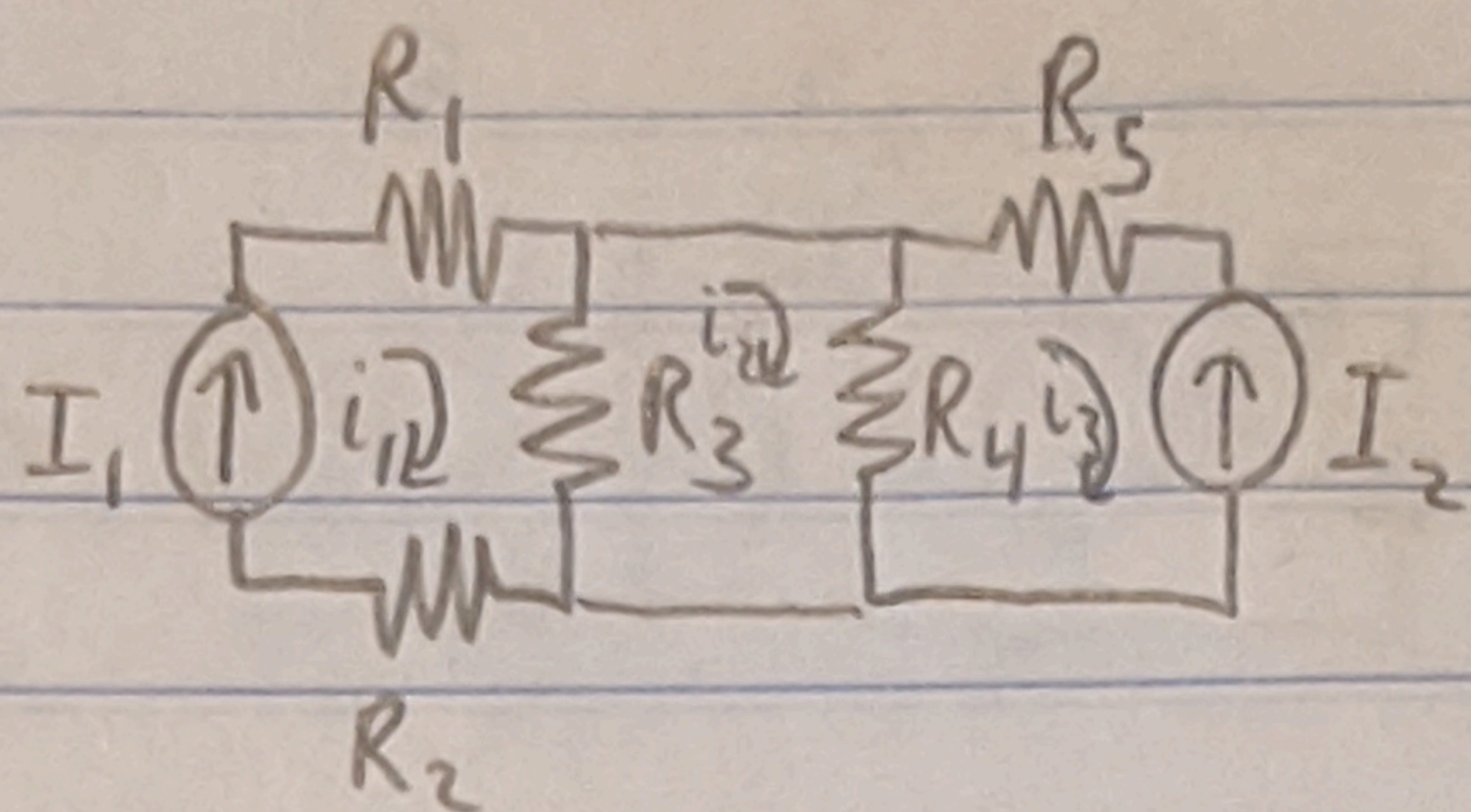

$$i_1 = I_1 \quad i_3 = -I_2$$

$$R_3(i_2 - i_1) + R_4(i_2 - i_3) = 0 \Rightarrow i_2(R_3 + R_4) = i_1 R_3 + i_3 R_4$$


$$i_2 = \frac{i_1 R_3 + i_3 R_4}{R_3 + R_4} = -8.43 \text{ mA}$$

$$v_3 = (i_1 - i_2) R_3 = \boxed{49.76 \text{ V}} \quad i_{R_4} = i_2 - i_3 = \boxed{11.57 \text{ mA}}$$

$$P_{\text{tot}} = (i_1)^2 R_1 + (i_1)^2 R_2 + (i_1 - i_2)^2 R_3 + (i_2 - i_3)^2 R_4 + (i_3)^2 R_5$$

$$= \boxed{2.97 \text{ W}}$$

1.3)

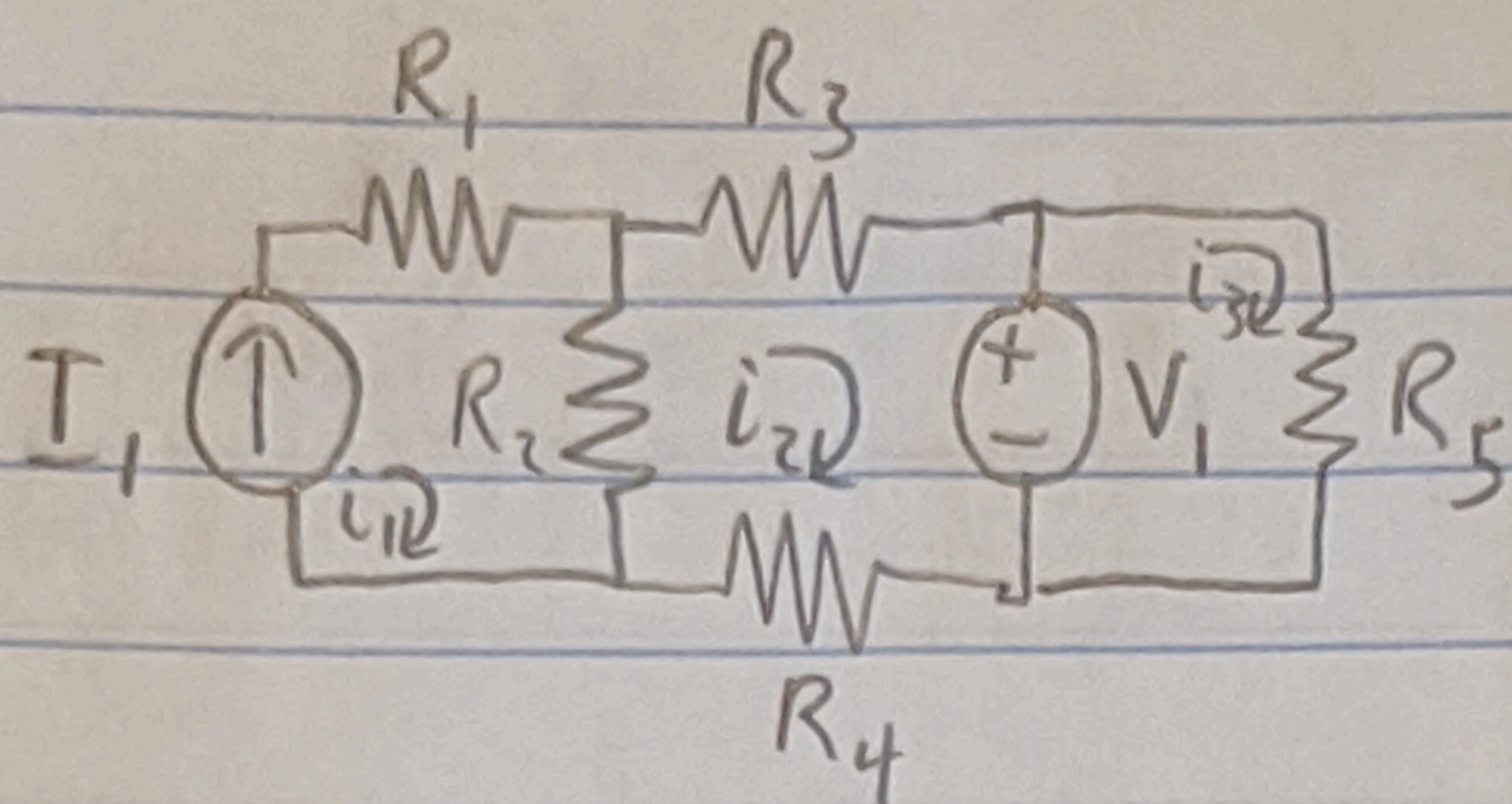

$$i_1 = I_1$$

$$R_2(i_2 - i_1) + R_3 i_2 + V_1 + R_4 i_2 = 0$$

$$-V_1 + R_5 i_3 = 0 \Rightarrow i_3 = \frac{V_1}{R_5} = \boxed{6.82 \text{ mA}}$$

$$i_2(R_2 + R_3 + R_4) = -V_1 + R_2 i_1 \Rightarrow \boxed{i_2 = 1.03 \text{ mA}}$$


$$V_{R_2} = (i_1 - i_2) R_2 = \boxed{24.23 \text{ V}}$$

$$i_{R_4} = i_2 = \boxed{1.03 \text{ mA}}$$

$$P_{\text{tot}} = (i_1)^2 R_1 + (i_1 - i_2)^2 R_2 + (i_2)^2 R_3 + (i_2)^2 R_4 + (i_3)^2 R_5$$

$$= \boxed{0.46 \text{ W}}$$

1.4)

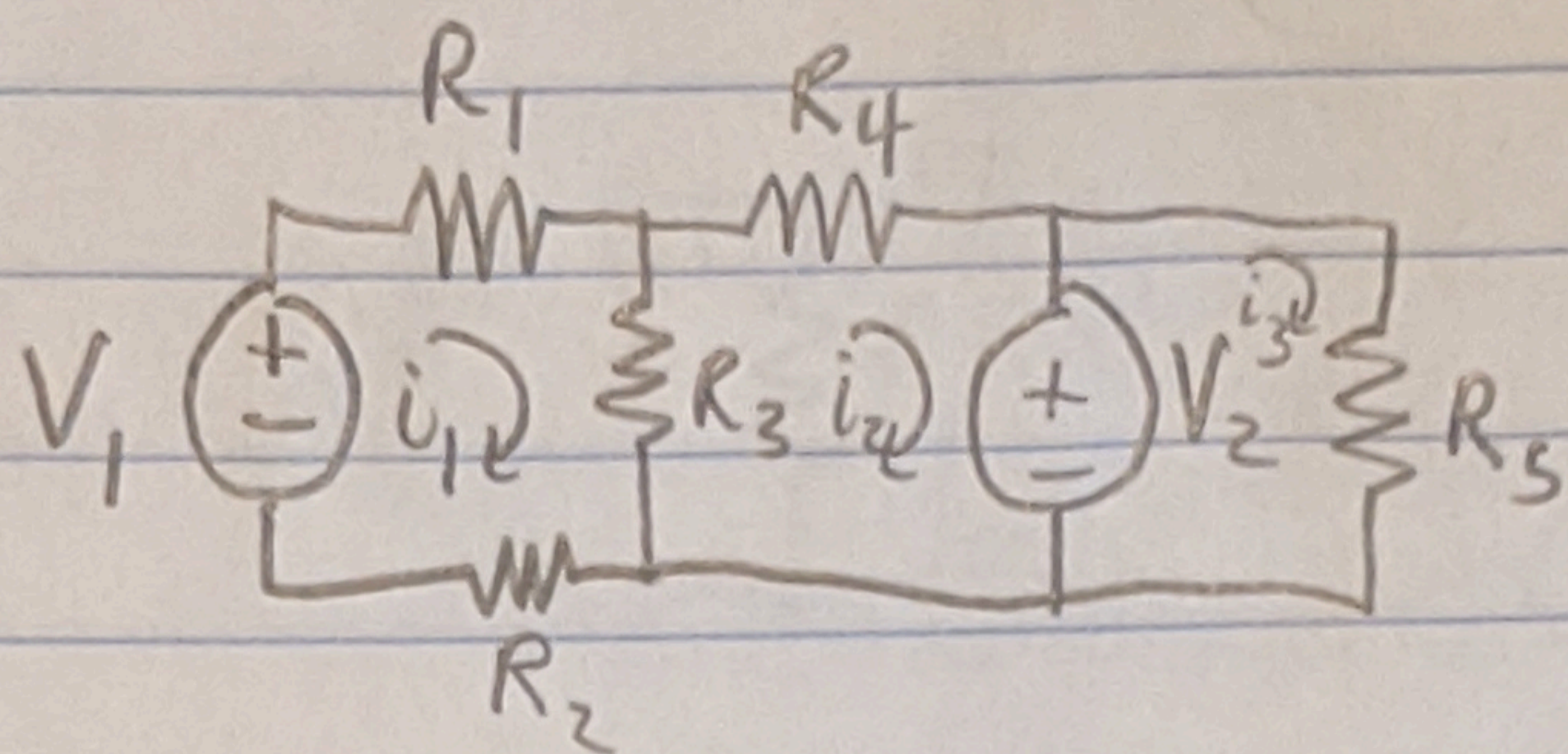

$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) + R_2 i_1 = 0$$

$$R_3 (i_2 - i_1) + R_4 i_2 + V_2 = 0$$

$$-V_2 + R_5 i_3 = 0$$

$$i_1 = 0.55 \text{ mA}$$

$$i_2 = -1.93 \text{ mA}$$

$$i_3 = 6.82 \text{ mA}$$


$$V_{R_3} = (i_1 - i_2) R_3 = 6.70 \text{ V}$$

$$i_{R_4} = i_2 = -1.93 \text{ mA}$$

$$P_{\text{tot}} = (i_1)^2 R_1 + (i_1)^2 R_2 + (i_1 - i_2)^2 R_3 + (i_2)^2 R_4 + (i_3)^2 R_5$$

$$= 137 \text{ mW}$$

2.1)

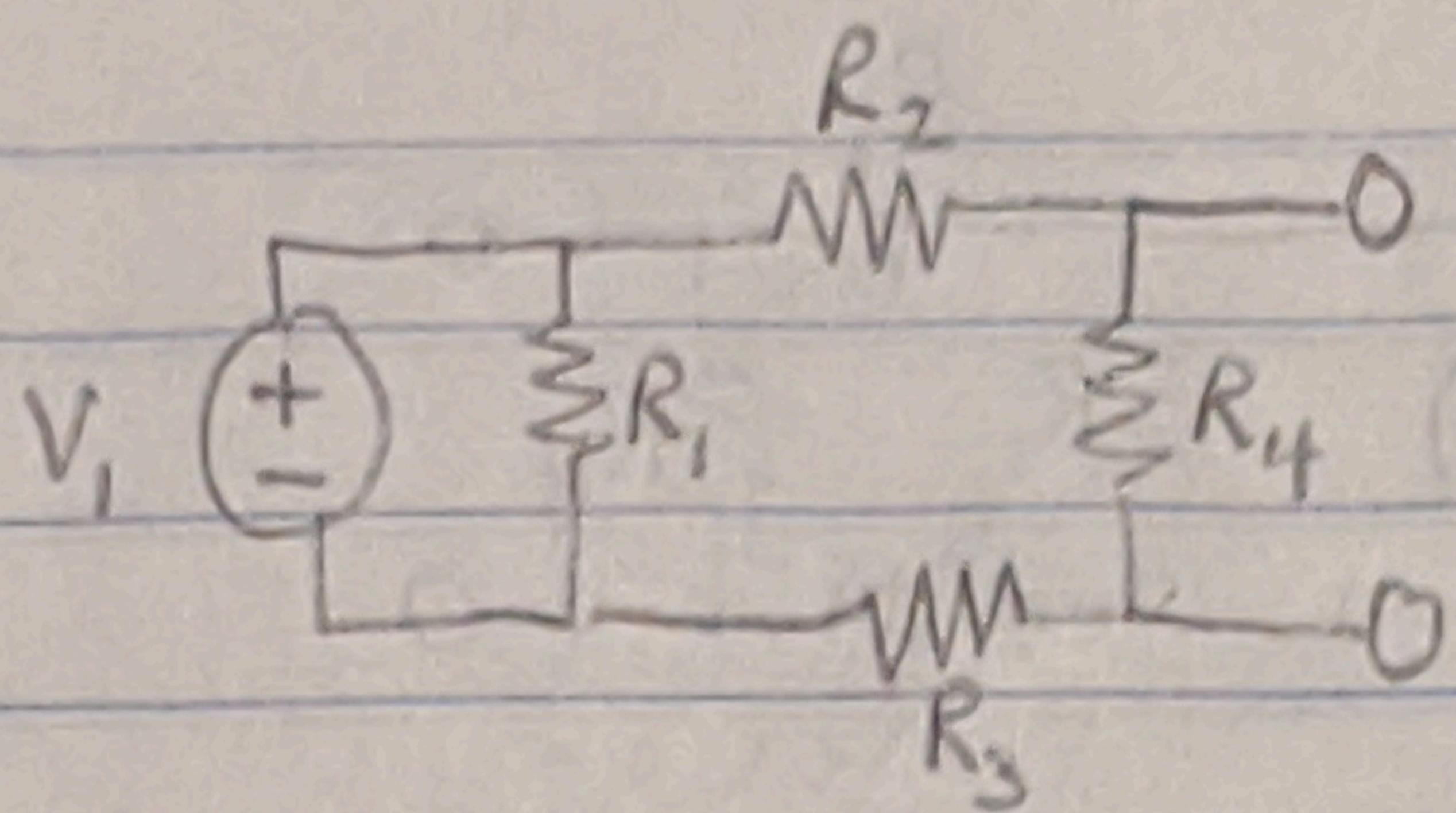


$$a) R_{eq} = (R_2 + R_3) // R_4 = \left[(R_2 + R_3)^{-1} + R_4^{-1} \right]^{-1} = \boxed{530 \Omega}$$

$$V_{Th} = V_{R_4} = \frac{R_4}{R_2 + R_3 + R_4} V_1 = \boxed{5.30 V}$$

$$I_N = \frac{V_{Th}}{R_{eq}} = \boxed{10 mA}$$
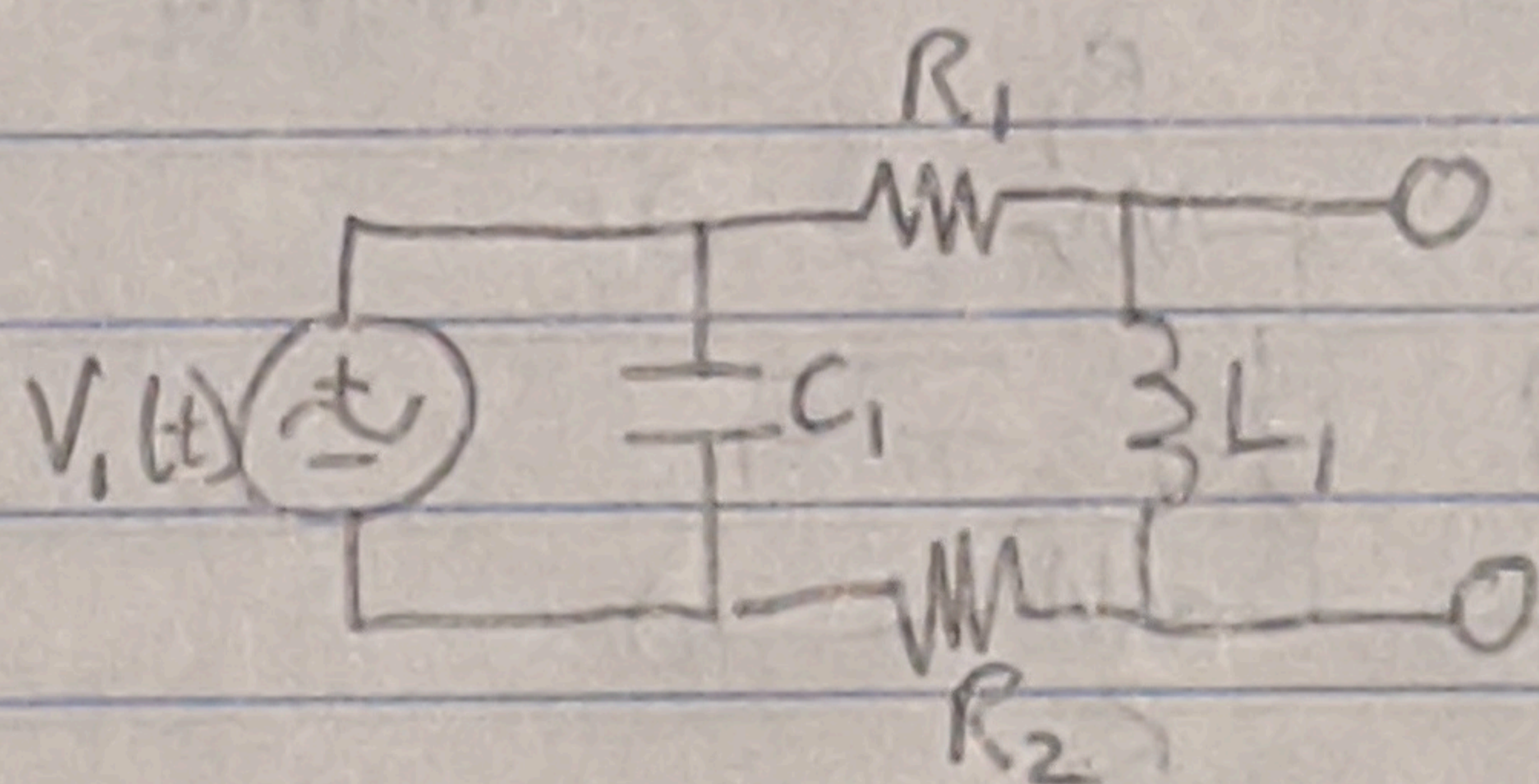
$$b) R_L = R_{eq} = \boxed{530 \Omega} \quad P_{max} = \frac{(V_{Th})^2}{R_{eq} + R_L} = \boxed{26.5 mW}$$



$$c) Z_{eq} = (R_1 + R_2) // Z_L = \left[(R_1 + R_2)^{-1} + Z_L^{-1} \right]^{-1} = \boxed{376 \angle -89.99 m\Omega}$$


$$V_{Th} = V_L = \frac{Z_L}{R_1 + R_2 + Z_L} V_1 = \boxed{3.8 \angle -89.99 mV}$$

$$I_N = \frac{V_{Th}}{Z_{eq}} = \boxed{10 \angle 0 mA}$$

$$d) Z_{load} = \overline{Z_{eq}} = \boxed{376 \angle -89.99 m\Omega}$$

$$P_{max} = \frac{(V_{rms})^2}{R_{eq} + R_{load}} = \frac{V_m^2}{2(R_{eq} + R_{load})} = \boxed{60 mW}$$

22)

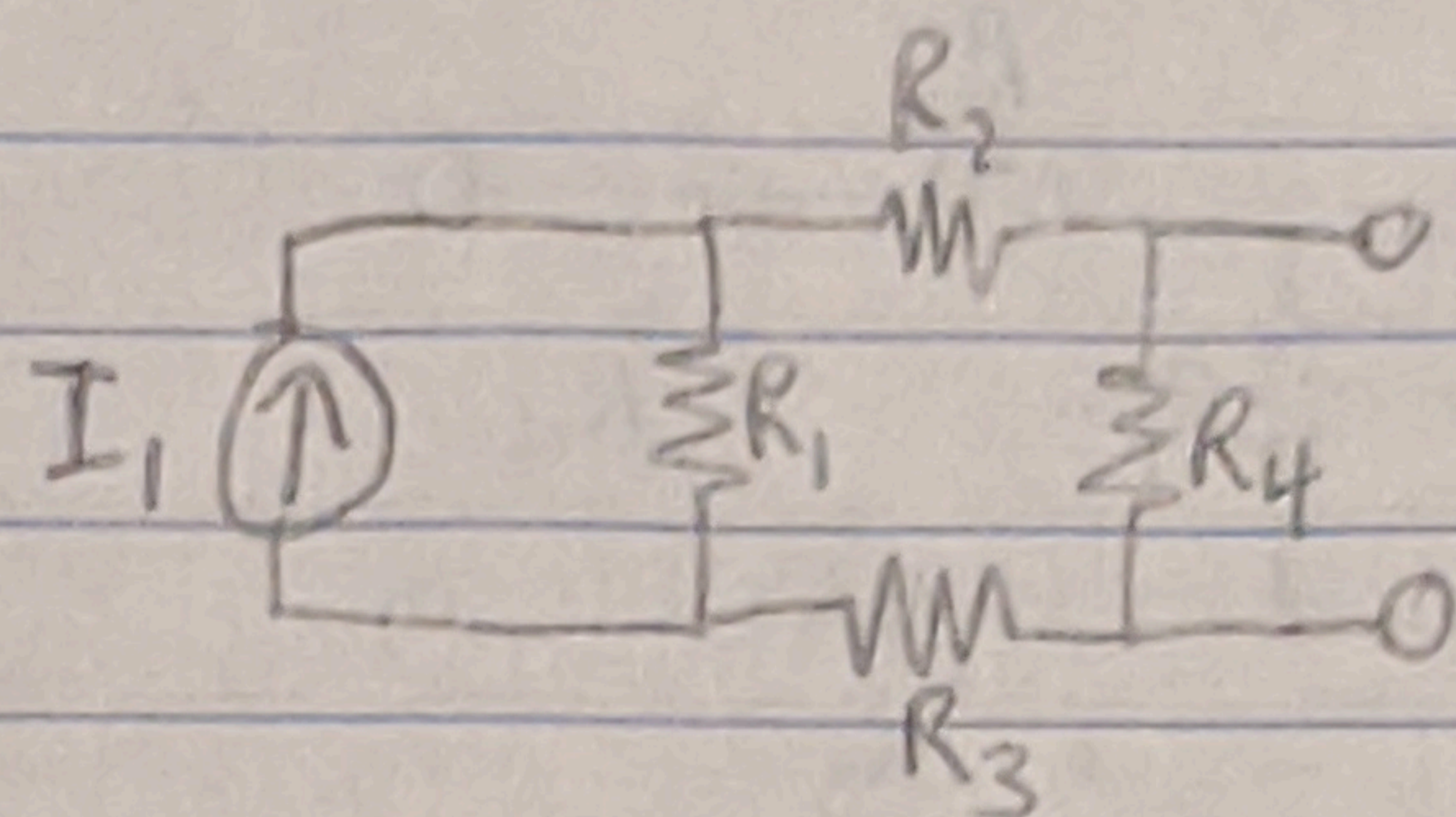


$$a) R_{eq} = (R_1 + R_2 + R_3) // R_4 = \left[(R_1 + R_2 + R_3)^{-1} + R_4^{-1} \right]^{-1} = \boxed{553 \Omega}$$

$$I_N = I_2 = I_3 = I_1 \frac{R_1}{R_1 + R_2 + R_3} = \boxed{94.6 \text{ mA}}$$

$$V_{th} = I_N R_{eq} = \boxed{52.31 \text{ V}}$$
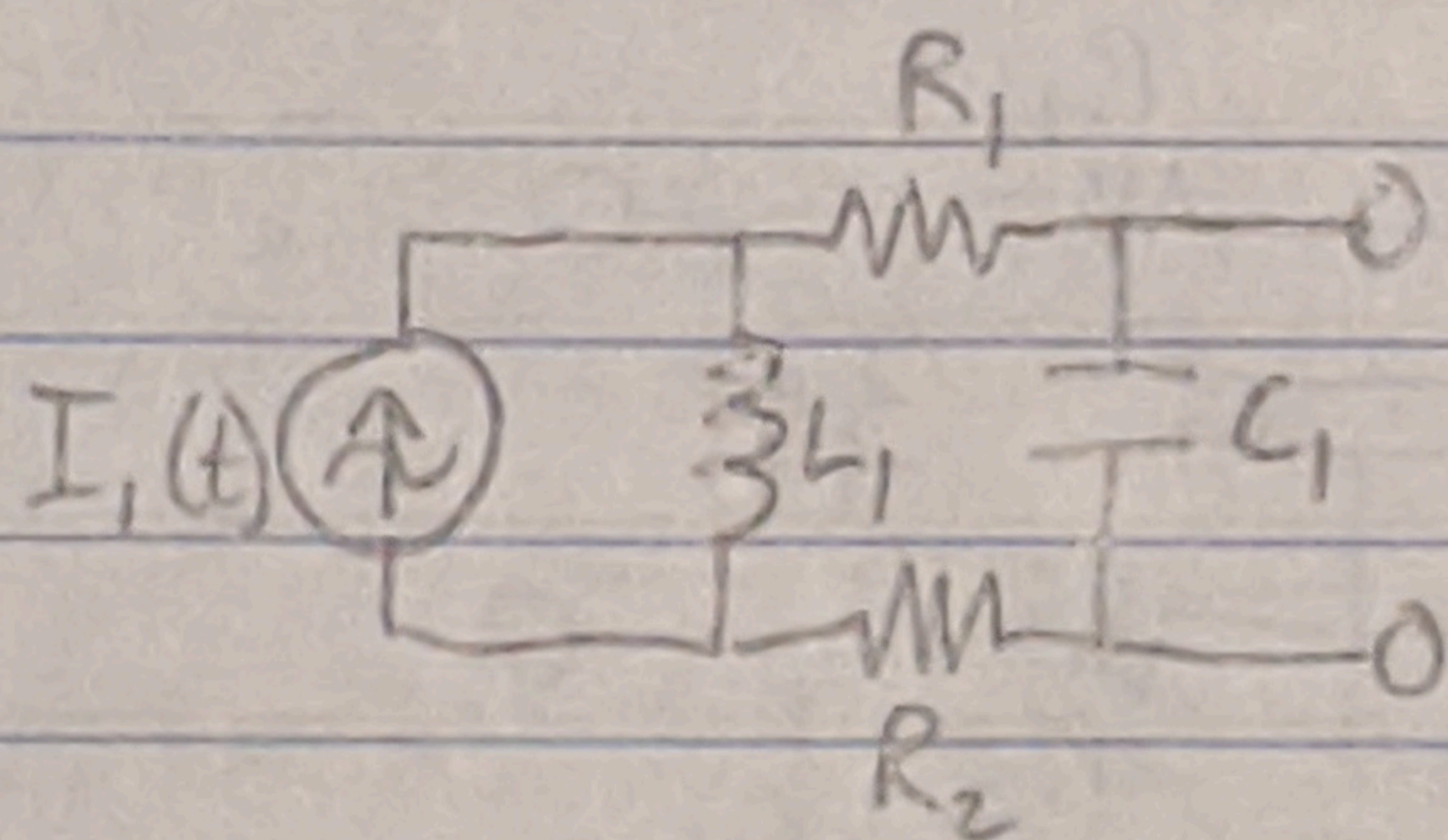
$$b) R_L = R_{eq} = \boxed{553 \Omega} \quad P_{max} = \frac{V_{th}^2}{R_{eq} + R_L} = \boxed{2.45 \text{ W}}$$



$$c) Z_{eq} = (Z_L + R_1 + R_2) // Z_C = \left[(Z_L + R_1 + R_2)^{-1} + Z_C^{-1} \right]^{-1} = \boxed{2.31 \angle -16^\circ \text{ k}\Omega}$$


$$I_N = I_1 = I_2 = I_1(t) \frac{Z_L}{Z_L + R_1 + R_2} = \boxed{78.3 \angle 89.99^\circ \text{ mA}}$$

$$V_{th} = I_N Z_{eq} = \boxed{181 \angle -73.93^\circ \text{ mV}}$$

$$d) Z_{load} = \overline{Z_{eq}} = \boxed{2.31 \angle 16^\circ \text{ k}\Omega}$$


$$P_{max} = \frac{(V_{rms})^2}{R_{eq} + R_{load}} = \frac{V_m^2}{2(R_{eq} + R_{load})} = \boxed{3.68 \text{ mW}}$$

3.1)

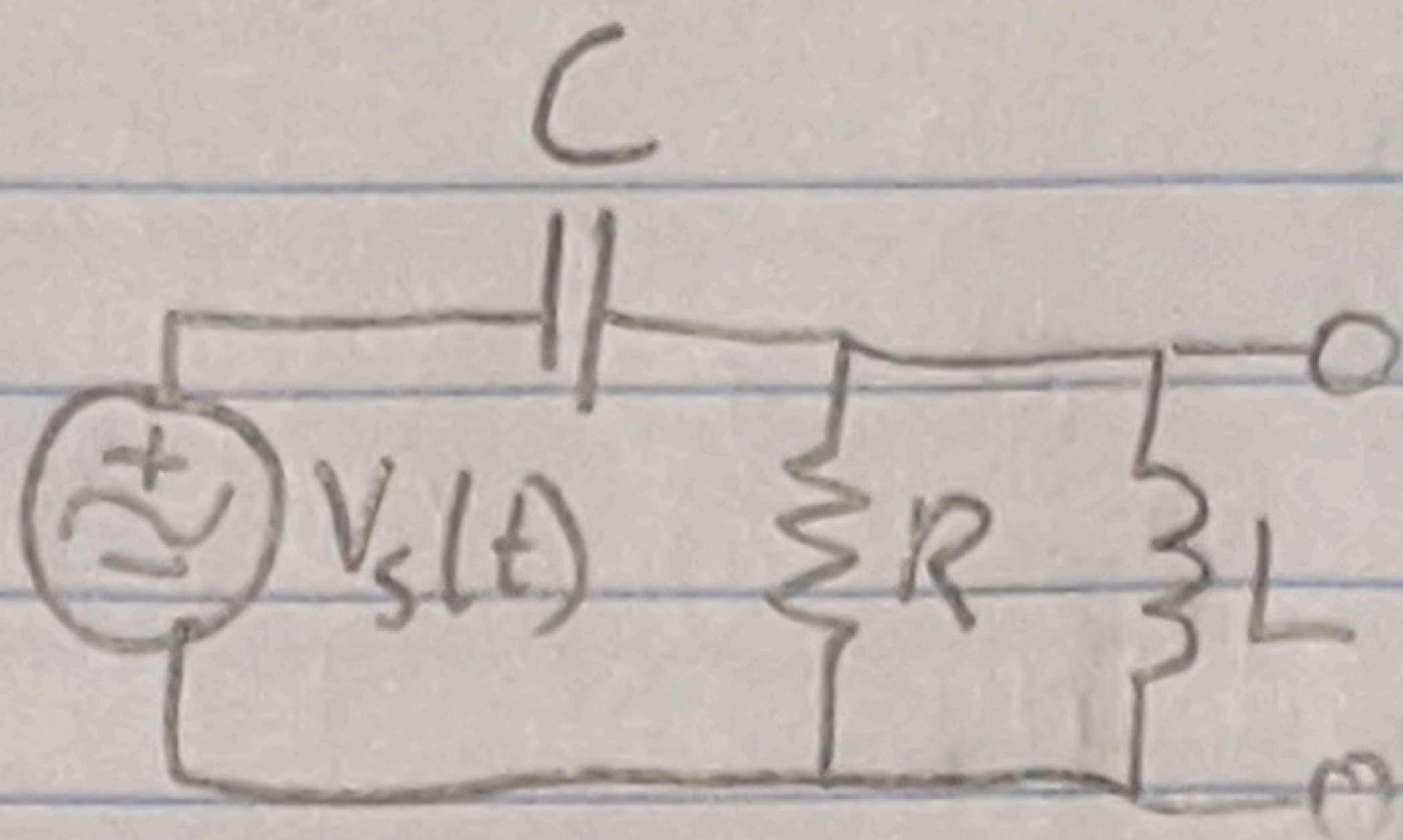


$$a) Z_{eq} = R // Z_L // Z_C = (R^{-1} + Z_L^{-1} + Z_C^{-1})^{-1} = \boxed{99.76 \angle -4.00^\circ \Omega}$$
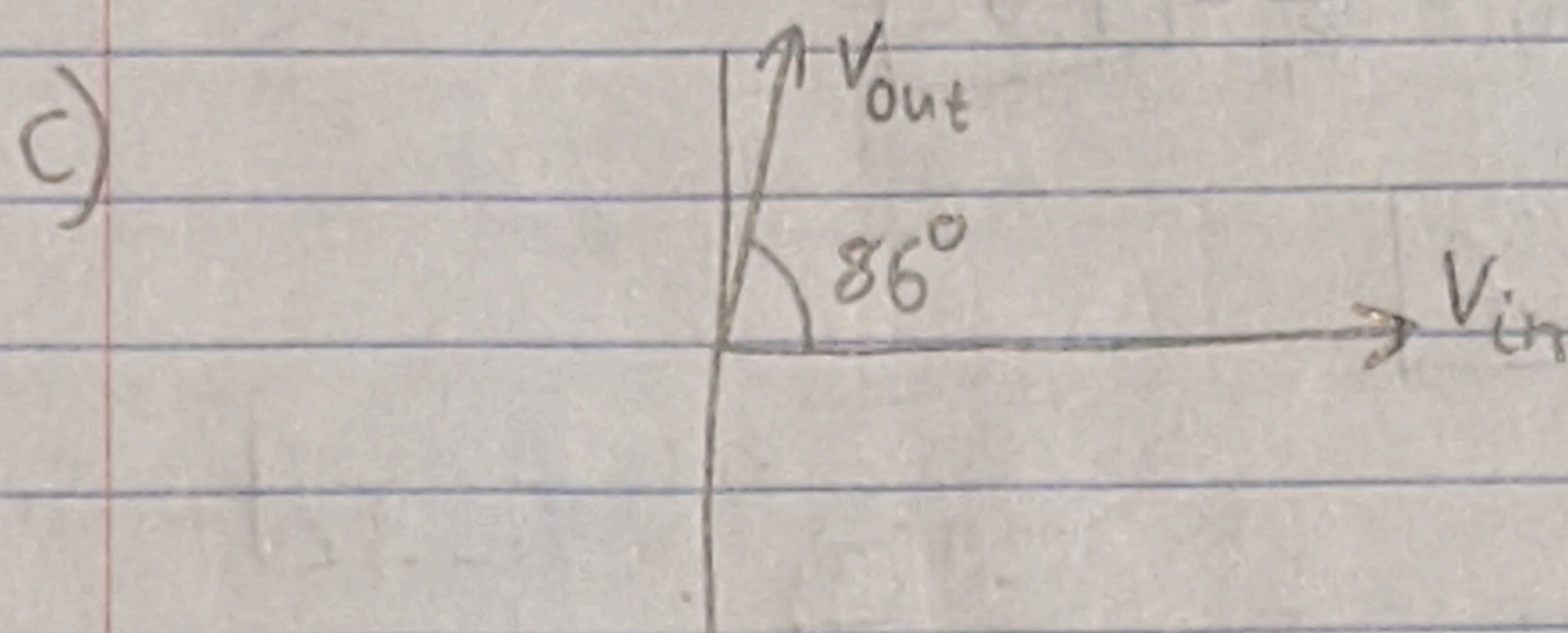
$$b) V_{out} = V_R = V_L = V_C = V_s \frac{R // Z_L}{R // Z_L + Z_C} = V_s \frac{(R^{-1} + Z_L^{-1})^{-1}}{Z_{eq}} = \boxed{13.17 \angle 86^\circ V}$$




$$d) \text{Im}\{(R^{-1} + Z_L^{-1})^{-1}\} = \frac{1}{\omega C} \Rightarrow C = \left[\text{Im}\{(R^{-1} + Z_L^{-1})^{-1}\} \cdot \omega \right]^{-1} = \boxed{51.25 \mu F}$$

3.2)

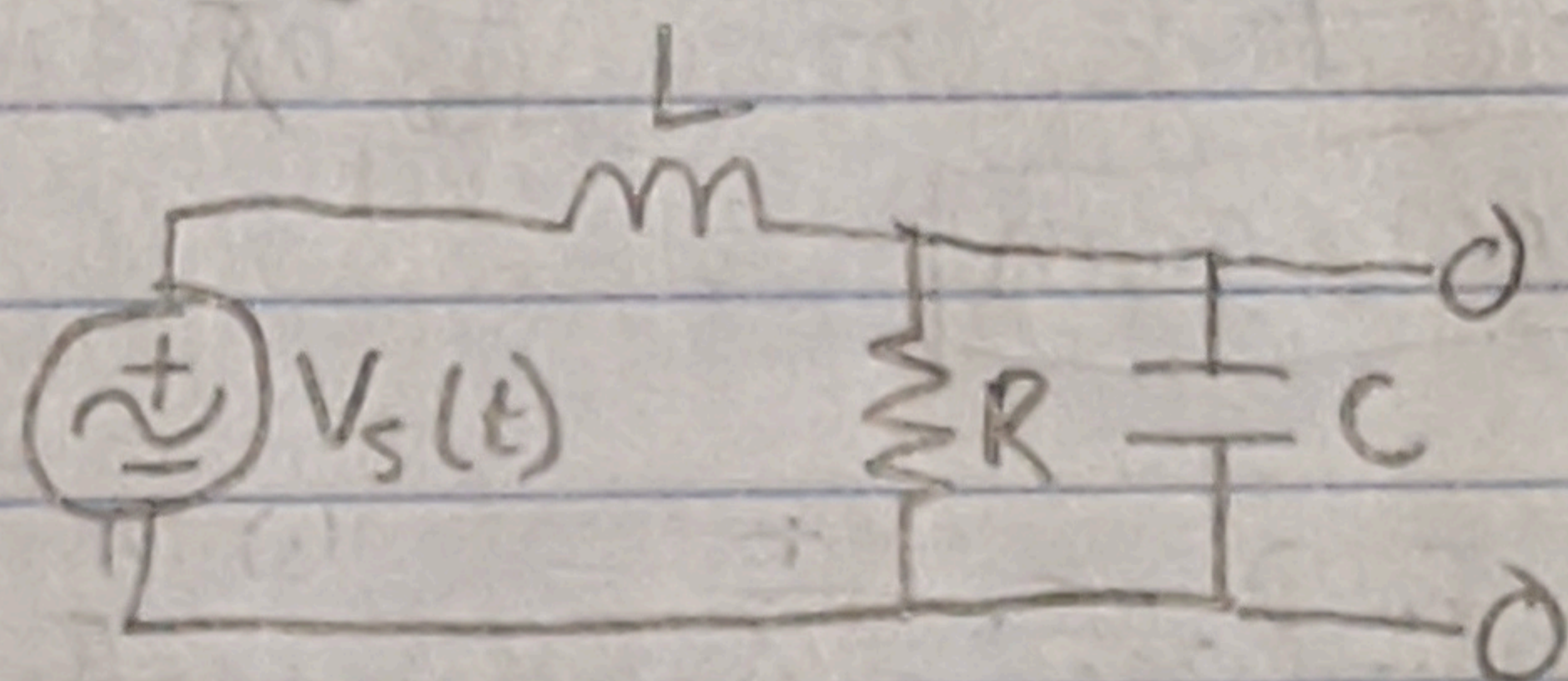


$$a) Z_{eq} = (R // Z_C // Z_L = (R^{-1} + Z_C^{-1} + Z_L^{-1})^{-1} = \boxed{93.79 \angle 20.30^\circ \Omega}$$
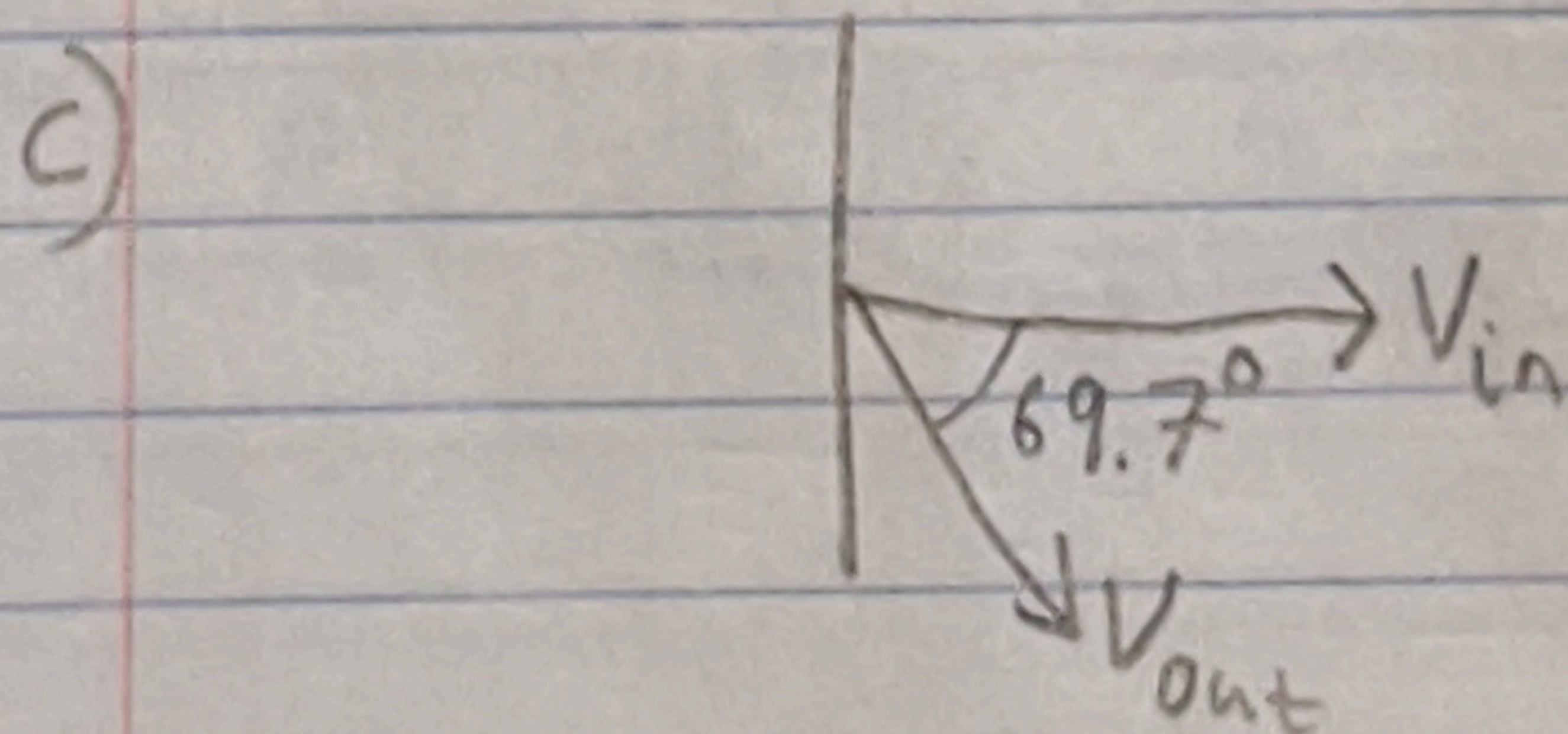
$$b) V_{out} = V_R = V_C = V_L = V_s \frac{R // Z_C}{R // Z_C + Z_L} = \boxed{11.72 \angle -69.7^\circ V}$$



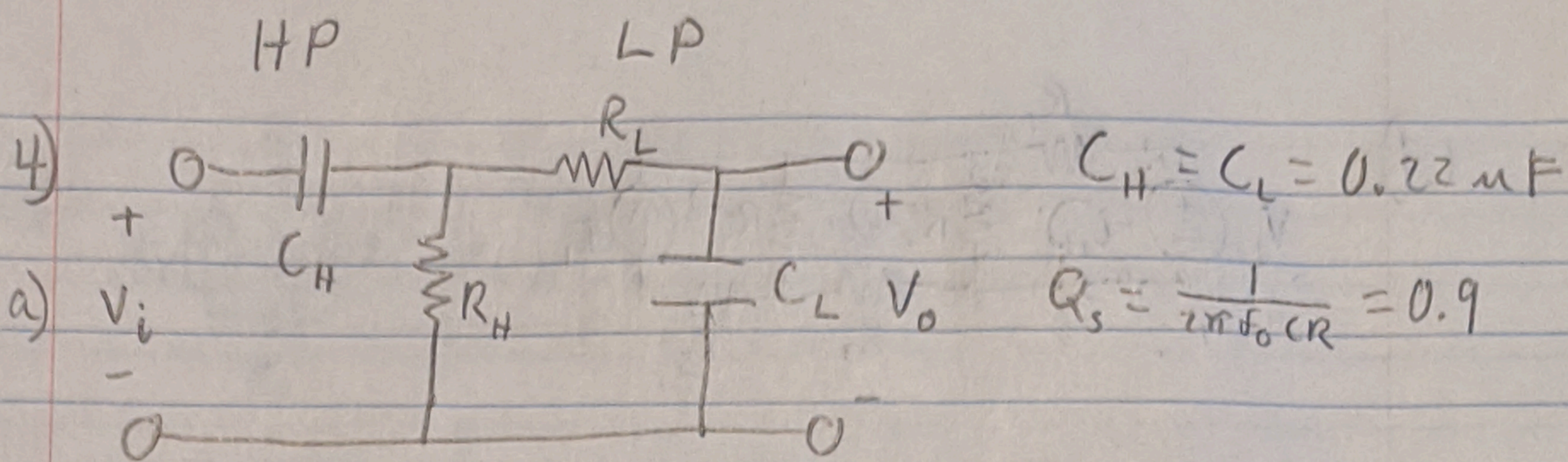
$$d) \text{Im}\{(R^{-1} + Z_C^{-1})^{-1}\} = \omega L \Rightarrow \boxed{L = 124 \mu H}$$






$$f_H = \frac{1}{2\pi R_H C_H} = 3400 \text{ Hz} \rightarrow R_H = (2\pi f_H C_H)^{-1} = \boxed{213 \Omega}$$
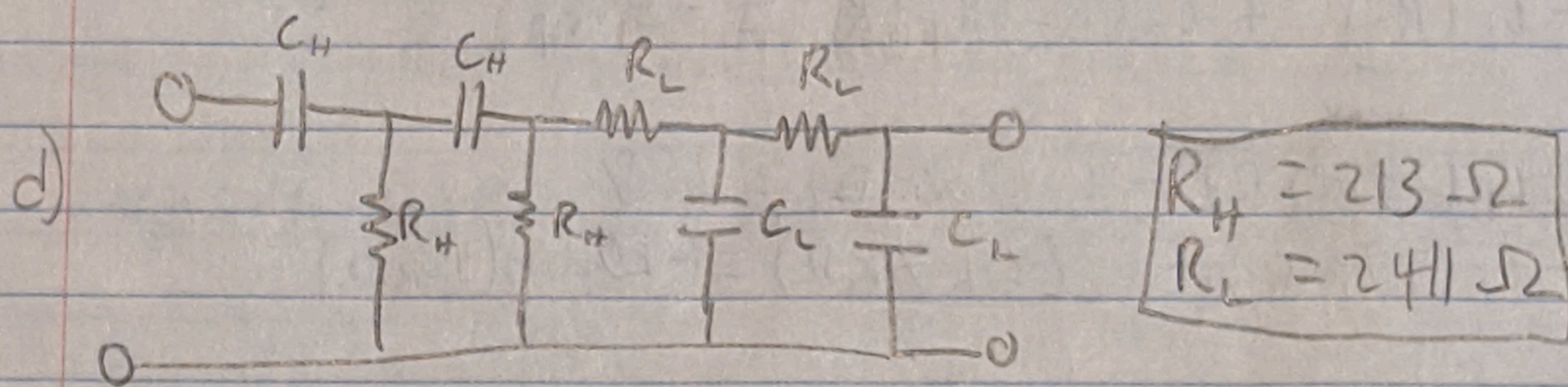
$$f_L = \frac{1}{2\pi R_L C_L} = 300 \text{ Hz} \rightarrow R_L = (2\pi f_L C_L)^{-1} = \boxed{2411 \Omega}$$




b) Passive first-order bandpass filter

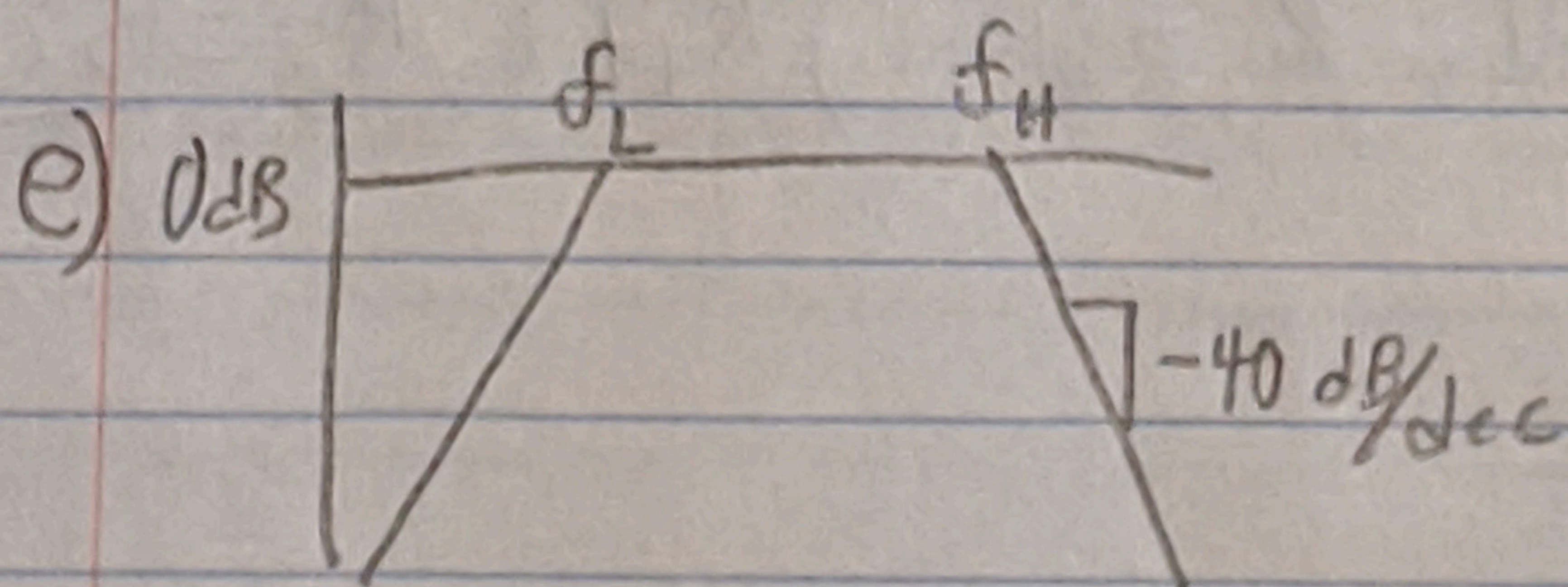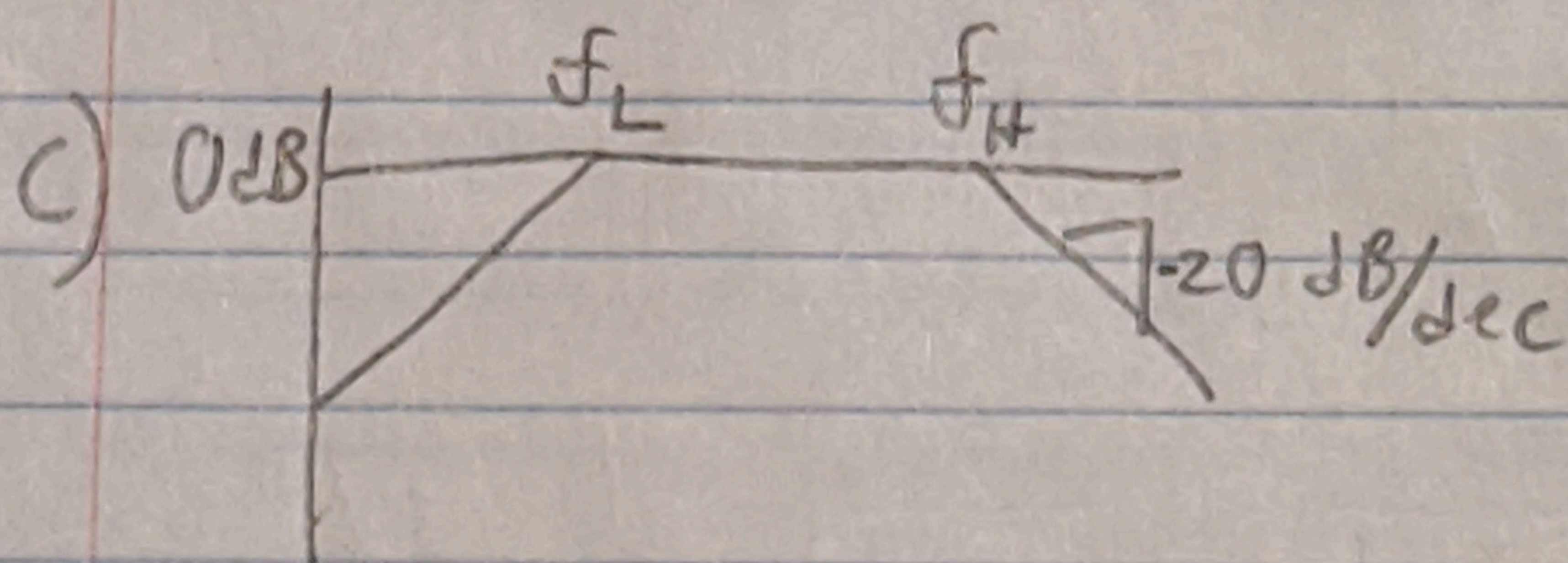

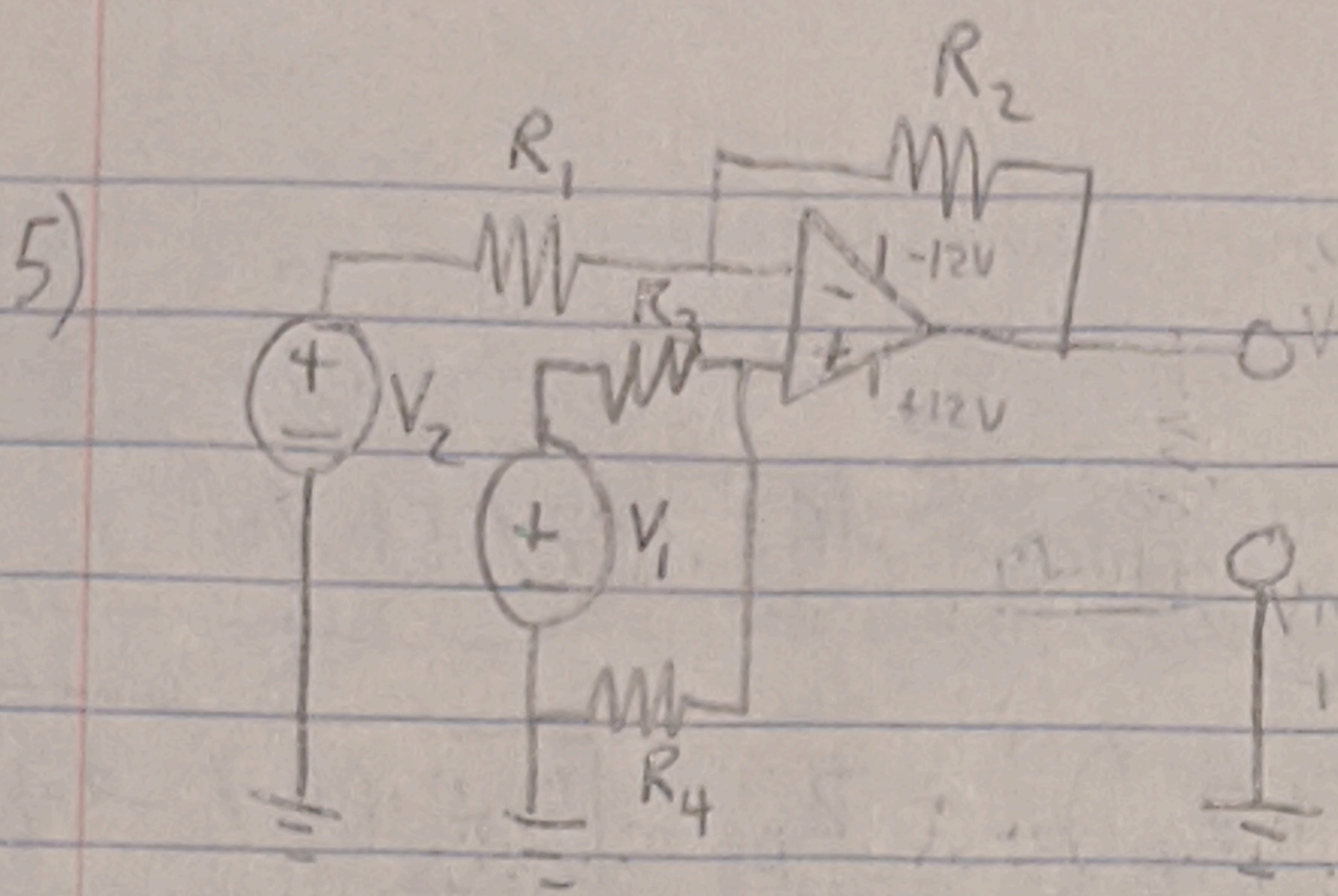


$$a) V_o = \frac{R_2}{R_1} (V_1 - V_2) \Rightarrow A_v = \frac{R_2}{R_1} = \boxed{4.62}$$

$$b) |V_1 - V_2|_{\max} = \frac{V_+}{A_v} = \boxed{2.6}$$

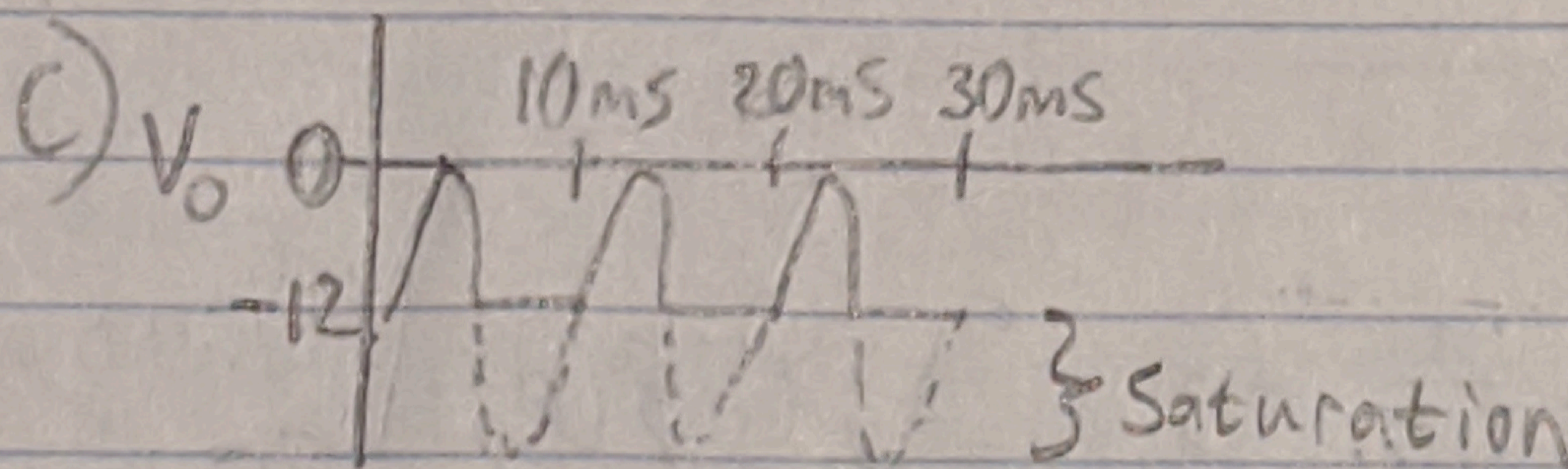

d) Finite impedance \rightarrow current leak through op-amp
 \rightarrow reduced gain

a)

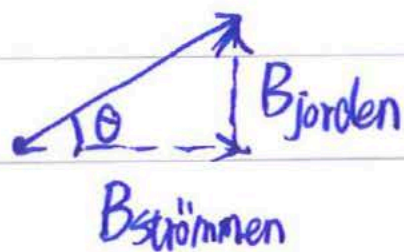

$$\tan \theta = \frac{B_{\text{jorden}}}{B_{\text{strömmen}}}$$

$$\Rightarrow B_{\text{strömmen}} = \frac{B_{\text{jorden}}}{\tan 45^\circ}$$

$$= B_{\text{jorden}} = 50 \cdot 10^6 \text{ T}$$

b) Enligt Ampères lag:

$$\oint_C \vec{B} \cdot d\vec{l} = \mu_0 I \Rightarrow B \cdot 2\pi d = \mu_0 I$$

$$\Rightarrow I = \frac{B \cdot 2\pi d}{\mu_0} = 2.5 \cdot 10^{14} \text{ A}$$