

Lösningar Kretsanalys april 2013

1a. $V = 325 \angle 0^\circ \text{ V}$ $S = 1500 + j 3000 \text{ VA} = 3354 \angle 63,4^\circ \text{ VA}$

$$S = \frac{V \cdot I^*}{2} \Rightarrow I^* = \frac{2S}{V} = \frac{2 \cdot 3354 \angle 63,4^\circ}{325 \angle 0^\circ} \text{ A} = 20,64 \angle 63,4^\circ \text{ A}$$

$$\Rightarrow I = 20,64 \angle -63,4^\circ \text{ A} \Rightarrow$$


$$\underline{i(t) = 20,64 \cos(314t - 63,4^\circ) \text{ A}}$$

1b. $Z = \frac{V}{I} = \frac{325 \angle 0^\circ \text{ V}}{20,64 \angle -63,4^\circ \text{ A}} = 15,7 \angle -63,4^\circ \Omega =$


$= 7,05 + j14,1 \Omega = R + j\omega L$ eftersom $\text{Re} Z < \text{Im} Z$
den är induktiv \Rightarrow

$$\underline{R = 7,05 \Omega} \quad L = \frac{X}{\omega} = \frac{14,1}{314} \text{ H} = \underline{44,8 \text{ mH}}$$

3a

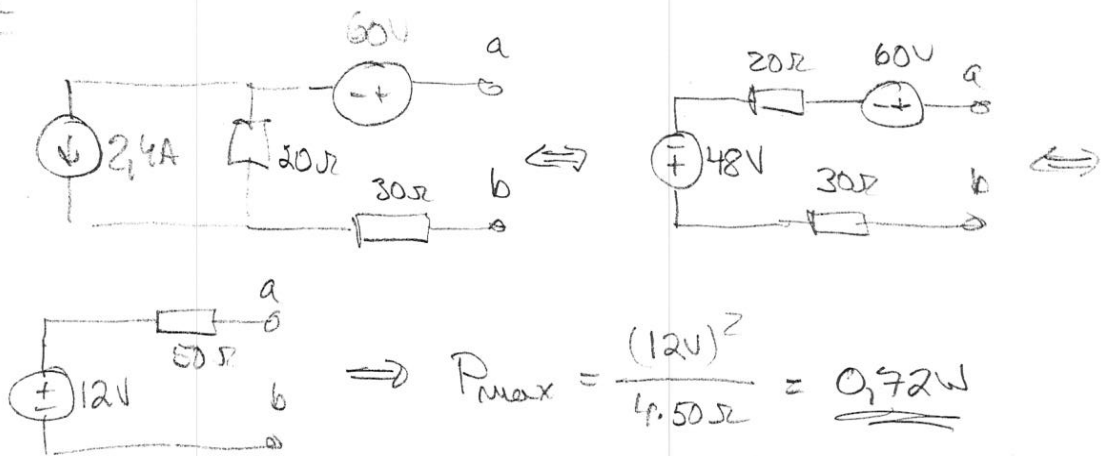

3b

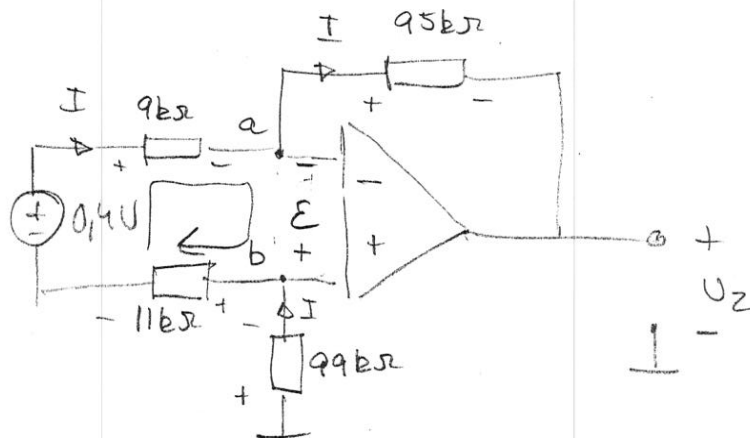

Ideal nichtgekoppelt OP \Rightarrow

- instrommar = 0
- $V_a = V_b = 0 \Leftrightarrow \Sigma = 0$.

• $U_a = V_a - 95k\Omega \cdot I$

• $V_b = V_b$



• I ges au Kirchhoff: $+0.4V - 9k\Omega \cdot I + \varepsilon - 11k\Omega \cdot I = 0$

$\Rightarrow I = \frac{0.4V}{9k\Omega + 11k\Omega} = 20\mu A$

• $V_b = 0 - 99k\Omega \cdot 20\mu A = -1.98V \Rightarrow$

$U_2 = -1.98V - 95k\Omega \cdot 20\mu A = \underline{\underline{-3.88V}}$

2. Schema for $t > 0$

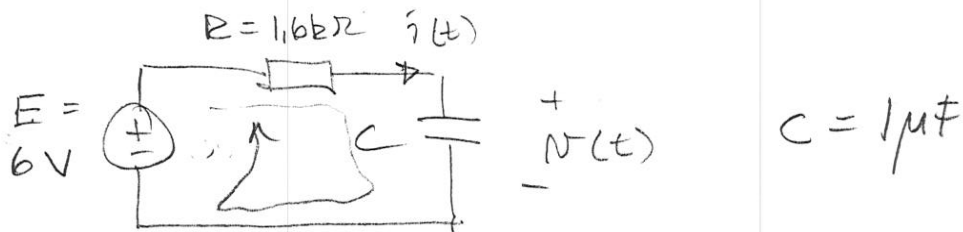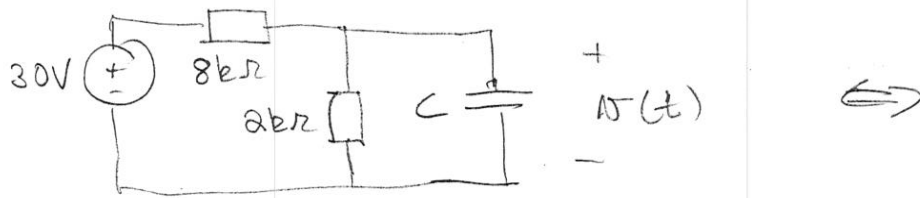

$V(t)$ ges. aus Kirchhoff:

$$+E - R \cdot i(t) - V(t) = 0, \text{ da} \bar{i}(t) = C \cdot \frac{dV}{dt} \Rightarrow$$

$$E - RC \frac{dV}{dt} - V(t) = 0 \Rightarrow \frac{dV}{dt} + \frac{1}{RC} \cdot V(t) = \frac{E}{RC}$$

$$\underline{V_h(t)} \quad \frac{dV}{dt} + \frac{1}{RC} \cdot V = 0 \Rightarrow V = A \cdot e^{-\frac{t}{RC}}$$

$$\underline{V_p(t)} \quad \text{Ansatz } V_p(t) = B \text{ (konstant)} \Rightarrow$$

$$0 + \frac{1}{RC} \cdot B = \frac{E}{RC} \Rightarrow B = E \Rightarrow$$

$$V(t) = V_h(t) + V_p(t) = A \cdot e^{-\frac{t}{RC}} + E$$

$$V(0) = 30V \Rightarrow$$



$$30V = A \cdot 1 + E = A + 6V \Rightarrow A = 24V \Rightarrow$$


$$V(t) = 24 \cdot e^{-\frac{t}{RC}} + 6V = \underline{\underline{24 \cdot e^{-\frac{t}{16ms}} + 6V}}$$

4a

$$H(\omega) = \frac{j\omega(10^6 + j\omega)}{(1000 + j10\omega)(10^4 + j\omega)} = \frac{j\omega \cdot 10^6 \left(1 + j\frac{\omega}{10^6}\right)}{1000 \left(1 + j\frac{10\omega}{1000}\right) \cdot 10^4 \left(1 + j\frac{\omega}{10^4}\right)}$$
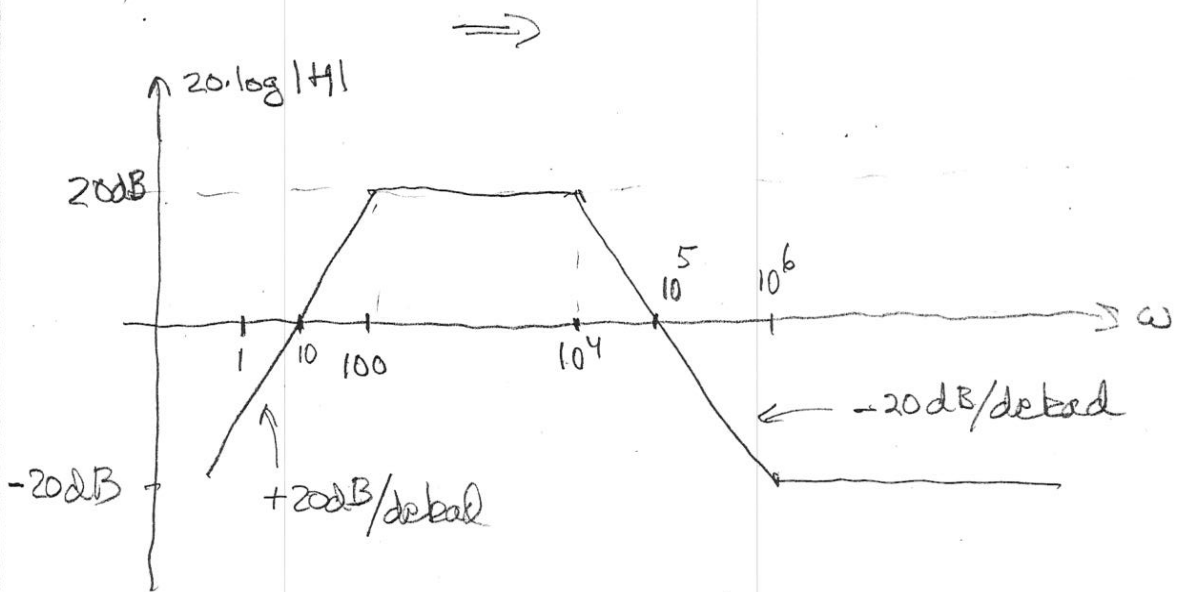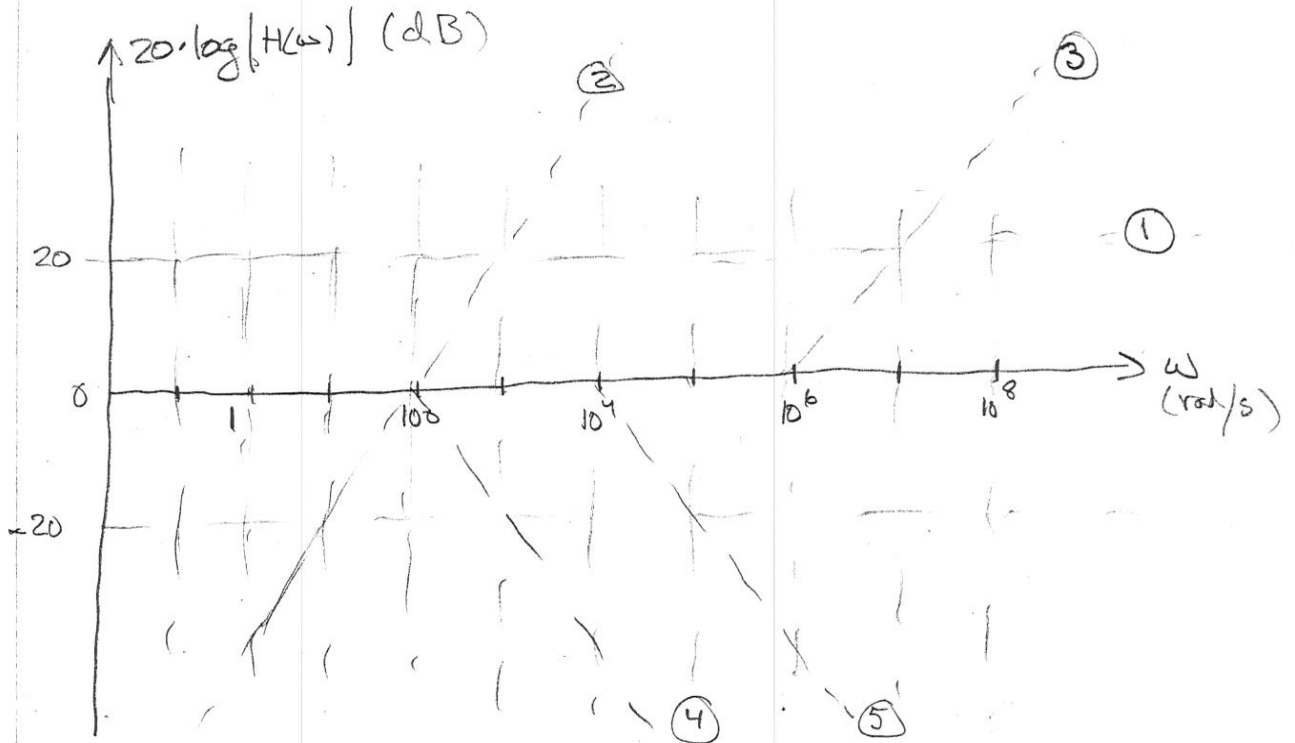
$$= \frac{1}{10} \cdot \frac{j\omega \left(1 + j\frac{\omega}{10^6}\right)}{\left(1 + j\frac{\omega}{100}\right) \left(1 + j\frac{\omega}{10^4}\right)} = 10 \cdot \frac{j\frac{\omega}{100} \left(1 + j\frac{\omega}{10^6}\right)}{\left(1 + j\frac{\omega}{100}\right) \left(1 + j\frac{\omega}{10^4}\right)}$$



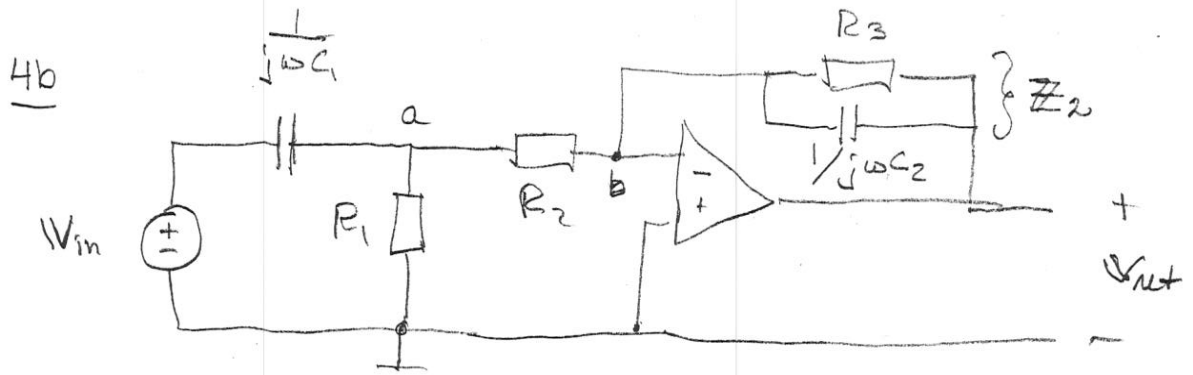

Ideal motkopplad OP \Rightarrow $i_{\text{in}} = 0$
 $V_b = 0$

Nodanalys:

a.
$$\frac{V_a - V_{in}}{1/j\omega C_1} + \frac{V_a}{R_1} + \frac{V_a - V_b}{R_2} = 0 ; V_b = 0 \Rightarrow$$

$$V_a \left(j\omega C_1 + \frac{1}{R_1} + \frac{1}{R_2} \right) = j\omega C_1 V_{in} \Rightarrow$$

$$V_a = \frac{j\omega R_1 R_2 C_1}{j\omega R_1 R_2 C_1 + R_1 + R_2} V_{in} = \frac{j\omega \frac{R_1 R_2}{R_1 + R_2} C_1}{1 + j\omega \frac{R_1 R_2}{R_1 + R_2} C_1} V_{in} \quad (1)$$

b.
$$\frac{V_b - V_a}{R_2} + \frac{V_b - V_{out}}{Z_2} = 0 ; V_b = 0 \Rightarrow$$


$$V_{out} = -\frac{Z_2}{R_2} V_a ; Z_2 = R_3 \parallel \frac{1}{j\omega C_2} = \frac{R_3 \cdot \frac{1}{j\omega C_2}}{R_3 + \frac{1}{j\omega C_2}} =$$

$$= \frac{R_3}{1 + j\omega R_3 C_2} \quad (1) \Rightarrow$$

$$V_{out} = -\frac{R_3}{R_2} \frac{1}{1 + j\omega R_3 C_2} V_a = -\frac{R_3}{R_2} \frac{j\omega \frac{R_1 R_2}{R_1 + R_2} C_1}{(1 + j\omega R_3 C_2) \left(1 + j\omega \frac{R_1 R_2}{R_1 + R_2} C_1 \right)} V_{in}$$

$$= -10 \cdot \frac{j \frac{\omega}{500}}{\left(1 + j \frac{\omega}{2 \cdot 10^5} \right) \left(1 + j \frac{\omega}{500} \right)} \Rightarrow$$
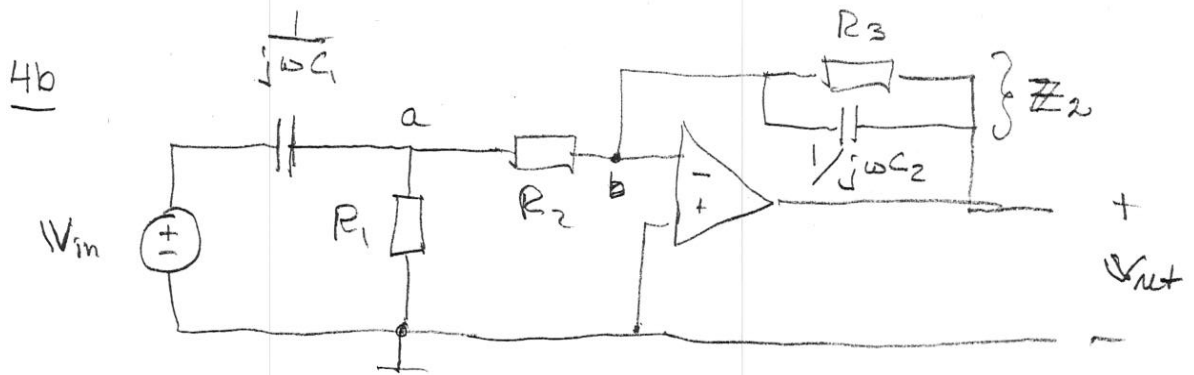
$$K = -10 \quad \omega_1 = 500 \text{ rad/s} \quad \omega_2 = 200\,000 \text{ rad/s}$$



Ideal untkoppelt OP \Rightarrow "inputsumme" = 0
 $\cdot V_b = 0$

Nodenanalyse:

a.
$$\frac{V_a - V_{in}}{1/j\omega C_1} + \frac{V_a}{R_1} + \frac{V_a - V_b}{R_2} = 0 ; V_b = 0 \Rightarrow$$

$$V_a \left(j\omega C_1 + \frac{1}{R_1} + \frac{1}{R_2} \right) = j\omega C_1 V_{in} \Rightarrow$$

$$V_a = \frac{j\omega R_1 R_2 C_1}{j\omega R_1 R_2 C_1 + R_1 + R_2} V_{in} = \frac{j\omega \frac{R_1 R_2}{R_1 + R_2} C_1}{1 + j\omega \frac{R_1 R_2}{R_1 + R_2} C_1} V_{in} \quad (1)$$

b.
$$\frac{V_b - V_a}{R_2} + \frac{V_b - V_{out}}{Z_2} = 0 ; V_b = 0 \Rightarrow$$



$$V_{out} = - \frac{Z_2}{R_2} V_a ; Z_2 = R_3 \parallel \frac{1}{j\omega C_2} = \frac{R_3 \cdot \frac{1}{j\omega C_2}}{R_3 + \frac{1}{j\omega C_2}} =$$

$$= \frac{R_3}{1 + j\omega R_3 C_2} \quad (1) \Rightarrow$$


$$V_{out} = - \frac{R_3}{R_2} \frac{1}{1 + j\omega R_3 C_2} V_a = - \frac{R_3}{R_2} \frac{j\omega \frac{R_1 R_2}{R_1 + R_2} C_1}{\left(1 + j\omega R_3 C_2\right) \left(1 + j\omega \frac{R_1 R_2}{R_1 + R_2} C_1\right)} V_{in}$$

$$= -10 \cdot \frac{j \frac{\omega}{500}}{\left(1 + j \frac{\omega}{2 \cdot 10^5}\right) \left(1 + j \frac{\omega}{500}\right)} \Rightarrow$$
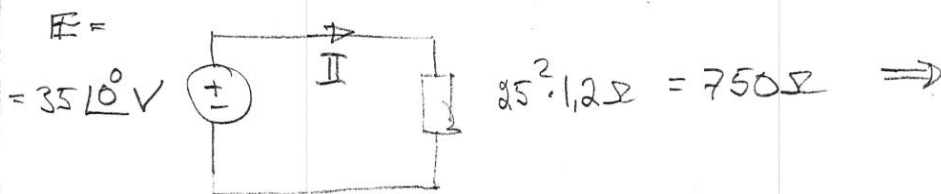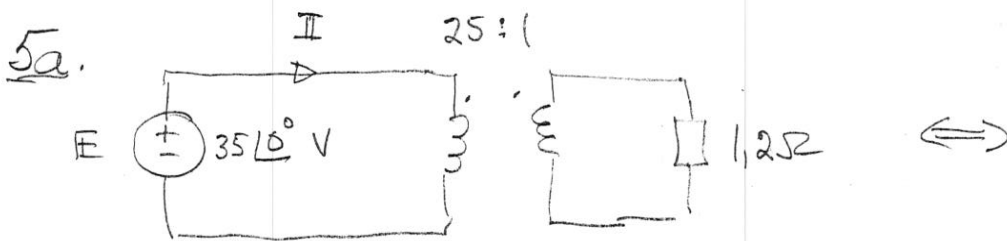
$$\underline{K = -10} \quad \underline{\omega_1 = 500 \text{ rad/s}} \quad \underline{\omega_2 = 200\,000 \text{ rad/s}}$$


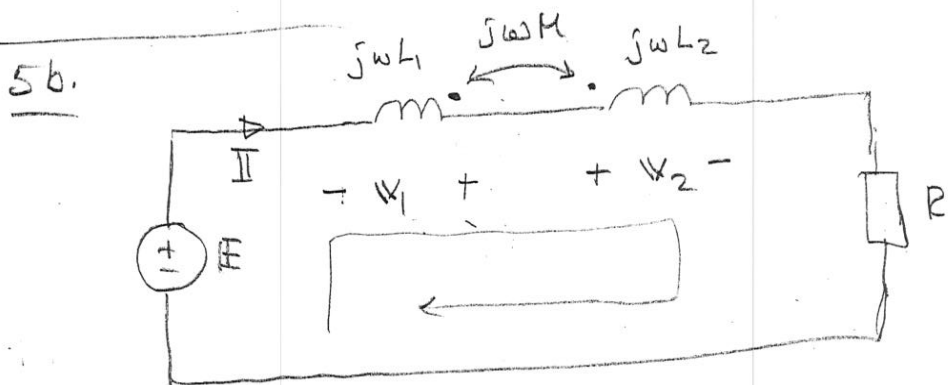
$$I = \frac{35 \angle 0^\circ}{750 \Omega} = 46,7 \angle 0^\circ \text{ mA} \Rightarrow \underline{\underline{i(t) = 46,7 \cdot \cos(1000t) \text{ mA}}}$$



Kirchhoff: $+E + V_1 - V_2 - R I = 0$

$$V_1 = -j\omega L_1 I + j\omega M I$$

$$V_2 = j\omega L_2 I - j\omega M I$$

$$E - j\omega L_1 I + j\omega M I - j\omega L_2 I + j\omega M I - R I = 0 \Rightarrow$$

$$E = (j\omega L_1 + j\omega L_2 - 2j\omega M + R) \cdot I =$$


$$= (j10 + j5 - j8 + 10) I = (10 + j7) \Omega \cdot I =$$

$$= 7,68 \angle 35,0^\circ \Omega \cdot I \Rightarrow$$

$$I = \frac{35 \angle 0^\circ \text{ V}}{7,68 \angle 35,0^\circ \Omega} = 4,56 \angle -35,0^\circ \text{ A} \Rightarrow$$

$$\underline{\underline{i(t) = 4,56 \cdot \cos(1000t - 35,0^\circ) \text{ A}}}$$

6.

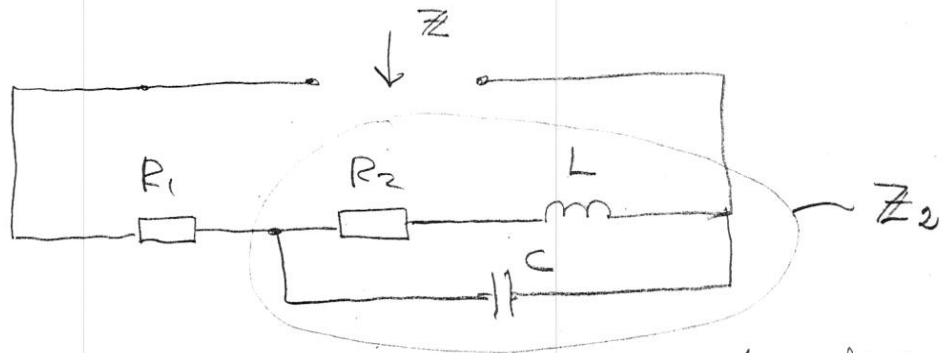

Resonans: Resonans om Z är reell, dvs om Z_2 är reell.

$$Z_2 = \frac{1}{j\omega C} \parallel (R_2 + j\omega L) = \frac{\frac{1}{j\omega C} (R_2 + j\omega L)}{\frac{1}{j\omega C} + R_2 + j\omega L} =$$
$$= \frac{R_2 + j\omega L}{1 + j\omega R_2 C - \omega^2 LC} = \frac{R_2 + j\omega L}{1 - \omega^2 LC + j\omega R_2 C} \Rightarrow$$

Z_2 reell om

$$\frac{R_2}{1 - \omega^2 LC} = \frac{\cancel{\omega L}}{\cancel{\omega R_2 C}} \Rightarrow 1 - \omega^2 LC = \frac{R_2^2 C}{L} \Rightarrow$$

$$\omega = \frac{1}{\sqrt{LC}} \cdot \sqrt{1 - \frac{R_2^2 C}{L}} = \underline{\underline{122,5 \text{ krads}}}$$

Resonans saknas om

$$1 - \frac{R_2^2 C}{L} < 0 \Leftrightarrow C > \frac{L}{R_2^2} = \underline{\underline{25 \text{ nF}}}$$

Z vid resonans

$$Z_{\text{res}} = R_1 + Z_{2\text{res}} = R_1 + \frac{L}{R_2} = \underline{\underline{1800 \Omega}}$$