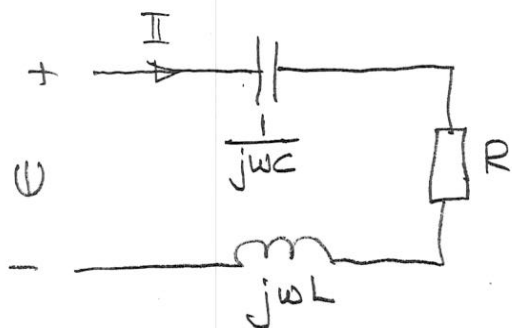


Lösungen Kretsanalyse aug 2013

1.



$$i(t) = 100 \cos(2000t - 10^\circ) \text{ mA}$$

$$\Rightarrow \underline{I} = 0,1 \angle -10^\circ \text{ A}$$

$$R = 330 \Omega$$

$$L = 150 \text{ mH}, C = 820 \text{ nF}$$

$$\bullet U = \underline{Z} \cdot \underline{I}, \quad \underline{Z} = R + j\omega L + \frac{1}{j\omega C} = (\omega = 2000 \text{ rad/s}) =$$


$$= 330 + j300 - j609,8 = 330 - j309,8 = 452,6 \angle -43,2^\circ \Omega$$

$$\Rightarrow U = 452,6 \angle -43,2^\circ \Omega \cdot 0,1 \angle -10^\circ \text{ A} = 45,3 \angle -53,2^\circ \text{ V} \Rightarrow$$


$$\underline{u(t)} = 45,3 \cos(2000t - 53,2^\circ) \text{ V}$$

$$\bullet P = R \cdot I_{\text{rms}}^2 = 330 \Omega \cdot \left(\frac{0,1 \text{ A}}{\sqrt{2}} \right)^2 = \underline{\underline{1,65 \text{ W}}}$$


2a.

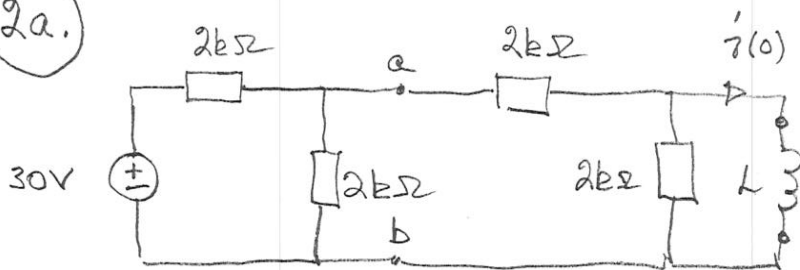

↔ (Tvåpols-
omvand-
ling)

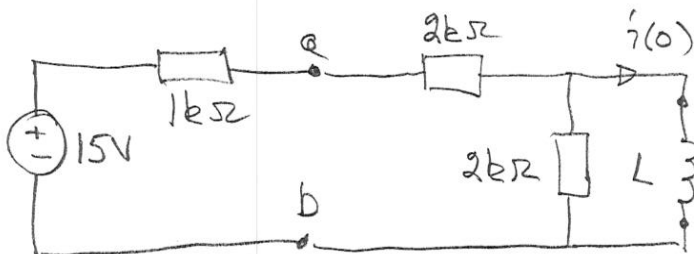


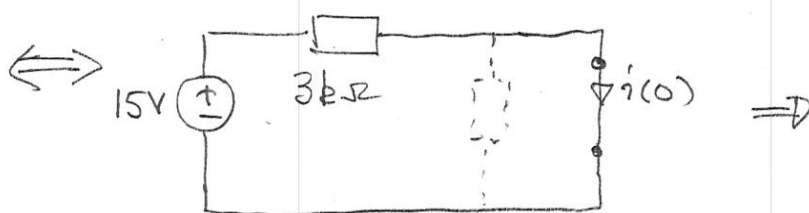Stationärtill-
stånd DC ⇒
Spole = kortslutn.




$$i(0) = \frac{15V}{3k\Omega} = \underline{\underline{5mA}}$$

2b

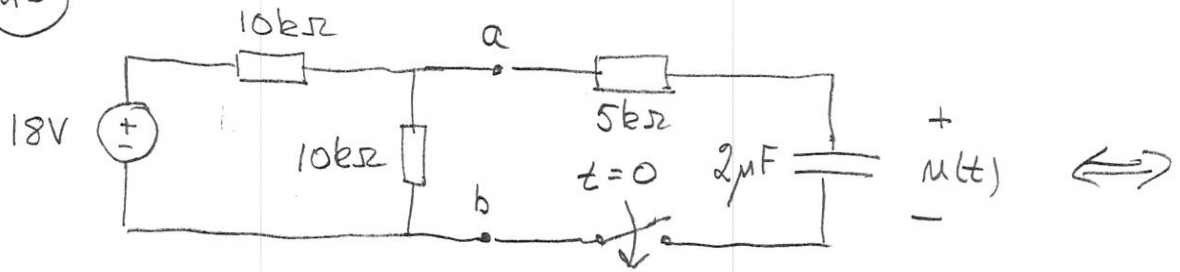

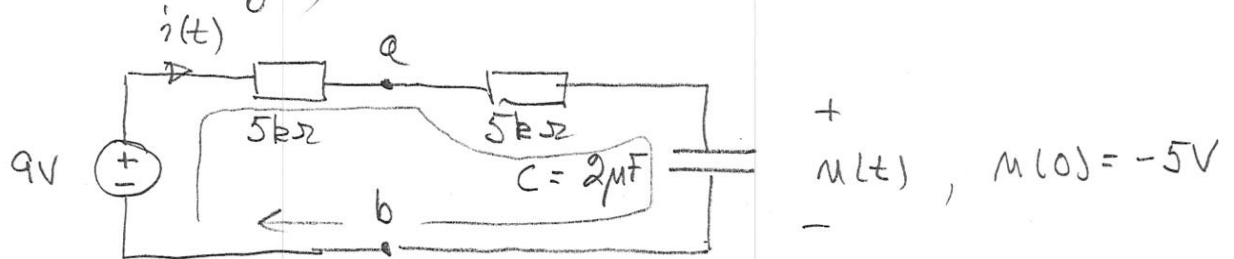(Tvåpolsom-
vandling) r Schema för $t > 0$.



• KVL ger $+9V - 5k\Omega \cdot i(t) - 5k\Omega \cdot i(t) - u(t) = 0$

• $i(t) = 2\mu F \cdot \frac{du}{dt} \Rightarrow$ (utau enheter)

$$9 - 10 \cdot 10^3 \cdot 2 \cdot 10^{-6} \frac{du}{dt} - u(t) = 0 \Rightarrow \frac{du}{dt} + 50u(t) = 450$$

$$u(t) = u_h(t) + u_p(t)$$

$$\underline{u_h(t)} \quad \frac{du}{dt} + 50u(t) = 0 \Rightarrow u_h(t) = A \cdot e^{-50t}$$

$$\underline{u_p(t)} \quad \text{Ansätt } u_p(t) = B \Rightarrow$$




$$0 + 50B = 450 \Rightarrow B = 9, \text{ så att}$$

$$u(t) = 9 + A \cdot e^{-50t}, \quad u(0) = -5V \Rightarrow$$

$$-5 = 9 + A \cdot e^0 \Rightarrow A = -14 \Rightarrow$$

$$\underline{\underline{u(t) = 9 - 14e^{-50t} \text{ V}}}$$


3a

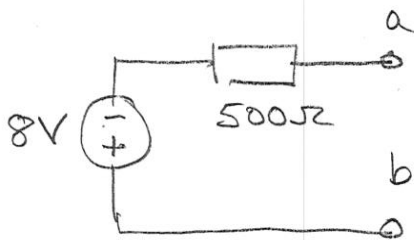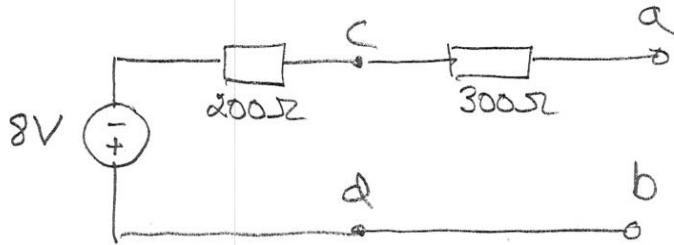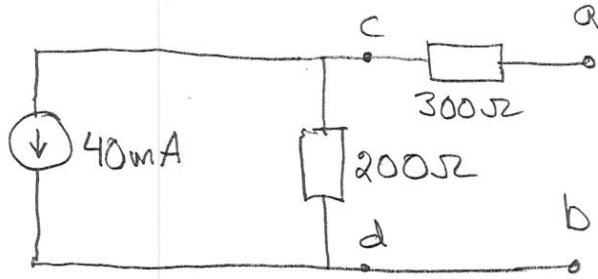

Maximal effekt i en resistor på 500Ω ansluten mellan a och b:

$$P_{\max} = \frac{\left(\frac{8V}{2}\right)^2}{500\Omega} = \underline{\underline{32\text{mW}}}$$

3b.

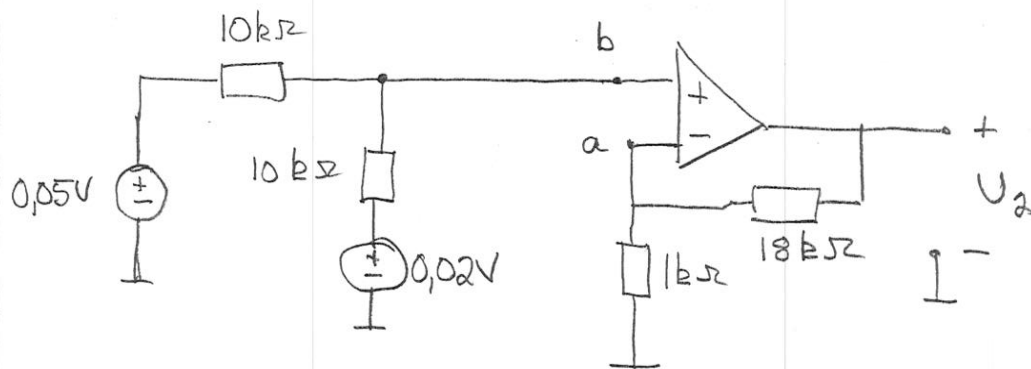

Ideal motkopplad OP \Rightarrow

- instömmar = 0
- $V_a = V_b$

Nodanalys

a.
$$\frac{V_a}{1k\Omega} + \frac{V_a - U_2}{18k\Omega} = 0 \Rightarrow V_a \left(\frac{1}{1k\Omega} + \frac{1}{18k\Omega} \right) = \frac{U_2}{18k\Omega}$$


$$\Rightarrow U_2 = (18+1) \cdot V_a = 19V_a$$

b.
$$\frac{V_b - 0,05V}{10k\Omega} + \frac{V_b - 0,02V}{10k\Omega} = 0 \Rightarrow$$

$$2V_b = 0,05V + 0,02V \Rightarrow V_b = 0,035V$$

$$V_a = V_b \Rightarrow U_2 = 19 \cdot 0,035V = \underline{\underline{0,665V}}$$

4.

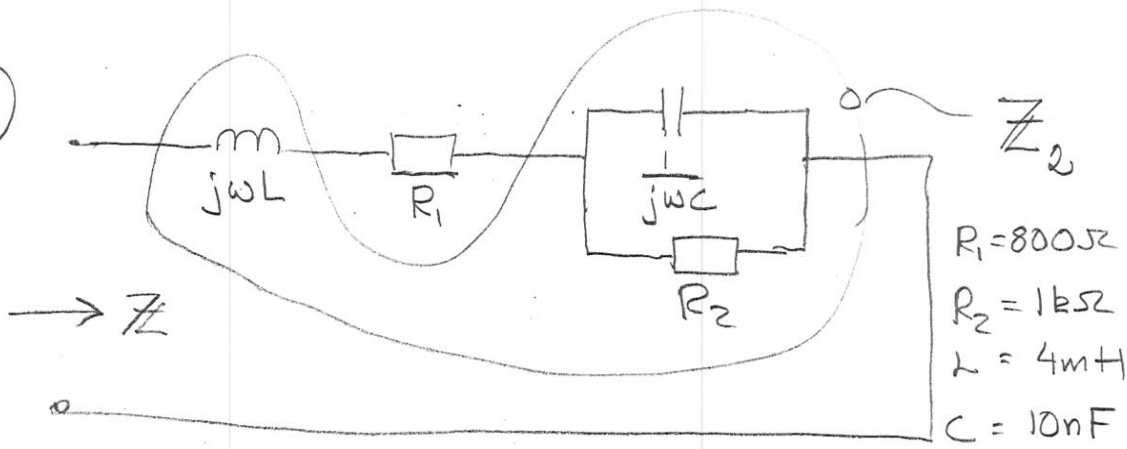

$$\begin{aligned} \bullet Z &= R_1 + Z_2 ; Z_2 = j\omega L + R_2 \parallel \frac{1}{j\omega C} = \\ &= j\omega L + \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = j\omega L + \frac{R_2}{1 + j\omega R_2 C} = \\ &= \frac{j\omega L - \omega^2 R_2 L C + R_2}{1 + j\omega R_2 C} = \frac{R_2 - \omega^2 R_2 L C + j\omega L}{1 + j\omega R_2 C} \end{aligned}$$

a. Resonans $\Leftrightarrow Z$ reell $\Leftrightarrow Z_2$ reell

$$\Rightarrow \frac{R_2 - \omega^2 R_2 L C}{1} = \frac{\omega L}{\omega R_2 C} \Rightarrow$$

$$R_2(1 - \omega^2 L C) = \frac{L}{R_2 C} \Rightarrow \omega^2 L C = 1 - \frac{L}{R_2^2 C} \Rightarrow$$

$$\omega = \frac{1}{\sqrt{LC}} \cdot \sqrt{1 - \frac{L}{R_2^2 C}} = \frac{1}{\sqrt{4 \cdot 10^{-3} \cdot 10 \cdot 10^{-9}}} \cdot \sqrt{1 - \frac{4 \cdot 10^{-3}}{1000^2 \cdot 10 \cdot 10^{-9}}} =$$


$$= 158,1 \cdot 10^3 \cdot \sqrt{1 - 0,4} \text{ rad/s} = \underline{\underline{122 \text{ krad/s}}}$$

b. $Z_{\text{resonans}} = R_1 + Z_{2\text{resonans}} =$
 $= R_1 + \frac{L}{R_2 C} = 800\Omega + 400\Omega = \underline{\underline{1,2\text{k}\Omega}}$

c. Resonans saknas om

$$1 - \frac{L}{R_2^2 C} < 0 \iff \frac{L}{R_2^2 C} > 1 \iff$$
$$C < \frac{L}{R_2^2} = \frac{4 \cdot 10^{-3}}{1000^2} = \underline{\underline{4\text{nF}}}$$

5. Komplexwertberechnungsschema

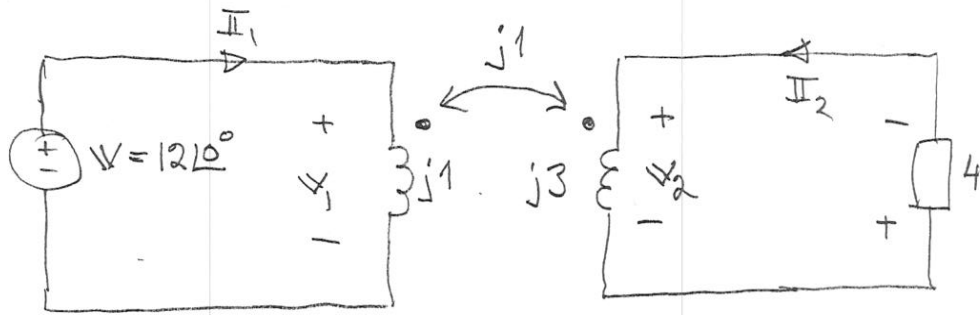

$$\left. \begin{array}{l} \bullet V_1 = V = 12\angle 0^\circ \\ \bullet V_1 = j1 \cdot I_1 + j1 \cdot I_2 \end{array} \right\} j(I_1 + I_2) = 12\angle 0^\circ \Rightarrow$$

$$I_1 + I_2 = -j \cdot 12\angle 0^\circ = -j12 \quad (1)$$

$$\left. \begin{array}{l} \bullet V_2 = -4 \cdot I_2 \\ \bullet V_2 = j3 I_2 + j1 I_1 \end{array} \right\} \Rightarrow -4I_2 = j3 I_2 + j I_1 \Rightarrow$$

$$j I_1 + (4 + j3) I_2 = 0 \quad (2), \quad (1) \text{ oder } (2) \Rightarrow$$

$$j I_1 + (4 + j3) \cdot (-j12 - I_1) = 0 \Rightarrow$$


$$j I_1 - j48 + 36 - 4 I_1 - j3 I_1 = 0 \Rightarrow$$

$$(-4 - j2) I_1 = -36 + j48 \Leftrightarrow (4 + j2) I_1 = 36 - j48 \Rightarrow$$

$$I_1 = \frac{36 - j48}{4 + j2} = \frac{60 \angle -53,1^\circ}{4,47 \angle 26,6^\circ} = 13,4 \angle -79,7^\circ \Rightarrow$$

$$i_1(t) = 13,4 \cos(1000t - 79,7^\circ) \text{ A}$$

6.

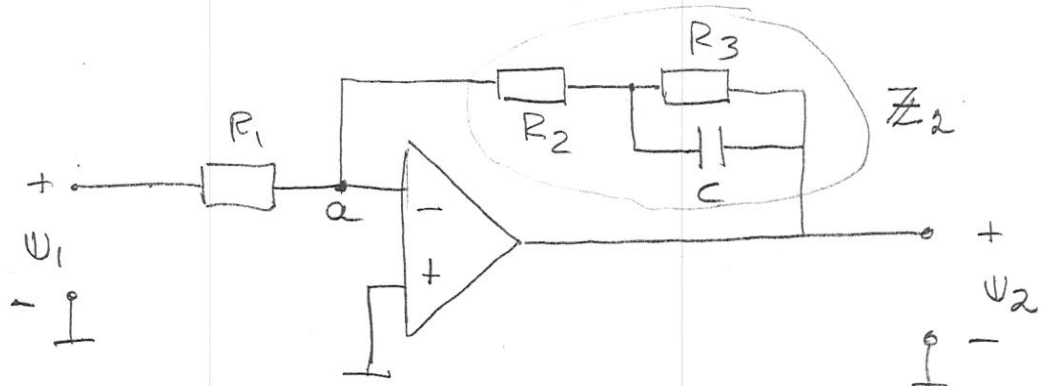

$$R_1 = 2,2 \text{ k}\Omega, \quad R_2 = 18 \text{ k}\Omega, \quad R_3 = 390 \text{ k}\Omega, \quad C = 4,7 \text{ nF}$$

Ideal motkopplad OP \Rightarrow \cdot instömmar = 0
 \cdot $V_a = 0$

$$\cdot Z_2 = R_2 + R_3 \parallel \frac{1}{j\omega C} = R_2 + \frac{R_3 \cdot \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} =$$

$$= R_2 + \frac{R_3}{1 + j\omega R_3 C} = \frac{R_2 + R_3 + j\omega R_2 R_3 C}{1 + j\omega R_3 C} =$$

$$= (R_2 + R_3) \cdot \frac{1 + j\omega \frac{R_2 R_3}{R_2 + R_3} C}{1 + j\omega R_3 C}$$

Nodanalys i a:

$$\frac{V_a - U_1}{R_1} + \frac{V_a - U_2}{Z_2} = 0; \quad V_a = 0 \Rightarrow$$

$$U_2 = - \frac{Z_2}{R_1} \cdot U_1 \Rightarrow \frac{U_2}{U_1} = - \frac{Z_2}{R_1} =$$

$$= - \frac{R_2 + R_3}{R_1} \cdot \frac{1 + j\omega \frac{R_2 R_3}{R_2 + R_3} C}{1 + j\omega R_3 C} = - 185,9 \cdot \frac{1 + j \frac{\omega}{12,4 \cdot 10^3}}{1 + j \frac{\omega}{546}}$$

$$\Rightarrow \underline{\omega_1 = 546 \text{ rad/s}}; \quad \underline{\omega_2 = 12,4 \text{ krad/s}}$$

$$\underline{\omega \ll 546} \Rightarrow$$

$$\frac{U_2}{U_1} \approx -185,9 \cdot \frac{1+j0}{1+j0} = -185,9 \Rightarrow$$

$$A = 20 \cdot \log |-185,9| = \underline{\underline{45,4 \text{ dB}}}$$

$$\omega \gg 12,4 \text{ krad/s} \Rightarrow$$

$$\frac{U_2}{U_1} \approx -185,9 \cdot \frac{\frac{\omega}{12,4 \cdot 10^3}}{\frac{\omega}{546}} = -8,19 \Rightarrow$$

$$B = 20 \cdot \log |-8,19| = \underline{\underline{18,3 \text{ dB}}}$$
