

CHALMERS August 2017	Anonymous code Melbn	Points for question (to be filled in by teacher)	Consecutive page no. Löpande sid nr 1
	Anonym kod ENM060/61	Poäng på uppgiften (fylls av lärare)	Question no. Uppgift nr 1 a) b)

(a) diode - uncontrolled device, conducts when forward biased
 thyristor - semiconrolled, conducts when forward biased and a gate signal is applied; it turns off when reverse voltage is applied.

4

GTO - a thyristor that can be turned off by applying a negative pulse current; fully controlled

MOSFET - a fully controlled device by applying a positive or negative gate-source voltage.

(b) air gap increases the maximum saturating current and hence the operating range of dc/dc converters.

Example show: $L = \frac{N^2}{R_c + R_g}$ (inductance) 2

$I_{sat} = \frac{B_{sat} A_c}{N} (R_c + R_g)$
 ↑ air gap reluctance

energy $\rightarrow W = \frac{1}{2} L I_{sat}^2 = \frac{1}{2} B_{sat}^2 A_c^2 (R_c + R_g)$
 increase in operation range!

Aug. 2017

ENM060/061


$$V_o = 16V$$

$$P_o = 64W$$

$$V_d = 12V$$

$$f_{sw} = 20 kHz$$

(a) CCM Ideal

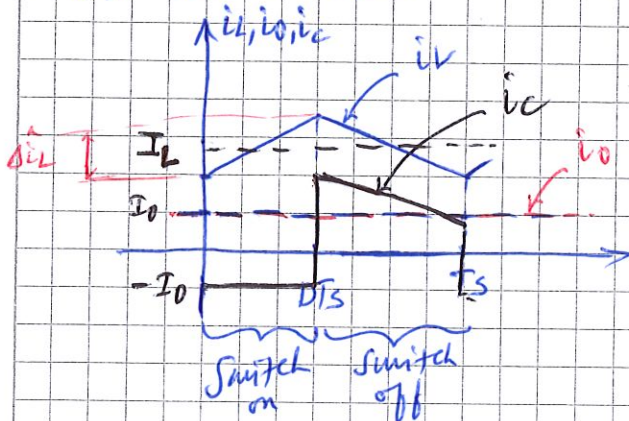


(2)

$$\Rightarrow V_d = \int_0^{T_s} v_L dt = 0$$

$$\Rightarrow D V_d - (1-D) V_o = 0$$
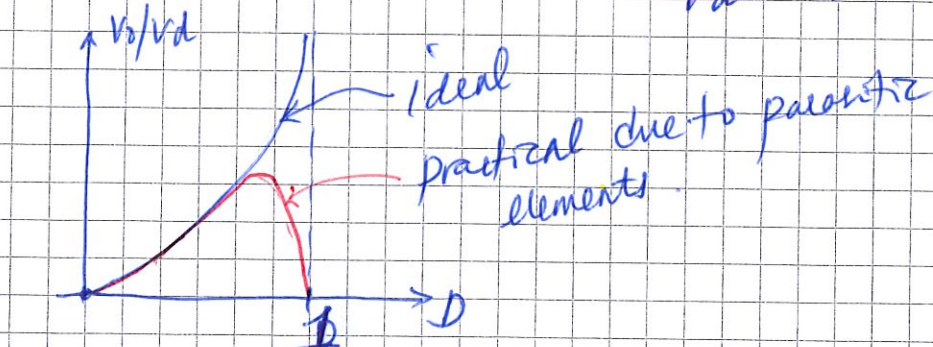
$$\Rightarrow \frac{V_o}{V_d} = \frac{D}{1-D} \quad (\text{Buck-boost Converter})$$



$$(b) \quad I_o = P_o / V_o = \frac{64}{16} A = 4A, \quad \Delta i_L = 0.1 I_L = \underline{0.4A}$$

$$I_L = P_o / V_d + I_o = I_d + I_o = \frac{64}{12} + 4 = \underline{\underline{9.33A}}$$

Aug. 2017

ENM066/061

$$\text{During on period: } v_L = L \frac{di_L}{dt} = \frac{L \Delta i_L}{DT_s} = V_d$$


$$\Rightarrow L = \frac{DT_s V_d}{\Delta i_L} = \frac{D V_d}{f_w \Delta i_L} \quad (2)$$

$$\text{but } \left(\frac{\Delta i_L}{2} \right) < I_L \Rightarrow \text{CCM:}$$

$$\Rightarrow \frac{D}{1-D} = \frac{V_o}{V_d} \Rightarrow \frac{1-D}{D} = \frac{V_d}{V_o} = \frac{1}{D} - 1$$

$$\Rightarrow \frac{1}{D} = 1 + \frac{V_d}{V_o} = \frac{V_o + V_d}{V_o} \Rightarrow D = \frac{V_o}{V_o + V_d} = \underline{\underline{0.571}}$$
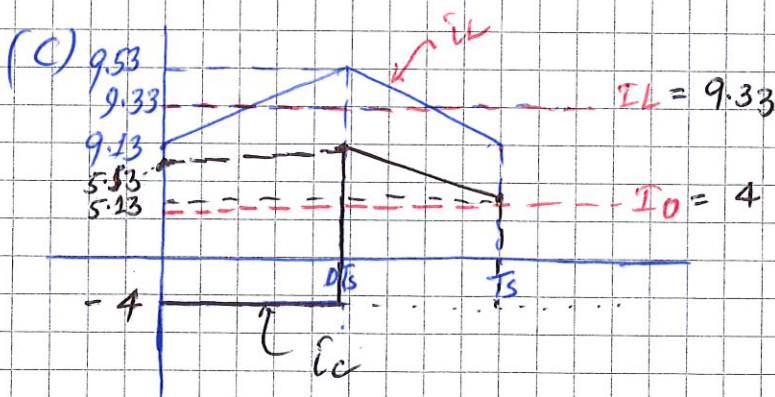
$$\Rightarrow L = \frac{(0.571)(12)}{20(10^3)(0.4)} \text{ H} = \underline{\underline{0.857 \text{ mH}}}$$



(d) $\Delta V_o = 0.01 V_o = 0.16 \text{ V}$

Consider the switch on period

$$\Rightarrow \Delta V_o = \frac{1}{C} \int_0^{DT_s} i_c dt = \frac{1}{C} (I_o \cdot DT_s) \quad (2)$$

$$\Rightarrow C = \frac{I_o D}{f_w \Delta V_o} \Rightarrow C_{\min} = \frac{D I_o}{f_w [\Delta V_o]_{\max}} = \frac{0.571(4)}{20(10^3)(0.16)} \text{ F}$$

$$\Rightarrow C_{\min} = \underline{\underline{0.714 \text{ mF}}}$$

CHALMERS Aug. 2017	Anonymous code Melbtr	Points for question (to be filled in by teacher)	Consecutive page no. Löpande sid nr 4
	Anonym kod ENM060/061	Poäng på uppgiften (fylls av lärare)	Question no. Uppgift nr 3

$$N_1 : N_2 : N_3 = 1 : 2 : 1$$

$$V_d = 20V$$

$$f_{sw} = 20 \text{ kHz}$$

$$D = 0.3$$

$$L_m = 100 \mu\text{H}$$

$$R_{load} = 10 \Omega$$

V_o, V_{sw}, i_d, i_o

Identify mode of operation.

if CCM ; $V_o = \frac{D}{1-D} V_d = \frac{0.3}{0.7} (20) = 8.57 < \frac{N_3 V_d}{N_2} = 10V$

$\Rightarrow I_m \approx \frac{\hat{\Delta i_m}}{2} \Rightarrow$ During on period
 $V_d = V_L = L_m \frac{\Delta i_m}{\Delta t}$

winding N_2 not used.

$$\Rightarrow \hat{\Delta i_m} = \frac{D V_d}{f_{sw} L_m} = \frac{0.3(20)}{20(10^3)(100 \cdot 10^{-6})} = 3A$$

but $I_m = I_d + I_o \frac{N_3}{N_1} = I_d + I_o \Rightarrow I_m = \frac{I_o}{1-D}$

But $I_o = \frac{V_o}{R_{load}} = \frac{8.57}{10} = 0.857A \Rightarrow I_m = 1.224A$

But $I_m = 1.224 < \frac{\hat{\Delta i_m}}{2} = 1.5A \Rightarrow$ Converter in CCM!

For DCM: $\frac{V_o}{V_d} = D \sqrt{\frac{R}{2L_m f_{sw}}}$ [should be derived first]

$\Rightarrow V_o = 0.3 \sqrt{\frac{10}{2(100 \cdot 10^{-6})(20 \cdot 10^3)}} \cdot 20V = 9.487V < 10V$

(winding N_2 not used!!!)

Aug. 2017

So for DCM,

$$\hat{\Delta i_m} = 3A$$

For the off period,

$$V_1 = \frac{N_1}{N_3} V_0 = L_m \left(-\frac{\hat{\Delta i_m}}{\Delta t_s} \right)$$

$$\Rightarrow V_0 = L_m \frac{\hat{\Delta i_m}}{\Delta t_s} \Rightarrow \Delta_1 = \frac{L_m \hat{\Delta i_m}}{V_0 T_s}$$

$$\Rightarrow \Delta_1 = \left(\frac{L_m \hat{\Delta i_m}}{D T_s} \right) \frac{D}{V_0}$$


↑ V_d

$$\Rightarrow \Delta_1 = \frac{V_d \cdot D}{V_0} = \frac{20 \times 0.3}{9.487} = \underline{\underline{0.632}}$$

During the off period, $i_D = \frac{N_1}{N_3} i_m \Rightarrow i_m$; $i_d = 0$, $V_{sw} = V_d + \frac{N_1}{N_3} V_0$


During on period, $i_D = 0$, $i_d = i_m$, $V_{sw} = 0$

For current on period (total demagnetization), $V_{sw} = V_d$, $i_d = i_m = i_m$

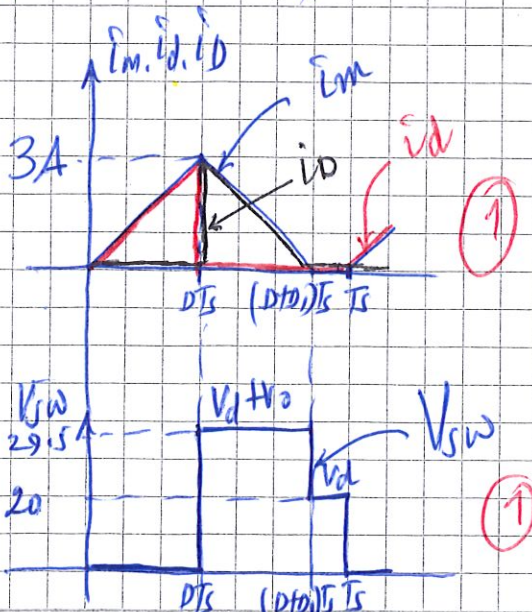

Aug. 2017

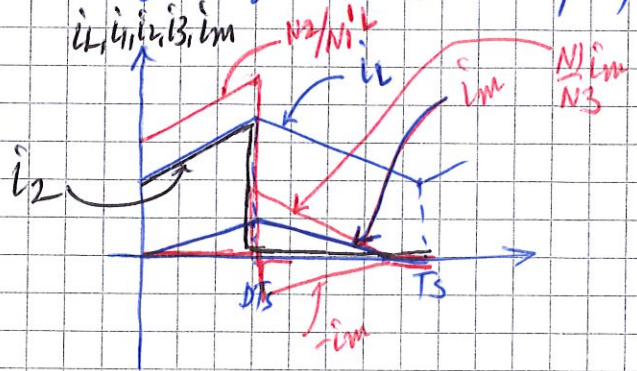(a) For a proper operation of the forward Converter, the magnetic core of the transformer should be totally demagnetized by the start of each switching cycle.




3

When switch on, i_m, i_L increases
 $i_2 = i_L$; $i_1 = \frac{N_2}{N_1} i_L = \frac{N_2}{N_1} i_L$, $i_3 = 0$

When switch off, i_m, i_L decreases
 $i_2 = 0$, $i_1 = -i_m$, $i_3 = \frac{N_1}{N_3} i_1 = \frac{N_1}{N_3} (-i_m)$
 $\Rightarrow i_3 = 0$

after total demagnetization
 $i_1 = i_3 = i_m = 0$

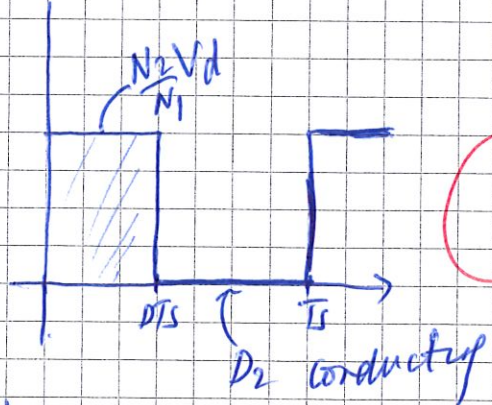(b) $V_o = V_{oi} = \frac{1}{T_s} \int_0^{T_s} V_{oidt}$



2

$\Rightarrow V_o = \frac{1}{T_s} (DT_s \cdot \frac{N_2 V_d}{N_1}) \Rightarrow \frac{V_o}{V_d} = \frac{N_2 D}{N_1}$

(c) For ^{magnete} core demagnetization of the transformer, this ^{also} prevents overvoltage on the switch due to leakage inductances.

1


Aug. 2017

Mebtm
ENMO60/061

7
4 d) e)

d) (ϕ) flux \sim magnetizing current (i_m); flux density (B)

$\rightarrow B \sim i_m$

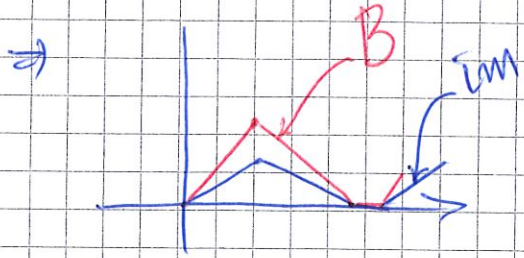

2

- ✓ unipolar excitation core
- ✓ high saturation flux
- ✓ high mutual inductance to require small magnetizing current
 \Rightarrow no air-gap in the core

(e) For flyback

- ✓ unipolar excitation
- ✓ higher saturation flux airforcem 2
- ✓ low mutual inductance hence higher magnetizing current for higher operating range!
 \Rightarrow air-gap in the core!

Aug. 20.17

ENMO60/061

5 a)

(a) The phase voltages are calculated from the neutral voltage and connected ^{phase} leg output voltage



$$V_{A,B,C} = \underbrace{V_{CA,B,C}}_{\text{Converter phase voltage}} - V_N$$

For a balanced system

$$V_A + V_B + V_C = V_{CA} + V_{CB} + V_{CC} - 3V_N = 0$$

$$\Rightarrow V_N = \frac{V_{CA} + V_{CB} + V_{CC}}{3}$$

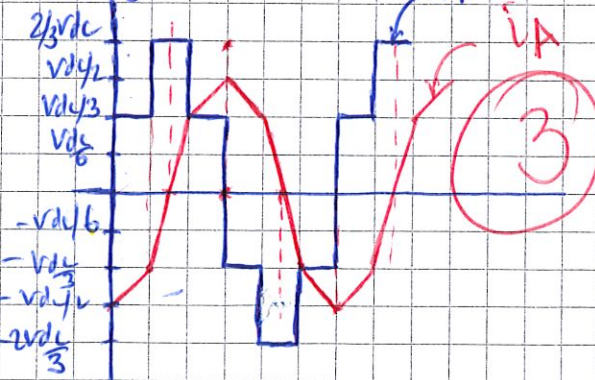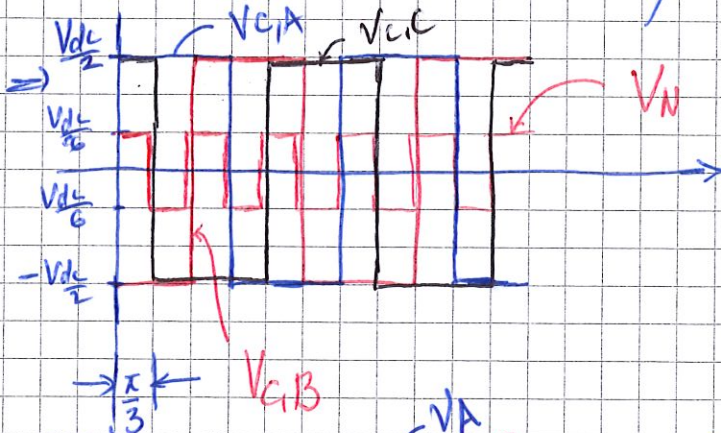V_{CA} , V_{CB} and V_{CC} are 120° phase-shifted square waves.



plot V_A & i_A , the other voltage & currents are 120° phase shifted!!

$$L \frac{di_A}{dt} = V_A$$

$$\Rightarrow i_A = \frac{1}{L} \int V_A dt$$

$\Rightarrow i_A$ is linearly increasing or decreasing based on the sign of V_A .

* i_A is maximum at the zero crossing of V_A .

Aug. 2017

5b) c)

(b) inductive load \Rightarrow power = zero

$\Rightarrow V_d \cdot I_d = 0 \Rightarrow I_d = 0$ (1)
the average dc-current is zero.

* Due to the square-wave 4 three phase equation the harmonic components in the dc-current are multiples of the 6th order harmonics.

$\Rightarrow 6n, n = \pm 1, \pm 2, \dots$ (1)

* For a PWM operation, the harmonic orders will be around the switching frequency (1)


(c) PWM, $\hat{V}_{A(1)} = m_a \cdot \frac{V_{dc}}{2} = \frac{V_{dc}}{2}$ (peak value) (1)

square-wave, $\hat{V}_{A(1)} = \frac{4}{\pi} \cdot \frac{V_{dc}}{2}$ [Fourier calculation] (2)

Aug. 2017

$I_d = 10A$,
 $L_s = 2mH$
 $f = 50Hz$

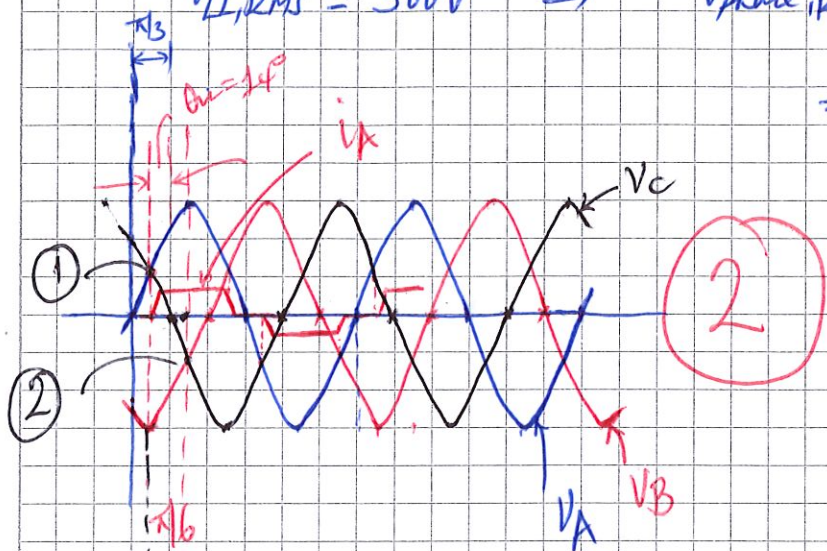$V_{LL,RMS} = 300V \Rightarrow V_{phase, peak} = \frac{300 \times \sqrt{2}}{\sqrt{3}} = 245V$




$\Rightarrow V_A = 245 \sin(2\pi \cdot 50t)$
 $V_B = 245 \sin(2\pi \cdot 50t - 2\pi/3)$
 $V_C = 245 \sin(2\pi \cdot 50t + 2\pi/3)$

Current flows in each phase when voltage is maximum or minimum & continuous to flow during commutation.

Commutation period = ?

at ① current should commute from phase C (D5) to phase A (D1)
 at ② current should commute from phase B (D6) to phase C (D2)

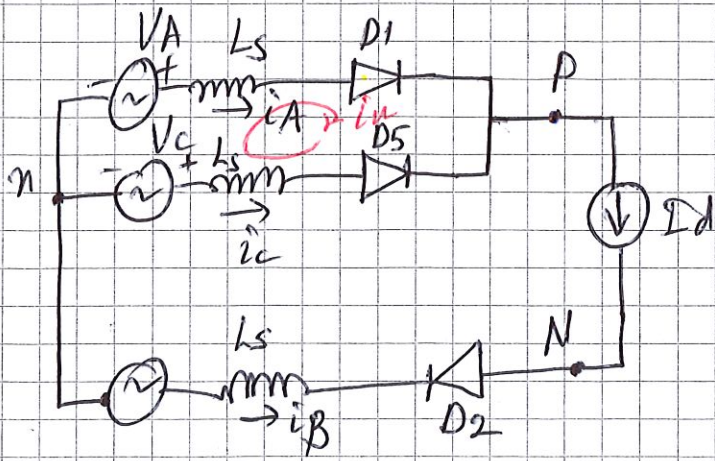\Rightarrow During commutation at ① i_A grows from 0 to I_d , where the commutation circuit is given by



i_A grows from 0 to I_d .

$i_A = i_u$
 $i_C = I_d - i_u$

$\Rightarrow V_A - V_C - L_s \frac{di_A}{dt} + L_s \frac{di_C}{dt} = 0$

$\Rightarrow 2L_s \frac{di_u}{dt} = V_A - V_C$

$\Rightarrow 2L_s \omega_s \frac{di_u}{d\theta} = \frac{V_A - V_C}{\sqrt{3} \omega_s}$

$\Rightarrow 2L_s \omega_s I_d = \int_{\pi/6}^{\pi/2} (V_A - V_C) dt$

Aug 2014

ENM060/061


θ_u

$$\Rightarrow 2L_s\omega_s I_d = \int_0^{\theta_u} \sqrt{2}V_{LL} \sin(\theta) d\theta = \sqrt{2}V_{LL} (1 - \cos\theta_u)$$

$$\Rightarrow \cos\theta_u = 0.9704 \Rightarrow \theta_u = 0.2439 \text{ rad} \approx \underline{\underline{14^\circ}}$$

Look the plot in the previous page for i_a (1)
 the DPF $\approx \cos\left(\frac{\theta_u}{2}\right) = \cos(7^\circ) \approx \underline{\underline{0.9926}}$

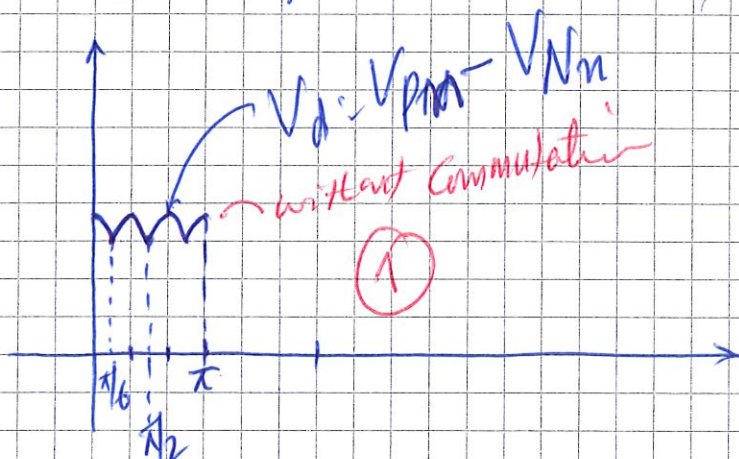(b) Check plots of V_d in the previous page for reference



For one cycle from $\pi/6$ to $\pi/2$ without commutation

$$V_{d0} = \frac{1}{\pi/3} \int_{-\pi/6}^{\pi/6} \sqrt{2}V_{LL} \cos\theta d\theta = \frac{3\sqrt{2}}{\pi} V_{LL} = \underline{\underline{405 \text{ V}}}$$

for each cycle, there is one commutation, that reduces the average voltage by $\Delta V_d = \frac{\text{Area}^{\text{loss}} \text{ due to commutation}}{\pi/3}$

for point (1), $V_{pN}(\text{idest}) = V_A$


$$V_{pN}(\text{comm}) = V_A - L_s \frac{di_a}{dt} = V_A - L_s \frac{di_u}{dt} = \frac{V_A + V_c}{2}$$

$$\Rightarrow \Delta V_d = \int_0^{\theta_u} \left(V_A - \frac{V_A + V_c}{2} \right) d\theta = \int_0^{\theta_u} \frac{V_A - V_c}{2} d\theta = L_s \omega_s I_d \quad (1)$$

$$\Rightarrow V_d = V_{d0} - \frac{3L_s \omega_s I_d}{\pi} = \underline{\underline{399 \text{ V}}}$$

$L_s = 5 \text{ mH}$
 $V_s = 300 \text{ V (peak)}$
 $\Rightarrow V_k = 300 \sin(2\pi \cdot 50 t)$
 $I_d = 20 \text{ A}$
 $\alpha = 30^\circ$

(a)

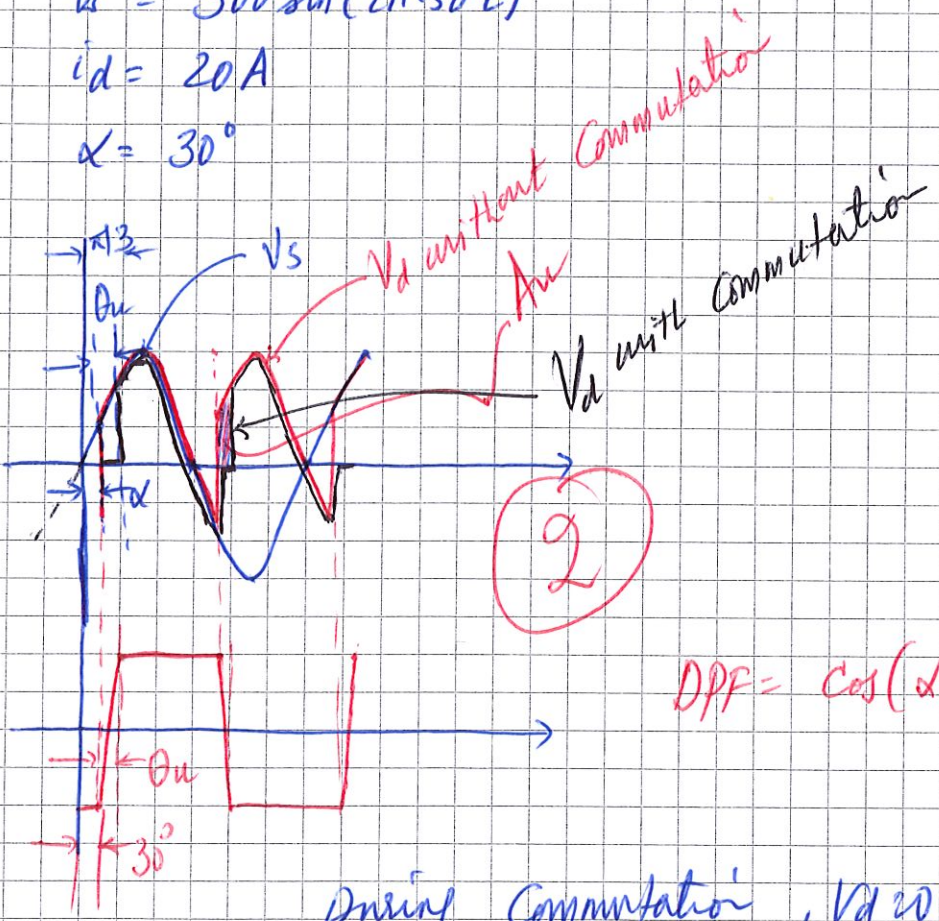

$\text{DPF} = \cos(\alpha + \theta/2)$

During commutation, $v_d = 0$, all thyristors conduct.

$\Rightarrow L_s \frac{di_d}{dt} = V_s \Rightarrow L_s \omega_s \frac{di_d}{d\theta} = V_s$
 $\Rightarrow \int_{-I_d}^{I_d} L_s \omega_s di_d = \int_{\alpha}^{\alpha+\theta} V_s d\theta$
 $\Rightarrow 2L_s \omega_s I_d = -300 \cos \theta \Big|_{\alpha}^{\alpha+\theta} = 300(\cos(\alpha) - \cos(\alpha+\theta))$
 $\Rightarrow \cos(\alpha + \theta) = -\frac{2L_s \omega_s I_d}{300} + \cos \alpha$
 $\Rightarrow \cos(\alpha + \theta) = 0.6566 \Rightarrow \theta = 0.33 \text{ rad} = 19^\circ$

$$(b) \quad V_d = V_{d0} - \frac{A_u}{\pi}$$

$$A_u = \int_{\alpha}^{\pi + \alpha} v_s d\theta = 2L_s \omega_s I_d$$

$$V_{d0} = \frac{1}{\pi} \int_{\alpha}^{\pi + \alpha} v_s d\theta = \left. -\frac{300 \cos \theta}{\pi} \right|_{\alpha}^{\pi + \alpha} \quad \text{(2)}$$

$$= 300 \{ \cos \alpha - \cos(\pi + \alpha) \}$$

$$= \frac{600 \cos \alpha}{\pi} = \underline{\underline{165.4V}}$$

$$\Rightarrow V_d = V_{d0} - \frac{2L_s \omega_s I_d}{\pi} = \underline{\underline{145.4V}}$$