

(a)

MOSFETIGBT

Conduction:

high  $R_{on}$  (high loss)low  $R_{on}$  (low loss)

(3)

Switching:

fast (low loss)

medium (high loss)

Blocking:

no reverse blocking

reverse blocking

low forward voltage blocking

medium forward voltage blocking

(b)

Flybackforwardhalf bridge

Core excitation:

unipolar

unipolar

bipolar

Core type:

air gap

no air gap

no air gap

(3)

transformer use:

forward isolation  
voltage scalingisolation  
voltage scalingisolation  
voltage scaling

magnetizing current:

high

low

low

(a)  $N_1 : N_2 : N_3 = 1 : 1 : 1$

$V_o = 12 \text{ V}$

$P_o = 48 \text{ W}$

$V_d = 20 \text{ V}$

$f_{sw} = 20 \text{ kHz}$

Boundary condition  $\Rightarrow \frac{\hat{\Delta i_L}}{2} = I_L = I_o = \frac{P_o}{V_o} = \frac{48}{12} \text{ A} = \underline{4 \text{ A}}$


$\Rightarrow \hat{\Delta i_L} = \underline{8 \text{ A}}$

$V_o = DV_d \Rightarrow D = \frac{12}{20} = \underline{0.6}$

$\Rightarrow$  during off period,  $V_L = -V_o = \frac{-L \hat{\Delta i_L}}{(1-D)T_s} = \frac{-L \hat{\Delta i_L} \cdot f_{sw}}{1-D}$

$\Rightarrow L = \frac{V_o(1-D)}{\hat{\Delta i_L} \cdot f_{sw}} = \frac{12(0.4)}{8(20)(10^3)} \text{ H} = \underline{0.03 \text{ mH}} \quad (2)$


(b)  $i_c = i_L - I_o \Rightarrow$

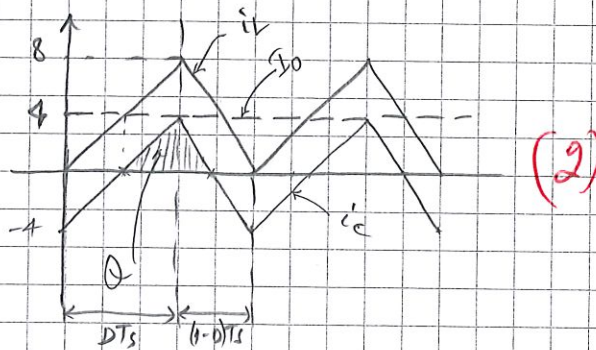

(c)  $\Delta V_o \leq 0.1V_o = 1.2 \Rightarrow \frac{Q}{C} = \left[ \frac{1}{2} (T_s) (\hat{\Delta i_L} / 2) \right] / C = \frac{\hat{\Delta i_L}}{8f_{sw}C} \leq 0.1V_o$

$\Rightarrow C \geq \frac{\hat{\Delta i_L}}{0.1V_o(8f_{sw})} = \underline{0.0417 \text{ mF}} \quad (2)$

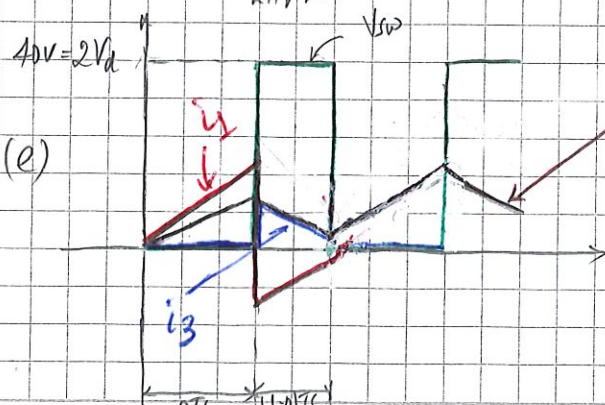(d)  $f_{corner} = \frac{1}{2\pi\sqrt{LC}} = 4.45 \text{ kHz} \Rightarrow \frac{f_{sw}}{10} = 2 \text{ kHz} !$  L & C are low for filtering the harmonics due to the switching. [L or C should increase] (2)



$i_m$ : No enough time for complete demagnetization.  
 during  $DT_s$ :  $V_d = L_m \frac{di_m}{dt} \quad (0.6T_s)$   
 during  $(1-D)T_s$ :  $-V_d = -L_m \frac{di_m}{dt} \quad (0.4T_s)$   
 but if  $L_m$  is very big,  $i_m \rightarrow 0!$

(a)  $N_1 : N_2 : N_3 = 1 : 2 : 2$

$V_d = 20 \text{ V}$

$f_{sw} = 20 \text{ kHz}$

$D = 0.3$

$L_m = 100 \mu\text{H}$

$R_{load} = 40 \Omega$

Assume CCM  $\Rightarrow V_o = \frac{N_3}{N_1} \cdot \frac{D}{1-D} \cdot V_d = \frac{2}{1} \cdot \frac{0.3}{1-0.3} \cdot 20 \text{ V} = \underline{\underline{17.143 \text{ V}}}$

$V_{o,max} = \frac{N_3 V_d}{N_2} = 20 \text{ V} > V_o$  ( $N_2$  winding not used)

$\Rightarrow I_D = \frac{V_o}{R_{load}} = \frac{17.143}{40} \text{ A} = \underline{\underline{0.429 \text{ A}}}$

During an period:  $\frac{L_m \Delta i_m}{D T_s} = V_d$

$\Rightarrow \Delta i_m = \frac{D V_d}{L_m f_{sw}} = 3 \text{ A}$


But,  $I_m = I_d + \frac{N_3 I_D}{N_1}$  &  $V_o I_D = V_o I_D \Rightarrow I_d = \frac{V_o I_D}{V_d} = \underline{\underline{0.367}}$

$\Rightarrow I_m = 0.367 + \frac{2}{1} (0.429) = \underline{\underline{1.223 \text{ A}}}$

Here  $\frac{\Delta i_m}{2} = 1.5 \text{ A} > I_m \Rightarrow$  Converter is in DCM mode

$\Rightarrow V_o = D \sqrt{\frac{R_{load}}{2 L_m f_{sw}}} \cdot V_d \leq V_{o,max} = 20$

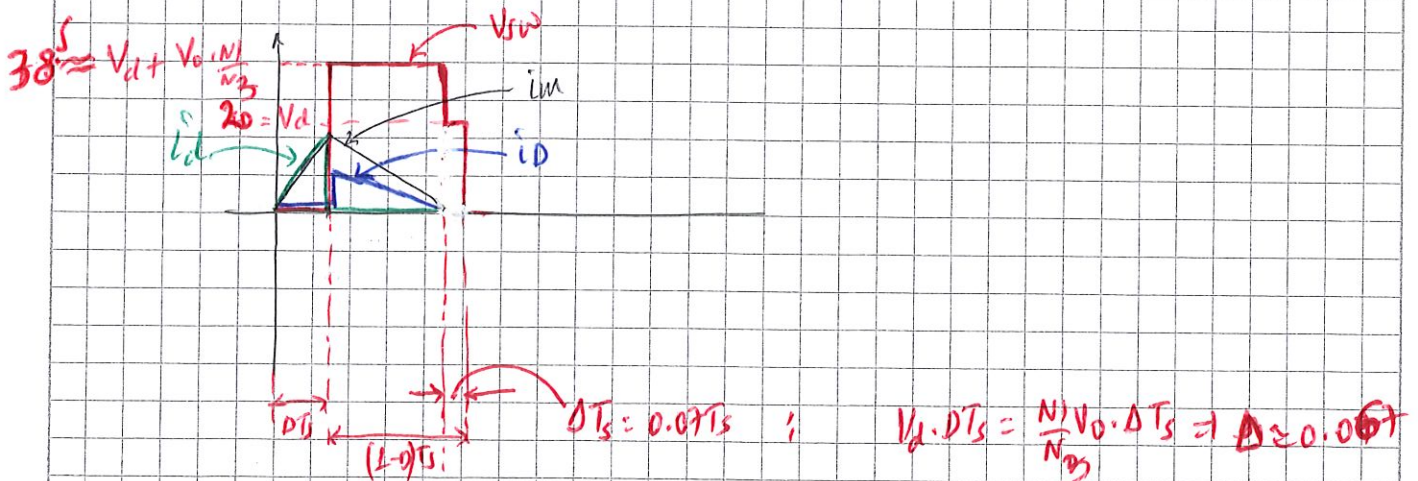$\Rightarrow V_o = 0.3 \sqrt{\frac{40}{2(0.1)(20)}} \cdot 20 = \underline{\underline{18.97 \text{ V}}} \quad (4)$



(b)  $R_{load}$ : 4 results DCM mode.

$\Rightarrow$  it should be reduced to get CCM. The maximum  $R_{load}$  to bring the converter to CCM mode is the value to make it operate on the boundary.

$$\begin{aligned}\Rightarrow \frac{\hat{\Delta i_m}}{2} &= I_m = I_D + \frac{N_3}{N_1} I_D = \frac{V_D I_D}{V_d} + \frac{N_3}{N_1} I_D \\ &= \left( \frac{V_D}{V_d} + \frac{N_3}{N_1} \right) I_D = \left( \frac{V_D}{V_d} + \frac{N_3}{N_2} \right) \left( \frac{V_D}{R_{load}} \right)\end{aligned}$$


At the Boundary,  $V_D = \frac{N_3}{N_1} \cdot \frac{D}{1-D} \cdot V_d$

$$\Rightarrow \frac{\hat{\Delta i_m}}{2} = \left( \frac{N_3}{N_1} \cdot \frac{D}{1-D} + \frac{N_3}{N_1} \right) \left( \frac{\frac{N_3}{N_1} \cdot \frac{D}{1-D} \cdot V_d}{R_{load}} \right) = \frac{D V_d}{L_m f_{sw}} \cdot \frac{1}{2} = \frac{\hat{\Delta i_m}}{2}$$

$$\Rightarrow \left( \frac{N_3}{N_1} \right)^2 \left( \frac{D}{1-D} + 1 \right) \left( \frac{1}{(1-D) R_{load}} \right) = \frac{1}{2 L_m f_{sw}} \quad (4)$$

$$\Rightarrow R_{load} = \left( \frac{2 L_m f_{sw}}{(1-D)^2} \right) \left( \frac{N_3}{N_1} \right)^2 = \underline{\underline{32.65 \Omega}}$$

(a)

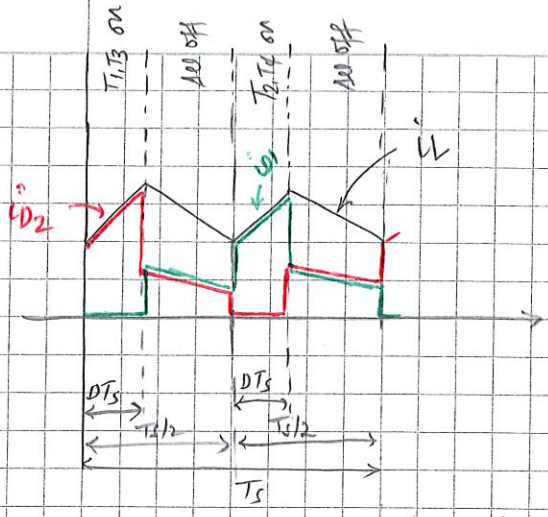

(2)


(b)

$$V_o = \frac{1}{T_s} \int_0^{T_s} v_{Di} dt$$

$$= \frac{1}{T_s} \cdot 2DT_s \cdot \frac{N_2 V_d}{N_1}$$

$$= 2 \frac{N_2}{N_1} D V_d$$
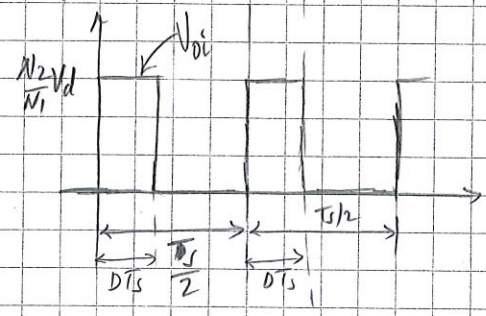
$$\Rightarrow \frac{V_o}{V_d} = 2 \frac{N_2}{N_1} D$$



(2)

(c)

Advantages :-


- ✓ optional dc capacitor
- ✓ twice the output voltage  
⇒ higher power output  
⇒ less windings for the same voltage output

Disadvantages

- ✓ more components count
- ✓ more conduction loss ⇒ less economical for lower power rating

(2)

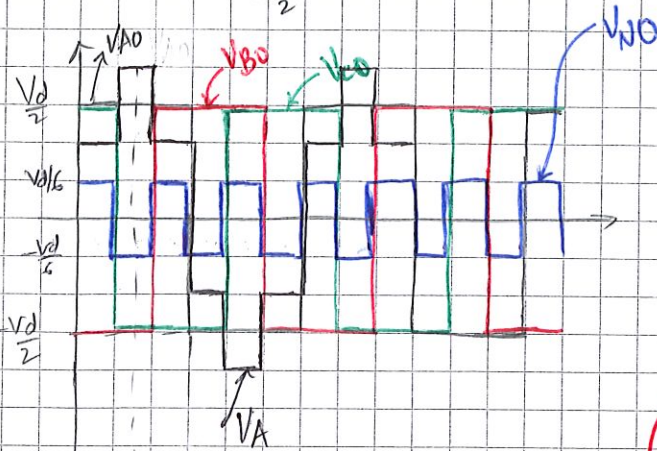(a)  $V_d = 300V \Rightarrow \pm \frac{V_d}{2} = \pm 150V$



$$V_{N0} = \frac{V_{A0} + V_{B0} + V_{C0}}{3}$$

$$V_A = V_{A0} - V_{N0}$$

$$i_A = i_{A0} + \frac{1}{L} \int_0^t V_A dt$$

(3)

(b)  $I_x = 0$  due to an inductive load

id harmonics are at  $6\omega$  for  $n = \pm 1, \pm 2, \pm 3$  (3)

id harmonics for PWM are around the switching frequency,  $n m f$ ,  $n = \pm 1, \pm 2$   
where  $m f$  is the frequency modulation ratio.


(c) PWM:  $\hat{V}_{A(n)} = m_a \cdot \frac{V_d}{2} = \underline{\underline{150V}}$  ( $m_a \leq 1$ ) (3)

square wave  $\hat{V}_{A(n)} = \frac{4}{\pi} \cdot \frac{V_d}{2} = \underline{\underline{191V}}$  (using Fourier Analysis)

(For the fundamental component,  $\hat{V}_{A(1)} = \hat{V}_{A0(1)}$  because  $\hat{V}_{N0(1)} = 0$ )

(a), (b)  $v_{s1} = 200 \sin(2\pi f t)$  ,  $\omega = 2\pi f = 100\pi$  ,  $L_s = 15 \text{ mH}$  ,  $I_d = 12 \text{ A}$   
 $v_{s2} = 200 \sin(2\pi f t - 180^\circ)$

(2) + (3)

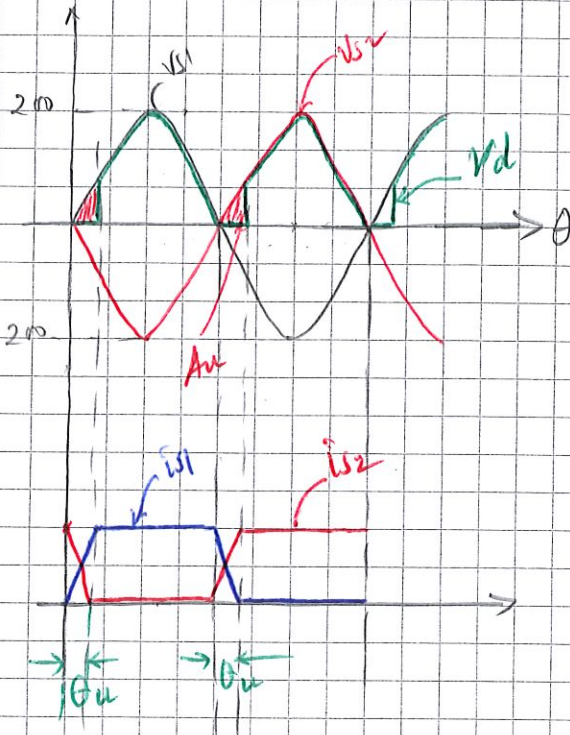

$v_{s1} > v_{s2}$  after commutation,  $i_{s1} = I_d$ ,  $i_{s2} = 0$ ,  $v_d = v_{s1}$   
 $v_{s2} > v_{s1}$  after commutation,  $i_{s1} = 0$ ,  $i_{s2} = I_d$ ,  $v_d = v_{s2}$   
 during commutation,  $i_{s1}, i_{s2} \neq 0$  and from  $T_1$  to  $T_2$   
 $i_{s1} = I_d - i_u$ ,  $i_{s2} = i_u$

$$v_d = v_{s2} - v_{s1} = v_{s2} - L_s \frac{di_u}{dt} = v_{s1} - v_{L1} = v_{s1} + L_s \frac{di_u}{dt}$$

$$\Rightarrow L_s \frac{di_u}{dt} = v_{s2} - v_{s1} = v_{L2}$$

$$\Rightarrow v_d = \frac{v_{s1} + v_{s2}}{2} \text{ during commutation} = 0$$

$i_u$  commutates from 0 to  $I_d$

$$\Rightarrow L_s \frac{di_u}{dt} = v_{s2} - v_{s1} = v_{L2}$$

$$\Rightarrow L_s \int_0^{I_d} di_u = \int_0^{\theta_u} 200 \sin \theta \cdot \frac{d\theta}{\omega}$$

$$L_s \omega I_d = [200 \cos \theta]_0^{\theta_u} = 200(1 - \cos \theta_u)$$


$$\Rightarrow \theta_u = \cos^{-1} \left[ 1 - \frac{L_s \omega I_d}{200} \right] = 25.1^\circ \quad (0.4376 \text{ rad})$$

$$V_d = \frac{1}{\pi} \int_{\theta_u}^{\pi} 200 \sin(\theta) \cdot d\theta = \frac{1}{\pi} [200 \cos \theta]_{\theta_u}^{\pi} = \frac{200 \cos \theta_u + 200}{\pi} = \underline{\underline{121.33 \text{ V}}}$$

Dot paper for Question 7 (give a page number and put this paper together with your answer sheets if you use it for your answers. The distance between the dots in the voltage plots is 5°.)

and current


1) Phase-voltage plot for part 7.a. (1)

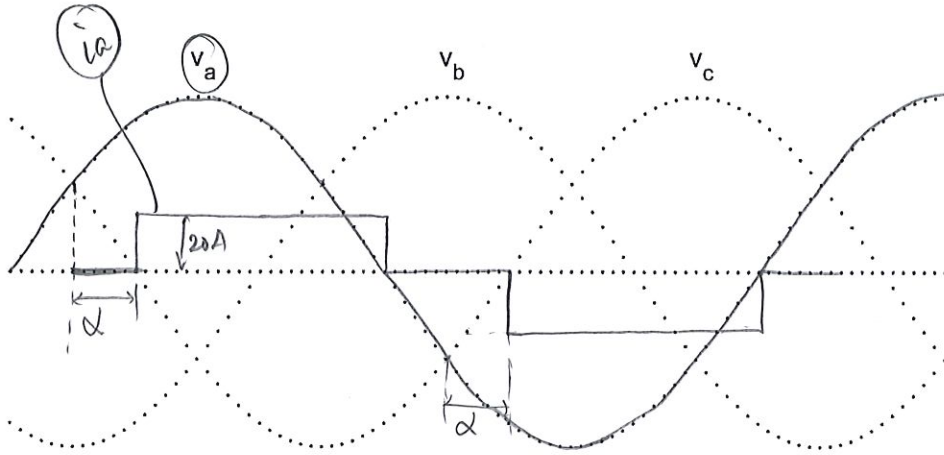


(2)

$$DPF = \cos(30^\circ) = \underline{\underline{0.866}}$$

2) Firing angle, \$\alpha\$

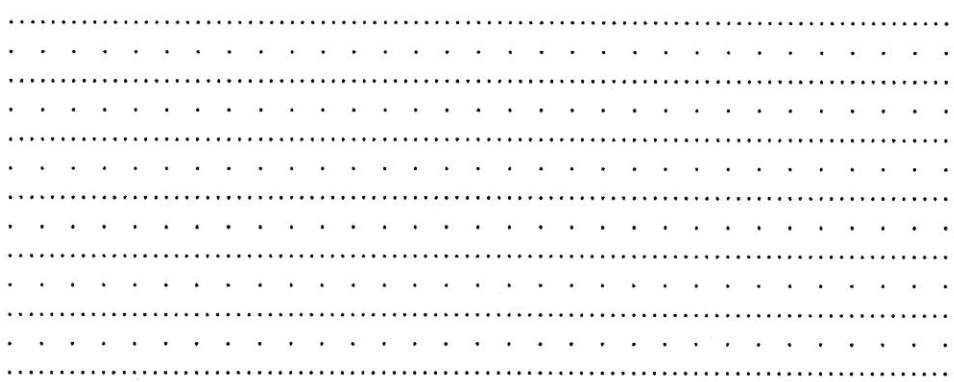

3) Output dc-voltage plot for part 7.b.

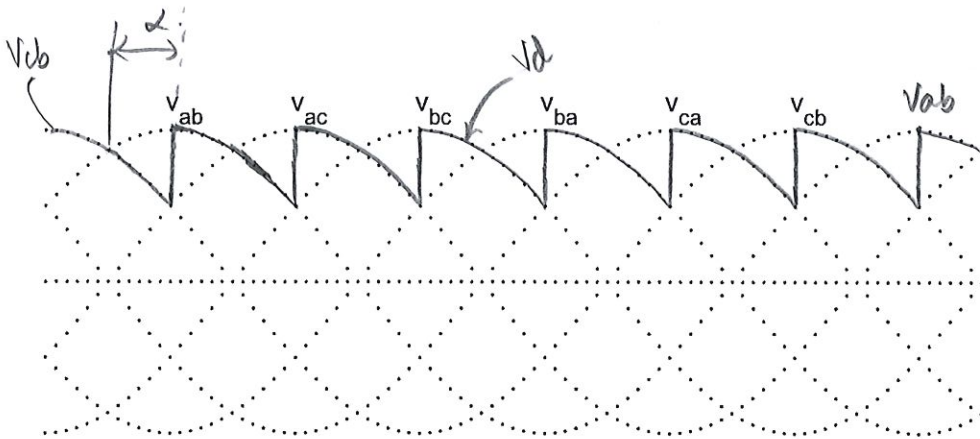

$$V_d = \frac{1}{\pi/3} \int_0^{\pi/6 + \alpha} \hat{V}_{LL} \cos(\theta) d\theta$$

$$= \frac{3}{\pi} \int_0^{\pi/6 + \alpha} 300\sqrt{3} \cos(\theta) d\theta$$

$$= \frac{3}{\pi} \{ 300\sqrt{3} \} \sin(\pi/6 + \alpha) \Big|_0^{\pi/6 + \alpha}$$

$$= \underline{\underline{429.72V}}$$

(2) OR

$$V_d = \frac{3\sqrt{2}}{\pi} V_{LL} \cos \alpha$$

$$= \frac{3\sqrt{2}}{\pi} (300\sqrt{3}) \cos \alpha$$

$$= \underline{\underline{429.72}}$$

(C) decrease \$V\_d\$ & DPF. (1)

DPF =  $\cos(\alpha + \mu/2)$  ; \$\mu\$ = commutation angle!