

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} v(\theta) d\theta = \frac{1}{2\pi} [\pi \cdot A + \pi \cdot (-A)] = \underline{0} \quad (1)$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v(\theta)^2 d\theta} = \sqrt{\frac{1}{2\pi} [A^2 \cdot 2\pi]} = \underline{A} \quad (1)$$

odd symmetry in the signal.
half-wave symmetry in the signal } \Rightarrow odd-quarter wave

\therefore the fourier coefficients are: -

$a_h = 0$ for all h , $b_h = 0$ for even h

$$b_h = \frac{4}{\pi} \int_0^{\pi/2} v(\theta) \sin(h\theta) d\theta = \frac{4}{\pi} \int_0^{\pi/2} A \sin(h\theta) d\theta = \frac{4A}{\pi h} \text{ for } h \text{ odd} \quad (2)$$

$$\Rightarrow b_1 = \frac{4}{\pi} \Rightarrow V_1^{rms} = \frac{\sqrt{a_1^2 + b_1^2}}{\sqrt{2}} = \frac{b_1}{\sqrt{2}} = \underline{\underline{\frac{2\sqrt{2}}{\pi} A}} \quad (2)$$

$$THD = \frac{\sqrt{V_{RMS}^2 - V_1^{rms2}}}{V_1^{rms}} \cdot 100\% = \frac{\sqrt{A^2 - \left(\frac{2\sqrt{2}}{\pi} A\right)^2}}{\frac{2\sqrt{2}}{\pi} A} \cdot 100\% = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} (100\%)$$

$$= \underline{\underline{48.34\%}} \quad (1)$$


CCM

switch on $\Rightarrow V_L = V_d$, diode off as it is reverse biased.switch off $\Rightarrow V_L = V_d - V_o$, diode must conduct to let the inductor current flow

$$\Rightarrow V_L = 0 = V_d \cdot DT_s + (V_d - V_o)(1-D)T_s = 0 \quad , \quad T_s = \text{switching cycle}$$

D = duty cycle
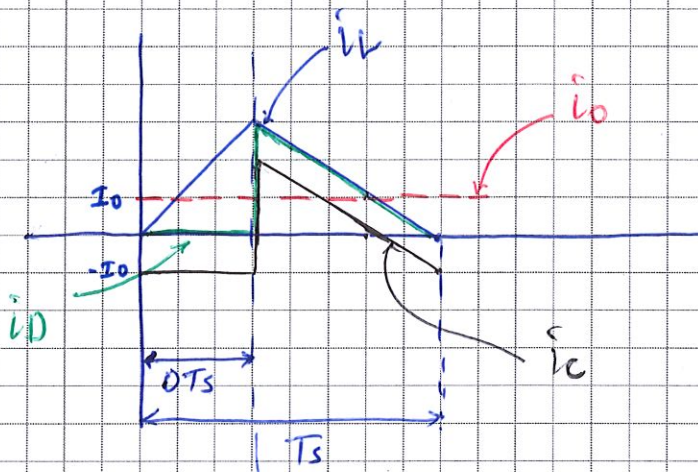
$$\Rightarrow \frac{V_o}{V_d} = \frac{1}{1-D} > 1 \quad \text{boost/stepup DC/DC converter}$$



$$i_C = i_D - i_L$$

3

CCM:
$$\left. \begin{array}{l} \text{son} \Rightarrow v_1 = V_d \\ \text{soff} \Rightarrow v_1 = -\frac{N_1}{N_3} V_o \end{array} \right\} \Rightarrow V_1^{\text{avg}} = 0 \Rightarrow V_d \cdot DT_s - \frac{N_1 V_o (1-D) T_s}{N_3} = 0$$

$$\Rightarrow \frac{V_o}{V_d} = \frac{N_3}{N_1} \cdot \frac{D}{1-D} \quad (1)$$

DCM: Energy stored during on period = energy dissipated to load in off period.

$$\Rightarrow \frac{1}{2} L_m \Delta i_m^2 = \frac{V_o^2}{R} \cdot \frac{1}{f_{sw}}$$

during on period $V_1 = V_d = L_m \frac{\Delta i_m}{DT_s} = L_m \frac{\Delta i_m \cdot f_{sw}}{D}$

$$\Rightarrow \Delta i_m = \frac{D V_d}{L_m f_{sw}}$$

$$\Rightarrow \frac{1}{2} L_m \left[\frac{D V_d}{L_m f_{sw}} \right]^2 = \frac{V_o^2}{R f_{sw}} \Rightarrow \frac{V_o^2}{V_d^2} = \frac{1}{2} \cdot \frac{D^2 R_{\text{load}}}{L_m f_{sw}}$$

$$\Rightarrow \frac{V_o}{V_d} = D \sqrt{\frac{R_{\text{load}}}{2 L_m f_{sw}}} \quad (2)$$

winding N_2 means that diode D_2 conducts if $V_{D_2} > 0$
this happens if $-V_d - V_2 > 0 \Rightarrow V_2 \leq -V_d$

during off period, this happens when $V_2 = \frac{N_2}{N_3} V_3 = \frac{N_2}{N_3} V_o \leq -V_d$

$\Rightarrow D_2$ conducts when $V_o \geq \frac{N_3}{N_2} V_d$ which then makes D to stop conducting and the V_o is limited to the maximum value.

$$\rightarrow V_o \leq \frac{N_3}{N_2} V_d.$$

$$R_{\text{load}} = \infty \Rightarrow V_o = V_{o,\text{max}} = \frac{N_3}{N_2} V_d \quad (2)$$

Midterm 2018


Melina Bezen

4

4

- (a) $0 \leq t \leq t_1$, S_1 on, S_2 off, $\Rightarrow v_o = V_d$, $i_o > 0 \Rightarrow S_1$ is conducting
 $t_1 < t \leq t_2$, S_1 off, S_2 on, $\Rightarrow v_o = 0$, $i_o > 0 \Rightarrow D_2$ conducting

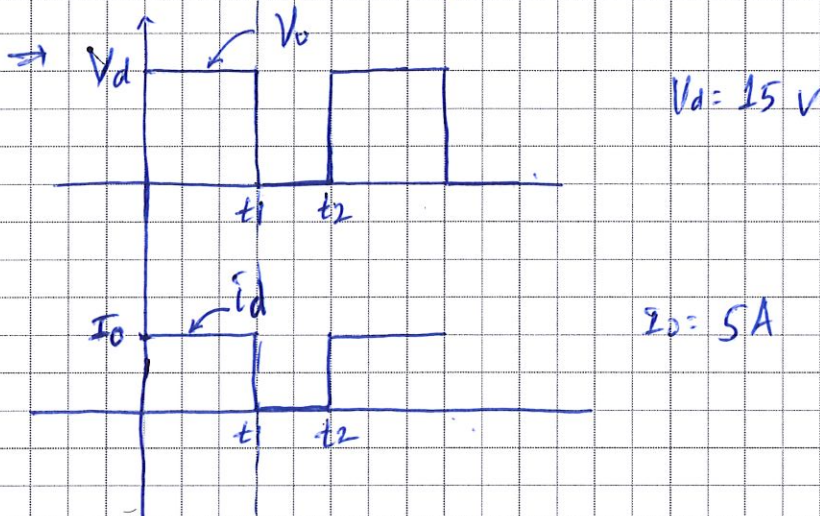- (b) $\Rightarrow i_d = i_o$ during this interval
 $\Rightarrow i_d = 0$ during this interval as S_1 and D_1 are not conducting



$$(c) \quad V_o = \frac{1}{t_2} \int_0^{t_2} v_o dt = V_d \cdot t_1 / t_2 \quad \text{but} \quad \frac{t_1}{t_2} = \frac{V_{\text{control}}}{V_d}$$

$$= V_d \cdot \frac{V_{\text{control}}}{V_d}$$

$$= V_{\text{control}} = \underline{\underline{9V}}$$

$$I_d = \frac{1}{t_2} \int_0^{t_2} i_d dt = I_o \cdot t_1 / t_2$$

$$= I_o \cdot \frac{V_{\text{control}}}{V_d}$$

$$= \frac{I_o \cdot V_o}{V_d} \quad (P_{\text{out}} = P_{\text{in}})$$

$$= \frac{5 \cdot 9}{15} \text{ A}$$

$$= \underline{\underline{3A}}$$