

Midterm Exam ENM061 Power Electronic Converters
Monday November 26, 2018


Lecturer/Tutor: Mebtu Beza/Zeyang Geng

Help: CTH approved calculator (Casio FX82, Texas TI30, Sharp EL531)


The bonus points are awarded as follows.

- 0: 0 – 3.5 pts.
 - 1: 4 – 8.5 pts.
 - 2: 8 – 11.5 pts.
 - 3: 12 – 15.5 pts.
 - 4: 16 – 20.0 pts.
-

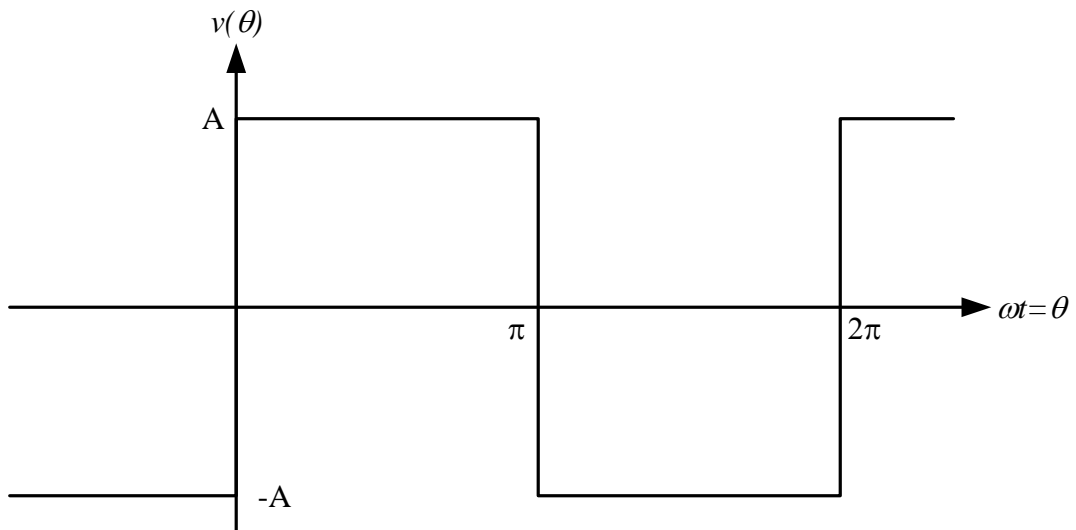
1. For the voltage waveform shown in the figure below, calculate the average value, the RMS-value of the fundamental and the total harmonic distortion of the voltage signal. (5 points)



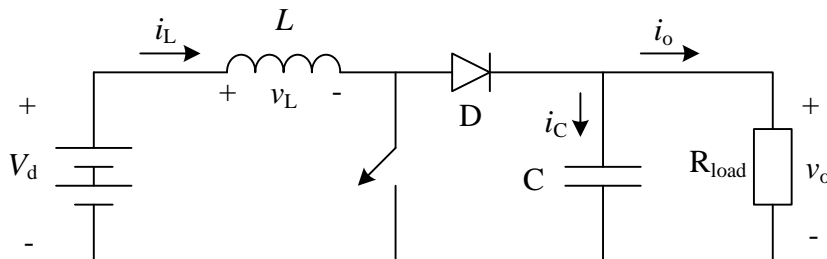2. For DC/DC converter shown below and operating in CCM mode, derive the expression of the output voltage to input voltage ratio (V_o/V_d) and identify what kind of converter it is. For the boundary condition between CCM and DCM, roughly sketch the waveforms for i_L , i_C and i_o . (5 points)





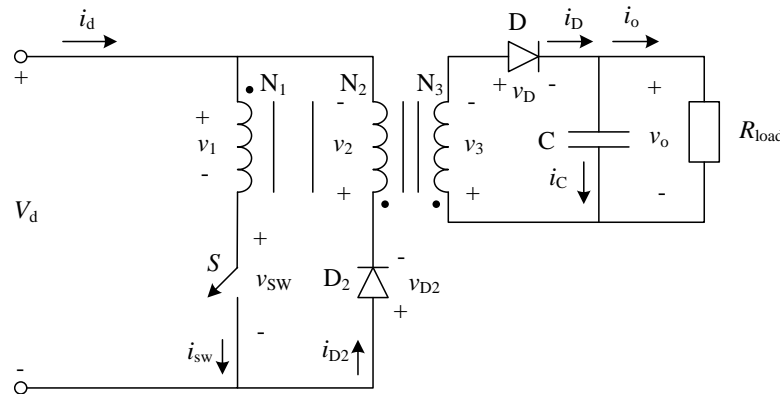3. The flyback converter below has a protective winding (N_2) with the total turns ratio of the transformer given by $N_1:N_2:N_3$ (5 points)



For CCM and DCM operation, derive the relationship between the output and input voltage (in terms of switching frequency f_{sw} , duty cycle D , mutual inductance L_m and load resistance R_{load}). From the expressions, what is the output voltage when there is no load connected, i.e. $R_{load} = \infty$.

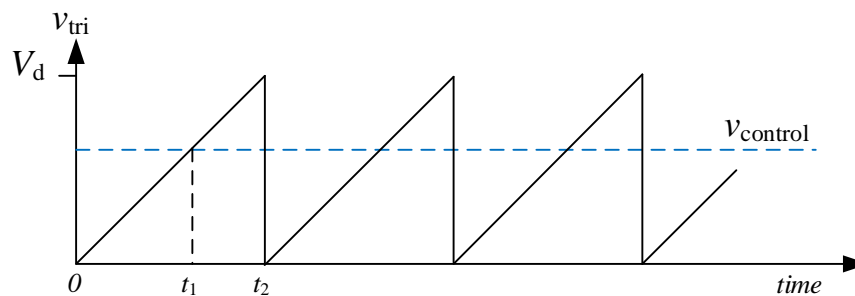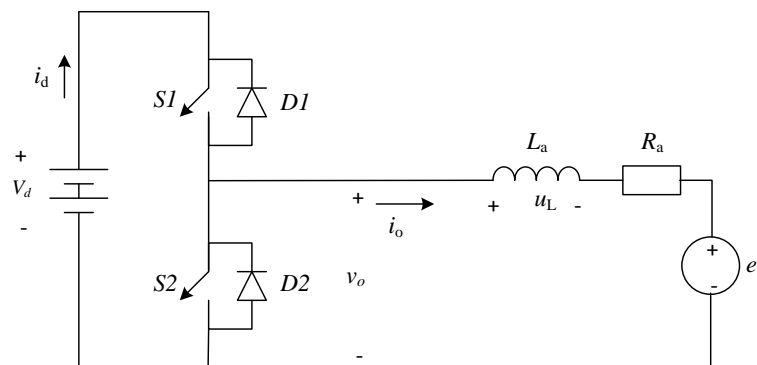4. The half-bridge DC/DC converter shown below uses a PWM voltage switching (i.e., when $v_{control} \geq v_{tri}$, $S1$ is on and $S2$ is off.; when $v_{control} < v_{tri}$, $S2$ is on and $S1$ is off). For $\hat{v}_{tri} = V_d = 15V$, $v_{control} = 9V$ and $i_o = 5A$ (5 points)



- Which active components are conducting for the interval $0 \leq t \leq t_1$ and $t_1 \leq t \leq t_2$.
- Plot the output voltage waveform v_o and input current waveform i_d for $0 \leq t \leq t_2$.
- Calculate the average output voltage V_o and the average input current I_d .

Formula sheet for the midterm exam of Power Electronic Converters (ENM061)

Fourier calculations

Table 3-1 Use of Symmetry in Fourier Analysis

Symmetry	Condition Required	a_h and b_h
Even	$f(-t) = f(t)$	$b_h = 0$ $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$ $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h $a_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \cos(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h $b_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \sin(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$

Definition of RMS-value:

$$F_{RMS} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} f(t)^2 dt}$$

Definition of RMS-value with Fourier-series:

$$F_{RMS} = \sqrt{F_0^2 + \sum_{n=1}^{\infty} F_n^2} = \sqrt{\left(\frac{a_0}{2}\right)^2 + \sum_{n=1}^{\infty} \left(\frac{\sqrt{a_n^2 + b_n^2}}{\sqrt{2}}\right)^2}$$

Trigonometry

$$\sin^2(\alpha) + \cos^2(\alpha) = 1$$

$$\sin(\alpha + \beta) = \sin(\alpha) \cos(\beta) + \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha + \beta) = \cos(\alpha) \cos(\beta) - \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha) \sin(\beta) = \frac{1}{2} (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\cos(\alpha) \cos(\beta) = \frac{1}{2} (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$

$$\int \sin(ax) dx = -\frac{1}{a} \cos(ax), \quad \int x \sin(ax) dx = \frac{1}{a^2} (\sin(ax) - ax \cos(ax)), \quad \int \cos(ax) dx = \frac{1}{a} \sin(ax)$$

$$\int x \cos(ax) dx = \frac{1}{a^2} (\cos(ax) + ax \sin(ax))$$

$$PF = \frac{P}{S} = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s}, \quad DPF = \cos \phi_1, \quad \%THD_i = 100 \frac{I_{dis}}{I_{s1}} = 100 \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} = 100 \sqrt{\sum_{h \neq 1} \left(\frac{I_{sh}}{I_{s1}}\right)^2}$$

Electromagnetics

$$e = \frac{d}{dt} \psi \quad \psi = N\phi \quad \phi = BA \quad R = \frac{l}{A\mu_r\mu_0} \quad L = \frac{\Psi}{i}$$

$$NI = R\phi = mmf \quad N\phi = LI \quad L = N^2/R \quad W = \frac{1}{2} Li^2$$

Capacitor and inductor current-voltage relationship

$$i_C = C \frac{dv_C}{dt} \quad v_L = L \frac{di_L}{dt}$$