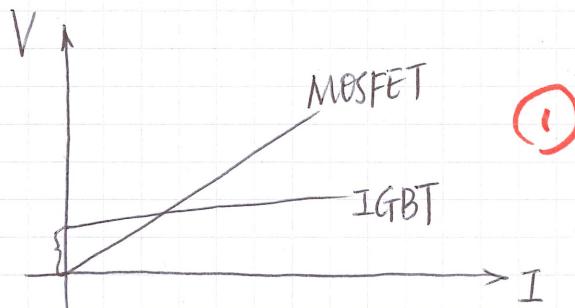


Q#1.

- (a) Fourier components represent sinusoidal components with frequencies multiples of the signal frequency of a periodic signal. ①

We need to calculate them to know the harmonic content (THD) of a signal to design the corresponding filters and avoid electromagnetic interference (EMI). ①

- (b) IGBT : smaller  $R_{on}$ , non-zero threshold conduction voltage. ①  
MOSFET : higher  $R_{on}$ , zero threshold conduction voltage. ①



Q#2.

$$(a) \ N_1 : N_2 : N_3 = 1 : 2 : 2, \ V_d = 20V, \ f_{sw} = 20 \text{ kHz}$$

$$D = 0.3, \ L_m = 100 \mu\text{H}, \ R_{load} = 20\Omega, 60\Omega, \ V_o ?$$

First identify CCM or DCM.

Assume CCM.

$$\Rightarrow \frac{V_o}{V_d} = \frac{N_3}{N_1} \cdot \frac{D}{1-D}$$

$$\Rightarrow V_o = \frac{2}{1} \cdot \frac{0.3}{0.7} \cdot 20V = 17.14V < \frac{N_3}{N_2} \cdot V_d = 20V$$

$$\Rightarrow I_o = \frac{V_o}{R_{load}} = \begin{cases} 0.857A & \text{for } R_{load} = 20\Omega \\ 0.286A & \text{for } R_{load} = 60\Omega \end{cases}$$

$$P_{in} = P_{out} \Rightarrow V_d I_d = V_o I_o$$

$$\Rightarrow I_d = \begin{cases} 0.734A & \text{for } R_{load} = 20\Omega \\ 0.244A & \text{for } R_{load} = 60\Omega \end{cases}$$

$$I_m = I_d + I_o \frac{N_3}{N_1} = \begin{cases} 2.45A & \text{for } R_{load} = 20\Omega \\ 0.82A & \text{for } R_{load} = 60\Omega \end{cases}$$
①

$$\frac{\Delta I_m}{2} = \frac{D V_d}{2 \cdot L_m \cdot f_{sw}} = 1.5A$$

$$\begin{cases} \frac{\Delta I_m}{2} < I_m & \text{for } R_{load} = 20\Omega \quad \text{CCM.} \\ \frac{\Delta I_m}{2} > I_m & \text{for } R_{load} = 60\Omega \quad \text{DCM.} \end{cases}$$
①

for  $R_{load} = 20\Omega$ .  $\Rightarrow$  CCM.  $\Rightarrow V_o = \frac{N_3}{N_1} \cdot \frac{D}{1-D} V_d = 17,14V$ .

$$< \frac{N_3}{N_2} \cdot V_d = 20V.$$

$\Rightarrow$  Winding  $N_2$  not used.



for  $R_{load} = 60\Omega$ .  $\Rightarrow$  DCM.

$$\Rightarrow V_o = D \cdot \sqrt{\frac{R_{load}}{2L_m f_{sw}}} \cdot V_d = 23,24V > \frac{N_3}{N_2} V_d = 20V.$$



$$\Rightarrow V_o = V_{o,\max} = \frac{N_3}{N_2} V_d = 20V. \quad (1)$$

$\Rightarrow$  Winding  $N_2$  is conducting.

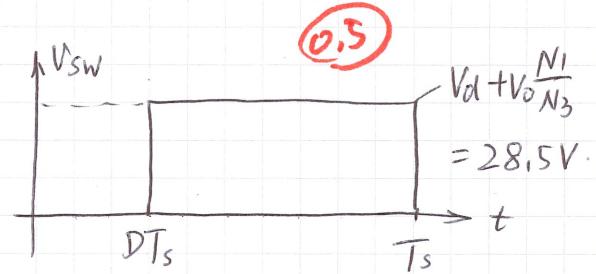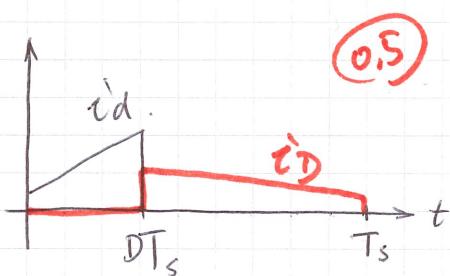(b)  $R_{load} = 20\Omega$ . CCM.  $\Delta i_m = 3A$ ,  $I_m = 1.591A$ .



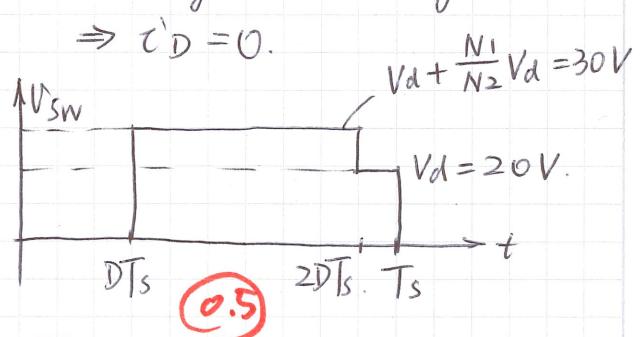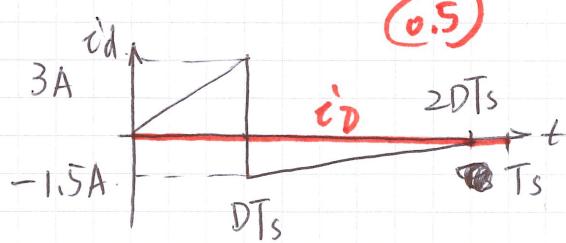$R_{load} = 60\Omega$ . DCM.  $\Delta i_m = 3A$ . winding  $N_2$  conducting.



(c) Unipolar core excitation. (1)

Core with airgap as the transformer is used for energy storage. (1)

Q #3.  $N_1 : N_3 : N_2 = 1 : 0.5 : 1$ .  $V_o = 15V$ ,  $P_o = 50W$ .

$$V_d = 25V \quad f_{sw} = 20 \text{ kHz}$$

$$(a) \quad I_o = \frac{P_o}{V_o} = \frac{50}{15} = 3.33A = I_L$$

$$\Rightarrow \Delta i_L = 0.1I_o = 0.333A \Rightarrow \frac{\Delta i_L}{2} < I_L \Rightarrow \text{CCM}$$

$$\frac{V_o}{V_d} = \frac{N_2}{N_1} \cdot D \Rightarrow D = 0.6. \quad (1)$$


$$\text{During on period. } V_L = \frac{N_2}{N_1} V_d - V_o = V_d - V_o = \frac{L \cdot \Delta i_L}{D T_s} \quad (1)$$

$$L = \frac{D \cdot (V_d - V_o)}{\Delta i_L \cdot f_{sw}} = \frac{0.6 \cdot (25V - 15V)}{0.333A \cdot 20 \text{ kHz}} = 0.9 \text{ mH}$$



$$\Rightarrow \Delta i_{Lm} = 0.01 I_o = 0.033A$$

$$\text{During on period. } V_i = V_d = L_m \frac{\Delta i_{Lm}}{D T_s}$$
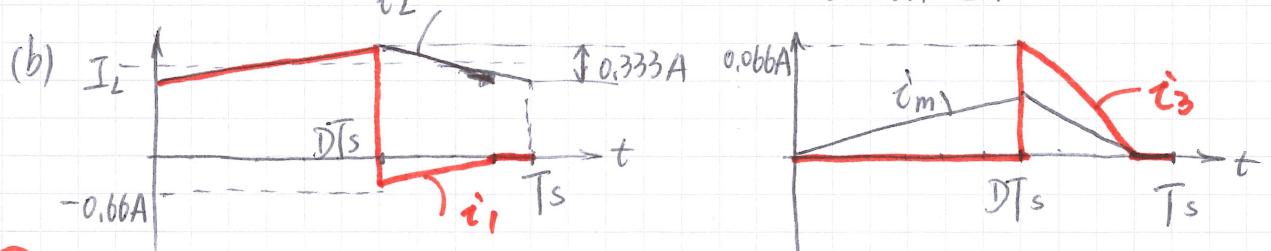
$$L_m = \frac{D \cdot V_d}{\Delta i_{Lm} \cdot f_{sw}} = \frac{0.6 \cdot 25V}{0.033A \cdot 20 \text{ kHz}} = 22.52 \text{ mH}$$





(4)

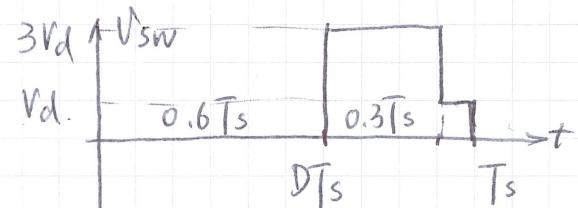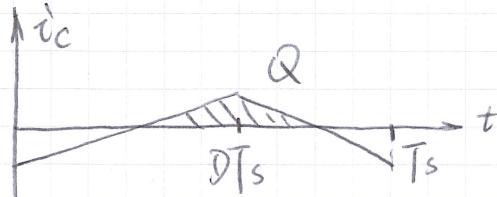


$$(c) \quad \Delta V_o = 0.01 V_o = 0.15V = \frac{Q}{C} = \frac{\frac{1}{2} \cdot \frac{\Delta i_L}{2} \cdot \frac{T_s}{2}}{C} \Rightarrow C = 13.9 \mu F. \quad (2)$$

(d). Unipolar core excitation. No air gap as  $L_m$  should be large so  $i_m$  is small. The transformer is not used for energy storage as there is another inductance. (2)

Q #4.

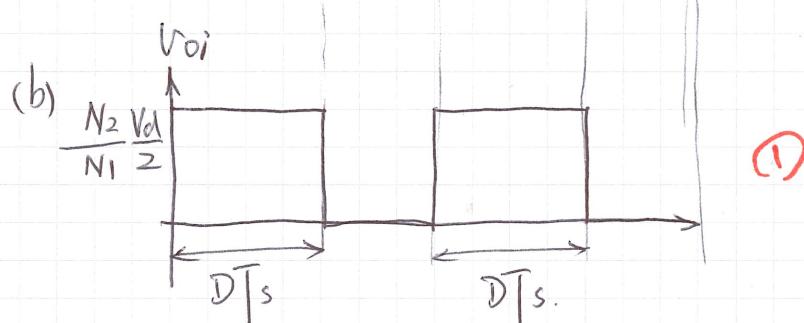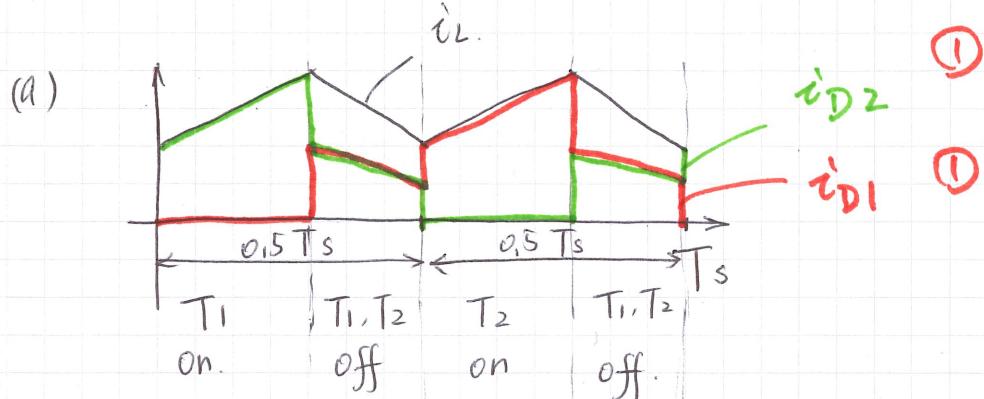
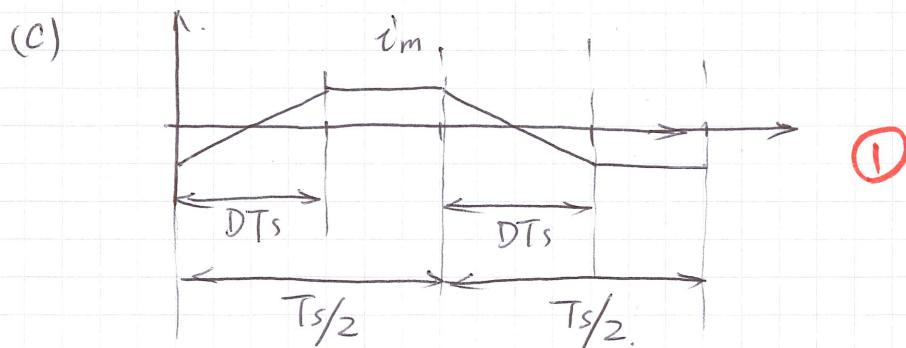
$$V_o = \frac{1}{T_s} \int_0^{T_s} V_{oi} \cdot dt = \frac{2 \cdot D\bar{T}_s \cdot \frac{N_2}{N_1} \cdot \frac{V_d}{2}}{T_s} = \frac{N_2}{N_1} \cdot V_d \cdot D$$




bipolar core excitation  $\Rightarrow$  higher operating range. ①

$\Rightarrow$  core saturation can be avoided.

Q #5

(a)

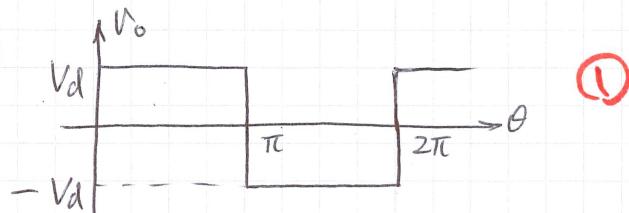

$$\hat{V}_{o,1} = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} V_d \cdot \sin \theta \cdot d\theta = V_d \cdot \frac{4}{\pi} \cdot (-\cos \theta) \Big|_0^{\frac{\pi}{2}} = \frac{4}{\pi} V_d.$$

$$V_{o,\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_d^2 \cdot d\theta} = V_d.$$

$$V_{o,1,\text{rms}} = \frac{4}{\pi} V_d \cdot \frac{1}{\sqrt{2}} = \frac{2\sqrt{2}}{\pi} V_d.$$

$$\Rightarrow \text{THD} = \frac{\sqrt{V_{o,\text{rms}}^2 - V_{o,1,\text{rms}}^2}}{V_{o,1,\text{rms}}} * 100\%.$$

$$= \frac{\sqrt{1 - (\frac{2\sqrt{2}}{\pi})^2}}{\frac{2\sqrt{2}}{\pi}} * 100\% = 48.3\%. \quad \textcircled{1}$$

(b) current harmonics

$$\left\{ \begin{array}{l} \text{1-phase : } 2n \pm 1 = 3, 5, 7, 9, \dots \\ \text{3-phase : } 6n \pm 1 = 5, 7, 11, 13, \dots \end{array} \right. \quad \textcircled{1}$$

3-phase removes odd harmonics that are multiples of 3. (1)

(c) Using PWM instead of square-wave - by using a high frequency triangular wave for modulation, (2)  
the low-order harmonics are pushed higher up.

(d) Multilevel: advantages.  $\Rightarrow$  better harmonics performance.  
 $\Rightarrow$  lower switching losses.  
disadvantages.  $\Rightarrow$  more components.  
 $\Rightarrow$  more complicated design. (1)

$$Q \# 6. \quad V_{S1} = 230V \frac{\sqrt{2}}{\sqrt{3}} \cdot \sin \theta = 230V \cdot \frac{\sqrt{2}}{\sqrt{3}} \cdot \sin(2\pi \cdot 50Hz \cdot t)$$


$$V_{S2} = 230V \cdot \frac{\sqrt{2}}{\sqrt{3}} \cdot \sin(\theta - \frac{2}{3}\pi) = 230V \cdot \frac{\sqrt{2}}{\sqrt{3}} \cdot \sin(2\pi \cdot 50Hz \cdot t - \frac{2}{3}\pi)$$

$$L_s = 5mH.$$

$$I_d = 10A$$

↑  
120°.

$$(a) \quad \alpha = 35^\circ$$

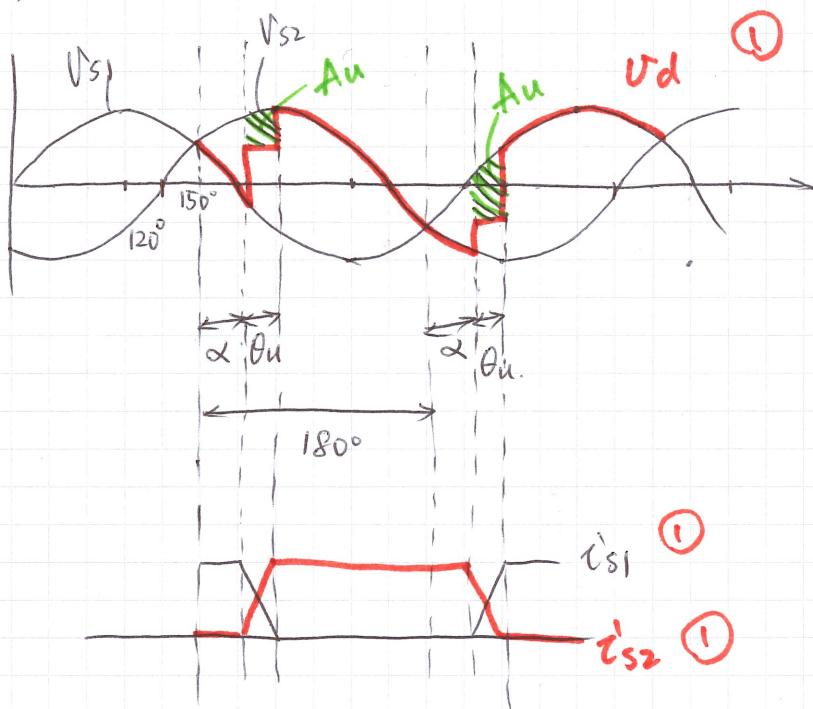

$$\textcircled{1} \quad V_d = \frac{1}{2\pi} \left( \int_{\alpha+150^\circ}^{\alpha+\pi+150^\circ} V_{S2} \cdot d\theta + \int_{\alpha+\pi+150^\circ}^{\alpha+\pi+150^\circ+\pi} V_{S1} \cdot d\theta \right) - \frac{2Au}{2\pi}$$

$$= \frac{1}{2\pi} \left[ \int_{\alpha+\frac{\pi}{6}}^{\alpha+\frac{\pi}{6}+\pi} V_{S1} \cdot d\theta + \int_{\alpha+\pi+\frac{5\pi}{6}}^{\alpha+\pi+\frac{5\pi}{6}+\pi} V_{S1} \cdot d\theta \right] - \frac{2Au}{2\pi}$$

$$\textcircled{1} \quad Au = ? \quad V_{S1} - V_{S2} - L_s \frac{di's_1}{dt} + L_s \frac{di's_2}{dt} = 0. \quad i's_1 = I_d - i'u$$

$$\Rightarrow 2L_s \frac{di'u}{dt} = V_{S2} - V_{S1}.$$

$$Au = \frac{1}{2} \int (V_{S2} - V_{S1}) \cdot d\theta = L_s \omega I_d.$$

(b)  $\alpha = 145^\circ \Rightarrow$  average output voltage will be negative. (1)  
use previous expression.

$$V_d = \frac{1}{2\pi} \left[ \int_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{\pi}{6} + \pi} V_{Si} d\theta + \int_{\alpha + \frac{5\pi}{6} + \pi}^{\alpha + \frac{5\pi}{6} + 2\pi} V_{Si} d\theta \right] - \frac{2Lswd}{2\pi}$$

$$\alpha = \frac{145}{180} \cdot \pi$$
(2)

(c) in this case  $\alpha = 0$ .

$$L_s = 0 \Rightarrow A_u = 0$$

use previous expression and no commutation in the plots.

$i_{S1}, i_{S2}$  plots. (1)

$V_d$  plot. (1)

$V_d$  calculation. (1)

$$V_d = \frac{1}{2\pi} \left[ \int_{\frac{\pi}{6}}^{\frac{\pi}{6} + \pi} V_{Si} d\theta + \int_{\frac{5\pi}{6} + \pi}^{\frac{5\pi}{6} + 2\pi} V_{Si} d\theta \right]$$