

①.

a. Varaktor, varicap (kapacitansdiod)

b. Elektrolytkondensator


c. Drossel

d. $T_j - T_a = P_F \cdot R_{thja} \cdot R_{thja} = R_{thjk} + R_{thcs} + R_{thsa} =$

$$= 10^\circ\text{C/W} + 0 + 20^\circ\text{C/W} = 30^\circ\text{C/W} \Rightarrow$$

$$P_{Fmax} = \frac{T_{jmax} - T_a}{R_{thja}} = \frac{175^\circ\text{C} - 40^\circ\text{C}}{30^\circ\text{C/W}} = \underline{\underline{45\text{W}}}$$

e. Schema där zenerdioden leder

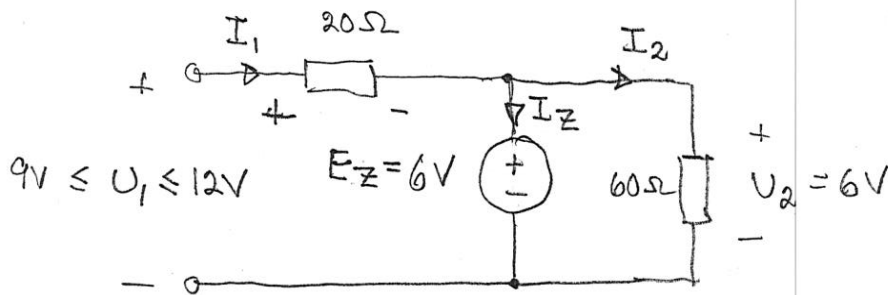

$$P_Z = E_Z \cdot I_Z \quad ; \quad I_Z = I_1 - I_2 \quad ; \quad I_2 = \frac{6\text{V}}{60\Omega} = 100\text{mA} \Rightarrow$$

$$I_Z = I_1 - 100\text{mA} \quad ; \quad I_1 = \frac{U_1 - 6\text{V}}{20\Omega}$$

$$P_{Zmax} = E_Z \cdot I_{Zmax} = 6\text{V} \cdot I_{Zmax} \quad ; \quad I_{Zmax} = I_{1max} - 100\text{mA} ;$$

$$I_{1max} = \frac{U_{1max} - 6\text{V}}{20\Omega} = \frac{12\text{V} - 6\text{V}}{20\Omega} = 300\text{mA} \Rightarrow$$

$$P_{Zmax} = 6\text{V} \cdot (300\text{mA} - 100\text{mA}) = \underline{\underline{1,2\text{W}}}$$

F. P_T = Effektivleistung
in einem Transistor

$$P_{in} = 2 \cdot E \cdot \overline{i_1}$$


$$P_{out} = R_L \cdot \frac{\hat{i}^2}{2}$$

$$\overline{i_1} = \frac{\hat{i}_1}{\pi} = \frac{\hat{i}}{\pi} = \frac{1,2A}{\pi}$$


$$\Rightarrow P_{in} = 2 \cdot 15V \cdot \frac{1,2A}{\pi} = 11,46W$$

$$P_{out} = 10\Omega \cdot \frac{(1,2A)^2}{2} = 7,2W$$
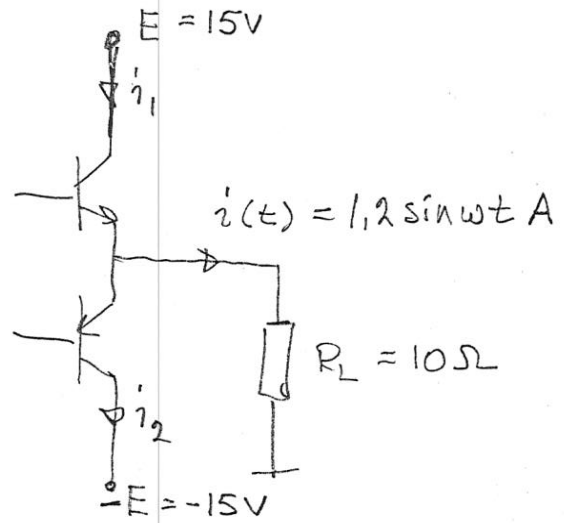
$$P_{in} = P_{out} + 2P_T \Rightarrow P_T = \frac{P_{in} - P_{out}}{2} = \frac{11,46W - 7,2W}{2} = \underline{\underline{2,13W}}$$



2.

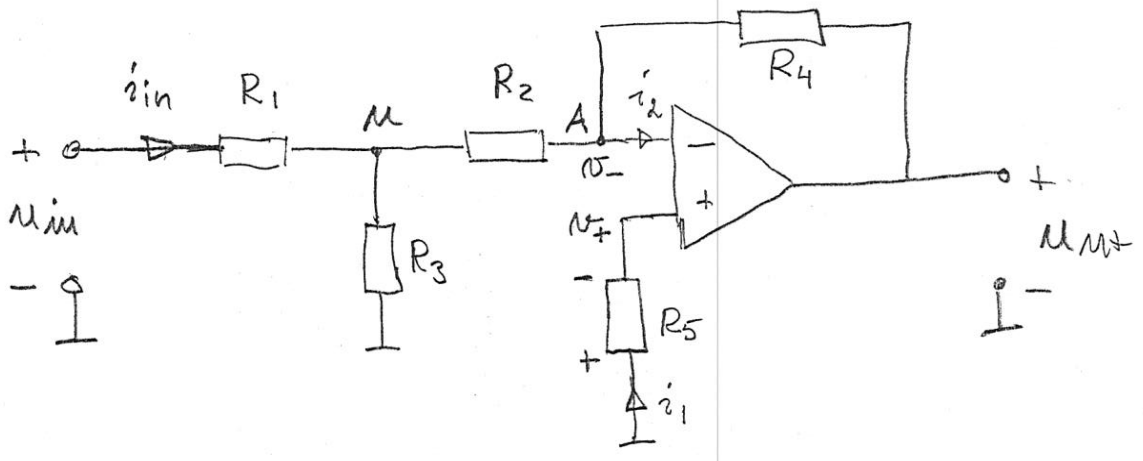

Ideal motkopplad OP $\Rightarrow i_1 = i_2 = 0$; $U_+ = U_-$
 $\Rightarrow U_+ = 0 - R_5 \cdot i_1 = 0$.

Nodanalys för att bestämma U_{Mut} :

U: $\frac{U - U_{in}}{R_1} + \frac{U}{R_3} + \frac{U - U_A}{R_2} = 0$; $U_A = U_- = U_+ = 0 \Rightarrow$

$U \cdot \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2} \right) = \frac{1}{R_1} \cdot U_{in} \Rightarrow$

$U \left(1 + \frac{R_1}{R_3} + \frac{R_1}{R_2} \right) = U_{in} \Rightarrow U = \frac{1}{1 + \frac{R_1}{R_3} + \frac{R_1}{R_2}} \cdot U_{in} \quad (1)$

A: $\frac{U_A - U}{R_2} + \frac{U_A - U_{Mut}}{R_4} = 0$; $U_A = 0 \Rightarrow$

$U_{Mut} = - \frac{R_4}{R_2} \cdot U \quad (2) \quad (\text{Inverterande förstärkare})$

$(1), (2) \Rightarrow U_{Mut} = - \frac{R_4}{R_2} \cdot \frac{1}{1 + \frac{R_1}{R_3} + \frac{R_1}{R_2}} \cdot U_{in} =$

$= - \frac{R_4}{R_2} \cdot \frac{R_2 R_3}{R_2 R_3 + R_1 (R_2 + R_3)} \Rightarrow$

$\frac{U_{Mut}}{U_{in}} = - \frac{R_3 R_4}{R_2 R_3 + R_1 (R_2 + R_3)}$



R_{in}: $U_A = 0 \Rightarrow R_2$ "parallel med" $R_3 \Rightarrow$

(4)


$$U_{in} = R_1 \cdot i_{in} + R_2 // R_3 \cdot i_{in} \Rightarrow$$

$$R_{in} = \frac{U_{in}}{i_{in}} = R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}$$

3

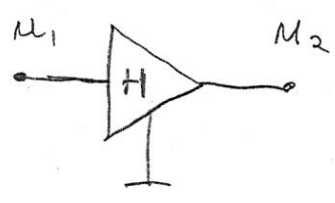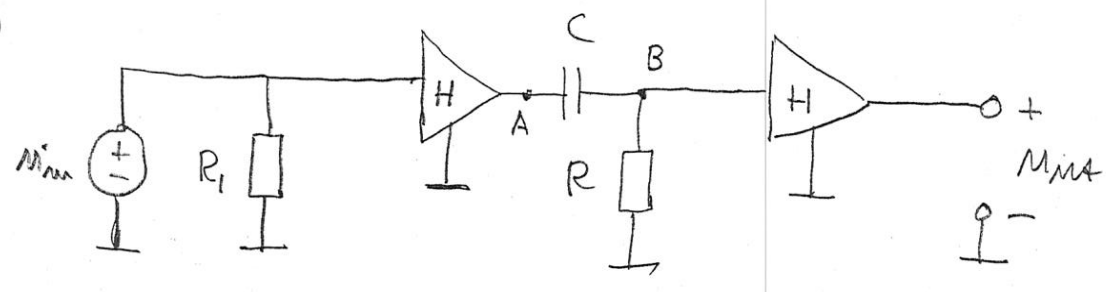

↔

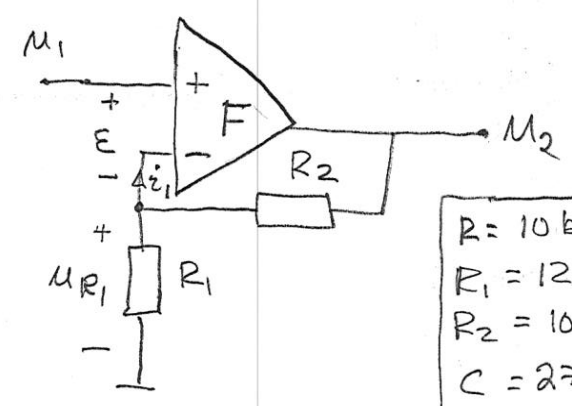

$R = 10 \text{ k}\Omega$
 $R_1 = 12 \text{ k}\Omega$
 $R_2 = 100 \text{ k}\Omega$
 $C = 270 \text{ nF}$

$F_0 = 200000$
 $\omega_0'' = 30 \text{ rad/s}$

$F(s) = \frac{F_0}{1 + \frac{s}{\omega_0''}}$; $R_{in} = \infty$, $R_{ut} = 0$; Bestäm $H(s)$:

$H(s) = \frac{M_2}{M_1}$; $M_2 = F(s) \cdot \varepsilon$; $\varepsilon = M_1 - M_{R1}$;

$i_1 = 0 \Rightarrow M_{R1} = \frac{R_1}{R_1 + R_2} \cdot M_2 = \beta \cdot M_2$, där $\beta = \frac{R_1}{R_1 + R_2} = 0,107$

$\Rightarrow M_2 = F(s) \cdot (M_1 - \beta \cdot M_2) = F(s) \cdot M_1 - \beta F(s) \cdot M_2 \Rightarrow$

$M_2 (1 + \beta F(s)) = F(s) \cdot M_1 \Rightarrow H(s) = \frac{F(s)}{1 + \beta \cdot F(s)} =$

$= \frac{\frac{F_0}{1 + \frac{s}{\omega_0''}}}{1 + \beta \cdot \frac{F_0}{1 + \frac{s}{\omega_0''}}} = \frac{F_0}{1 + \frac{s}{\omega_0''} + \beta \cdot F_0} = \frac{F_0}{1 + \beta F_0} \cdot \frac{1}{1 + \frac{s}{(1 + \beta F_0) \cdot \omega_0''}} =$

$= \frac{9,33}{1 + \frac{s}{643 \cdot 10^3}}$

6

Bestäm nu $F_{TOT} = \frac{U_{ut}}{U_{in}}$:

$R_{in} = \infty$; $R_{ut} = 0$ hos varje OP ger att de tre stegen ej belastar varandra, vilket ger


$$F_{TOT}(s) = \frac{U_{ut}}{U_{in}} = \frac{U_{MA}}{U_B} \cdot \frac{U_B}{U_A} \cdot \frac{U_A}{U_{in}}$$

$$U_B = \frac{R}{R + \frac{1}{sC}} \cdot U_A \Rightarrow \frac{U_B}{U_A} = \frac{sRC}{1+sRC} = \frac{\frac{s}{370}}{1 + \frac{s}{370}}$$

Så att $F_{TOT}(s) = H(s) \cdot \frac{\frac{s}{370}}{1 + \frac{s}{370}} \cdot H(s) =$

$$= \left(\frac{9,33}{1 + \frac{s}{640 \cdot 10^3}} \right)^2 \cdot \frac{\frac{s}{370}}{1 + \frac{s}{370}}$$

Amplitudfunktion:

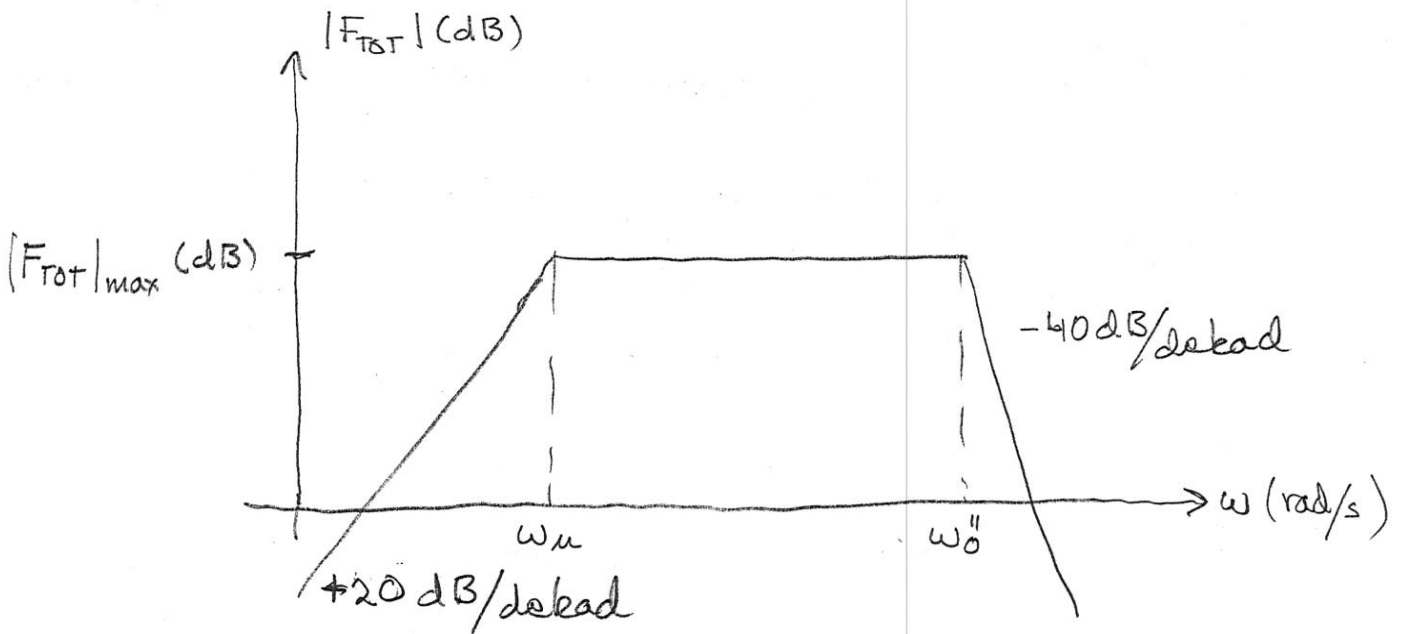

$|F_{TOT}|_{max}$ ges an $370 \ll \omega \ll 643 \cdot 10^3$:


$$|F_{TOT}| \approx \left| \left(\frac{9,3}{1+0} \right)^2 \cdot \frac{\frac{s}{370}}{\frac{s}{370}} \right| = \underline{\underline{87 \text{ ggr}}} = \underline{\underline{38,8 \text{ dB}}}$$

$$\omega_n = \underline{\underline{370 \text{ rad/s}}}$$

$$\omega_{\ddot{o}} \text{ (dubbelpol)} = 643 \cdot 10^3 \text{ rad/s} \cdot \sqrt{2^{1/2} - 1} = \underline{\underline{414 \text{ krad/s}}}$$

4


8

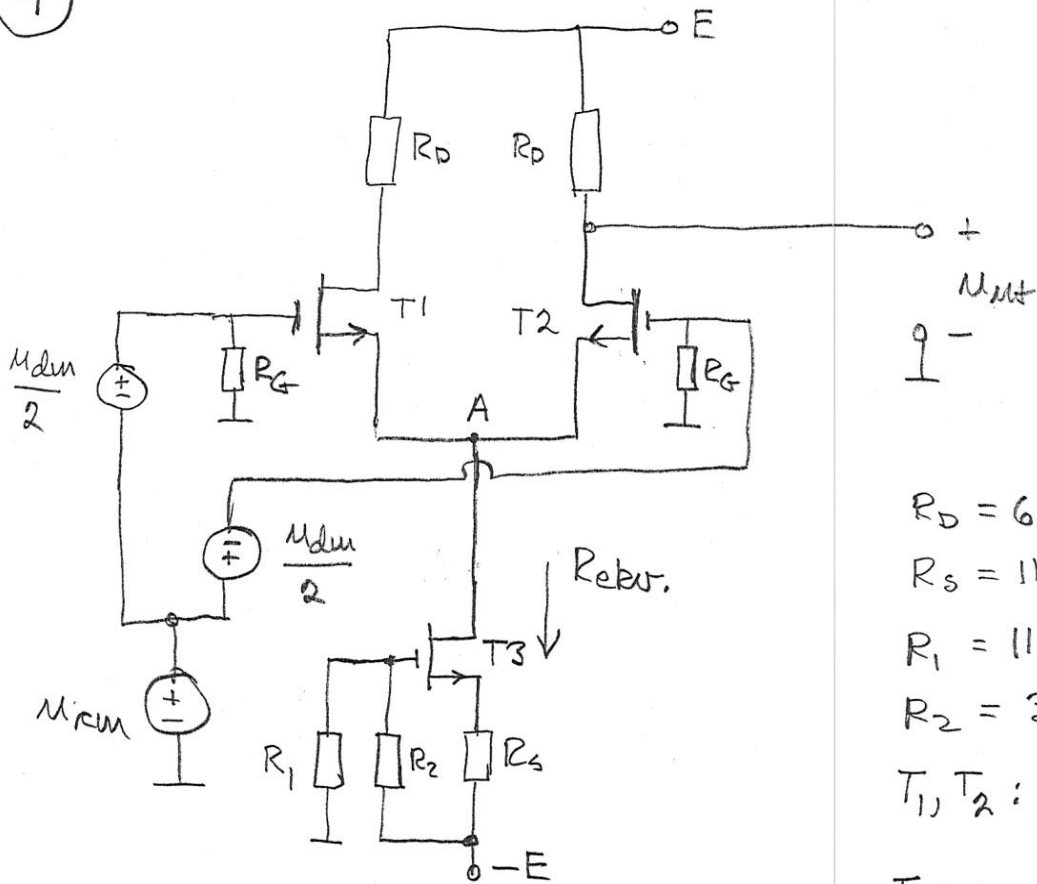


- $R_D = 6,8 \text{ k}\Omega$
- $R_S = 1 \text{ k}\Omega$
- $R_1 = 11,4 \text{ k}\Omega$
- $R_2 = 3,6 \text{ k}\Omega$
- $T_1, T_2: g_m = 3 \text{ mA/V}$
- $T_3: g_{m3} = 5 \text{ mA/V}; r_o = 30 \text{ k}\Omega$

Rekr. är den ekvivalenta signalresistansen hos den strömgenerator som T3 utgör

$$\text{CMRR} = \left| \frac{F_{dcm}}{F_{cm}} \right|$$

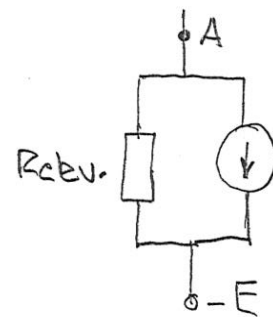

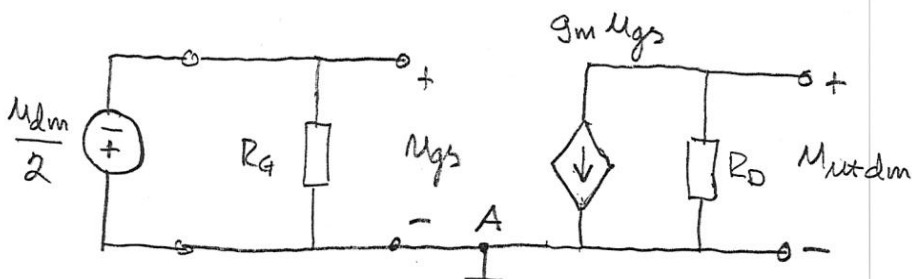
F_{dcm} : $U_{cm} = 0$; $U_A = 0$. Beträkta T2



$$\left. \begin{aligned} U_{utdcm} &= -g_m U_{gs} \cdot R_D \\ U_{gs} &= -\frac{U_{dcm}}{2} \end{aligned} \right\} \Rightarrow U_{utdcm} = -g_m \cdot \left(-\frac{U_{dcm}}{2}\right) \cdot R_D \Rightarrow$$

$$F_{dcm} = \frac{U_{utdcm}}{U_{dcm}} = \frac{g_m R_D}{2} = \underline{\underline{10,299}}$$

F_{cm} : Betrachte T2

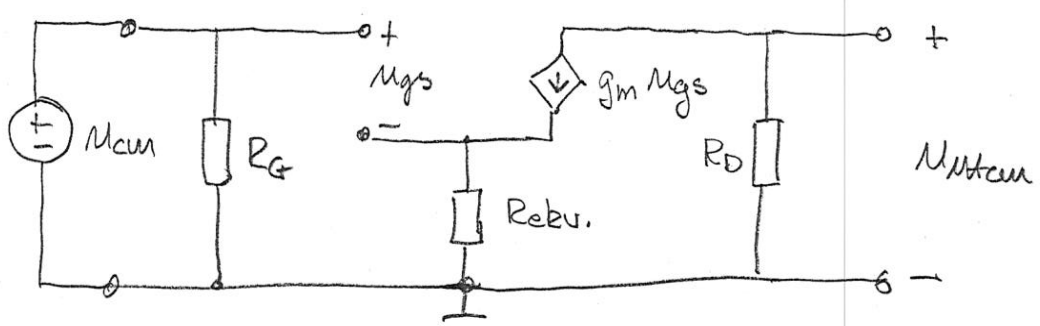


$$U_{M_{tcm}} = -g_m U_{gs} \cdot R_D$$

$$M_{cm} = U_{gs} + g_m U_{gs} \cdot R_{ebv} = (1 + g_m R_{ebv}) \cdot U_{gs} \Rightarrow$$

$$F_{cm} = \frac{U_{M_{tcm}}}{M_{cm}} = - \frac{g_m R_D}{1 + g_m R_{ebv}}$$

Rebv. Signalschema Strömgenerator

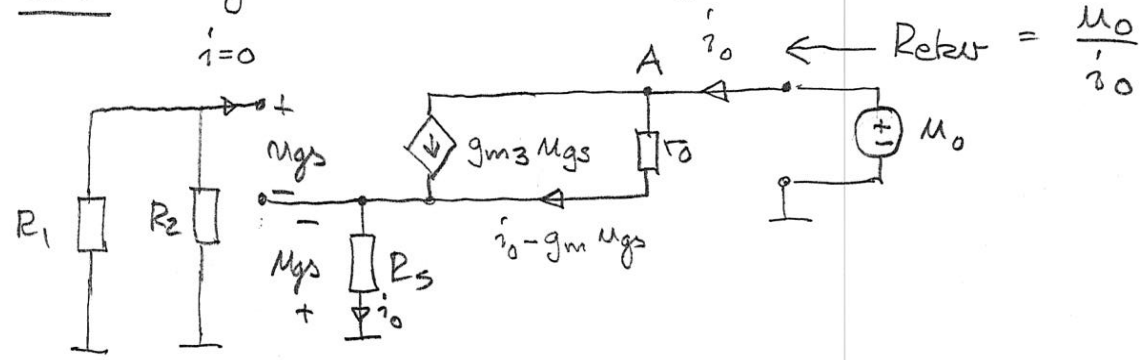

$$\left. \begin{aligned} M_0 &= r_o (i_0 - g_{m3} U_{gs}) + R_s \cdot i_0 \\ U_{gs} &= -R_s \cdot i_0 \end{aligned} \right\} \Rightarrow M_0 = [(1 + g_{m3} R_s) r_o + R_s] \cdot i_0 \Rightarrow$$

$$R_{ebv} = \frac{M_0}{i_0} = (1 + g_{m3} R_s) \cdot r_o + R_s = 180 \text{ k}\Omega \Rightarrow$$

$$F_{cm} = -18,8 \cdot 10^{-3} \text{ ggr} \Rightarrow$$


$$CMRR = \left| \frac{F_{dm}}{F_{cm}} \right| = \left| \frac{10,2}{-18,8 \cdot 10^{-3}} \right| = \underline{\underline{543 \text{ ggr}}} = \underline{\underline{54,7 \text{ dB}}}$$

⑤ Mellanhöga frekvenser betyder

⑩

- C_s, C kortslutna
- C_{gs}, C_{gd}, C_b avbrött

Detta ger följande småsignalschema

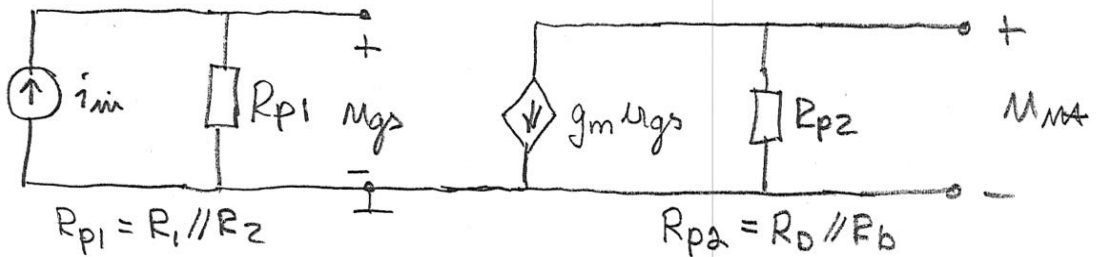


$$\left. \begin{aligned} \bullet U_{gs} &= R_{p1} \cdot i_{in} \\ \bullet U_{Mitt} &= -g_m U_{gs} \cdot R_{p2} \end{aligned} \right\} \Rightarrow \begin{aligned} U_{Mitt} &= -g_m R_{p1} \cdot R_{p2} \cdot i_{in} \Rightarrow \\ \frac{U_{Mitt}}{i_{in}} &= -g_m R_{p1} \cdot R_{p2} \quad (1) \end{aligned}$$

g_m : DC-schema: C_s, C avbrött $i_{in} = 0$ (signalström)
 $k = 10 \text{ mA/V}^2$ $V_t = 1,5 \text{ V}$ $R_b = 3,9 \text{ k}\Omega$

$$\bullet I_D = \frac{k}{2} (U_{GS} - V_t)^2 \quad (2)$$

$$\bullet I_D = \frac{U_{RS}}{R_S} = \frac{V_G - U_{GS}}{R_S} \quad (3)$$
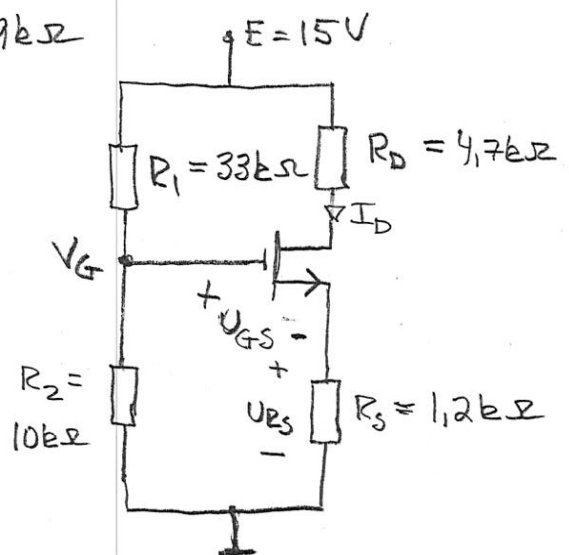
$$\bullet V_G = \frac{R_2}{R_1 + R_2} \cdot E = \frac{10 \text{ k}}{33 \text{ k} + 10 \text{ k}} \cdot 15 \text{ V} = 3,49 \text{ V} \quad (3)$$



(2), (3) ger

$$\frac{k}{2} (U_{GS} - V_t)^2 = \frac{V_G - U_{GS}}{R_S} \Rightarrow$$

$$(U_{GS} - V_t)^2 = \frac{2V_G}{k \cdot R_S} - \frac{2U_{GS}}{k \cdot R_S} \Rightarrow U_{GS}^2 - 2V_t \cdot U_{GS} + V_t^2 = \frac{2V_G}{k \cdot R_S} - \frac{2U_{GS}}{k \cdot R_S}$$

⇒

$$U_{GS}^2 + \left(\frac{2}{k \cdot R_S} - 2V_t \right) \cdot U_{GS} + V_t^2 - \frac{2V_G}{k \cdot R_S} = 0$$

⇒ (Utan enheter) tillsammans med (3)

$$U_{GS}^2 + \left(\frac{2}{10m \cdot 1,2k} - 2 \cdot 1,5 \right) U_{GS} + 1,5^2 - \frac{2 \cdot 3,49}{10m \cdot 1,2k} = 0$$

⇒

$$U_{GS}^2 - 2,83 U_{GS} + 1,67 = 0 \Rightarrow U_{GS} = \begin{cases} 2V \\ 0,831V \text{ (strykt)} \end{cases}$$

$$\Rightarrow U_{GS} = 2V \Rightarrow I_D = \frac{10mA/V^2}{2} (2V - 1,5V)^2 = \underline{1,25mA}$$


$$\Rightarrow g_m = \sqrt{2 \cdot k \cdot I_D} = \sqrt{2 \cdot 10mA/V^2 \cdot 1,25mA} = \underline{5mA/V}$$

$$(1) \text{ ger nu } \frac{M_{ut}}{i_{in}} = -5mA/V \cdot (33k\Omega // 10k\Omega) \cdot (4,7k\Omega // 3,9k\Omega) =$$

$$= \underline{\underline{-82kV/A}}$$

6

12

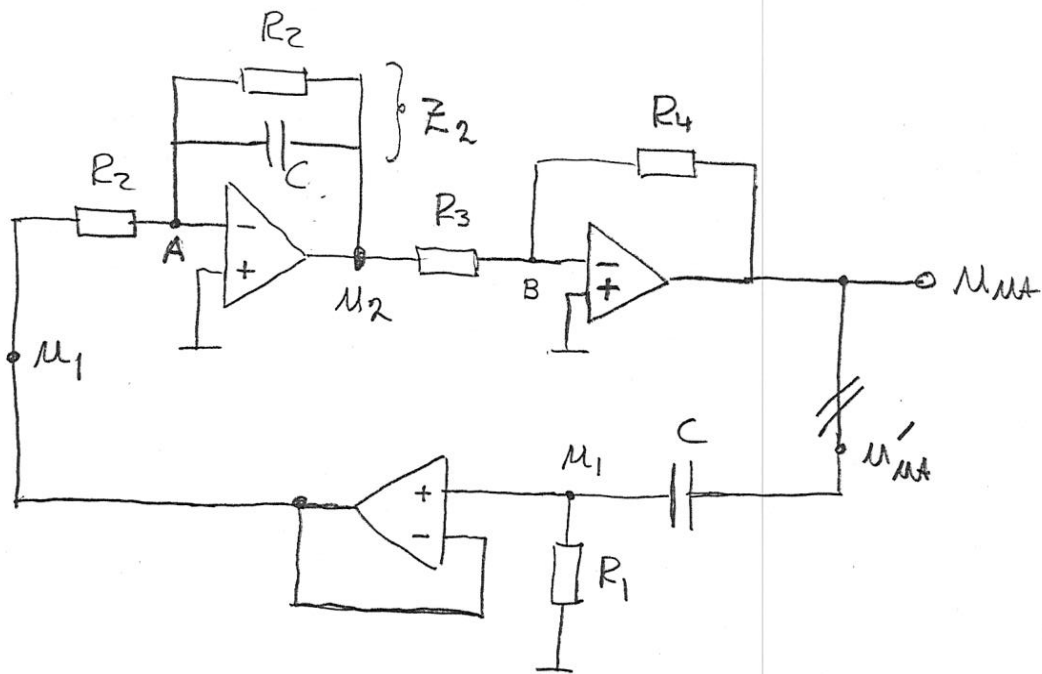

- $R_1 = 5k\Omega$
- $R_2 = 10k\Omega$
- $R_3 = 1k\Omega$
- $C = 15nF$

Sinussvängning: $R_4 = ? ; f = ?$

$$\text{Teckna } T(s) = \frac{U_{Mut}}{U'_{Mut}}$$

Ideala motkopplade OP: $\begin{cases} i_{strömmar} = 0 \\ \text{lika potential på ingångar} \end{cases}$

$\Rightarrow U_1$ ges av spänningsdelning:

$$U_1 = \frac{R_1}{R_1 + \frac{1}{sC}} \cdot U'_{Mut} = \frac{sR_1C}{1 + sR_1C} \cdot U'_{Mut} \quad (1)$$

Nodanalys i A: $\frac{V_A - U_1}{R_2} + \frac{V_A - U_2}{Z_2} = 0 ; V_A = 0 \Rightarrow$

$$U_2 = -\frac{Z_2}{R_2} \cdot U_1 \quad (\text{inverterande koppling}).$$

$$Z_2 = \frac{R_2 \cdot \frac{1}{sC}}{R_2 + \frac{1}{sC}} = \frac{R_2}{1 + sR_2C} \Rightarrow U_2 = -\frac{1}{1 + sR_2C} \cdot U_1 \quad (2)$$

Nodanalys i B:

$$\frac{U_B - U_2}{R_3} + \frac{U_B - U_{Mut}}{R_4} = 0 ; U_B = 0 \Rightarrow$$

$$U_{Mut} = -\frac{R_4}{R_3} \cdot U_2 \quad (3) \quad (\text{inverterande koppling})$$

(1), (2), (3) ger nu att

$$M_{Mtt} = \left(-\frac{R_4}{R_3}\right) \cdot \left(-\frac{1}{1+sR_2C}\right) \cdot \frac{sR_1C}{1+sR_1C} \cdot M'_{Mtt} \Rightarrow$$

$$T(s) = \frac{M_{Mtt}}{M'_{Mtt}} = \frac{R_4}{R_3} \cdot \frac{sR_1C}{(1+sR_2C)(1+sR_1C)}$$

\Rightarrow

$$T(j\omega) = \frac{R_4}{R_3} \cdot \frac{j\omega R_1C}{(1+j\omega R_2C)(1+j\omega R_1C)} = \frac{R_4}{R_3} \cdot \frac{j\omega R_1C}{1+j\omega(R_1+R_2)C - \omega^2 R_1R_2C^2}$$

Barkhausens svängningsvillkor $T(j\omega) = 1 \Rightarrow$

- $1 - \omega^2 R_1R_2C^2 = 0 \quad (4)$

- $\frac{R_4}{R_3} \cdot \frac{R_1C}{(R_1+R_2)C} = 1 \quad (5)$

$$(4) \Rightarrow 1 - (2\pi f)^2 \cdot R_1R_2C^2 = 0 \Rightarrow$$

$$f = \frac{1}{2\pi \cdot \sqrt{R_1R_2C^2}} = \underline{\underline{1,06 \text{ kHz}}}$$

$$(5) \Rightarrow R_4 = \frac{R_3(R_1+R_2) \cdot C}{R_1C} = \frac{R_3(R_1+R_2)}{R_1} = \underline{\underline{5 \text{ k}\Omega}}$$
