

1a  $T_j - T_a = P_f (R_{thjc} + R_{thcs} + R_{thsa}) \Rightarrow$   
 $150^\circ\text{C} - 40^\circ\text{C} = 8\text{W} (2^\circ\text{C/W} + 0^\circ\text{C/W} + R_{thsa}) \Rightarrow$   
 $110^\circ\text{C} = 16^\circ\text{C} + 8\text{W} \cdot R_{thsa} \Rightarrow R_{thsa} = \underline{\underline{11,8^\circ\text{C/W}}}$

1b Resistorer parallella kapacitans gör att resistorer impedans minskar.

1c  $I_{Zmax} = \frac{4\text{W}}{9,1\text{V}} = 439,5\text{mA}$

$U_{imax} = 20\text{V} \Rightarrow R_{min} = \frac{20\text{V} - 9,1\text{V}}{439,5\text{mA}} = \underline{\underline{25\Omega}}$

1d Klass AB-steglet har högre maximal verkningsgrad (mindre förluster i tungång).

1e SlewRate = utspänningens maximalt möjliga stighastighet


1f  $T(s) = \frac{a \cdot s}{s^2 + (b+100) \cdot s + 100b}$

$T(j\omega) = 1 \Rightarrow \frac{j a \omega}{-\omega^2 + 100b + j(b+100)\omega} = 1$

$\omega = 100 \Rightarrow$

$100b = 100^2 \Rightarrow \underline{\underline{b = 100}}$

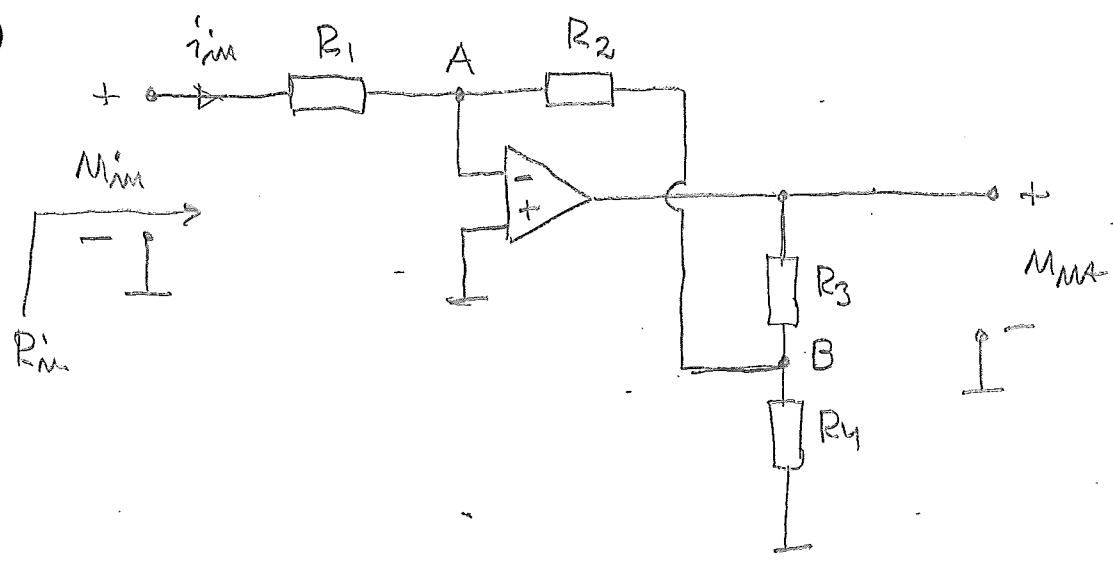$\frac{a \cdot 100}{(b+100) \cdot 100} = 1 \Rightarrow a = b+100 = \underline{\underline{200}}$



Ideal motkopplad OP  $\Rightarrow$    
 • inströmmar = 0   
 • lika potential på ingångarna.

R<sub>in</sub>:  $R_{in} = \frac{U_{in}}{i_{in}}$

$U_A = 0 \Rightarrow i_{in} = \frac{U_{in}}{R_1} \Rightarrow R_{in} = \frac{U_{in}}{i_{in}} = \underline{\underline{R_1}}$

$\frac{U_{out}}{U_{in}}$ : Nodanalys

A:  $\frac{U_A - U_{in}}{R_1} + \frac{U_A - U_B}{R_2} = 0$ ;  $U_A = 0 \Rightarrow$

$U_B = -\frac{R_2}{R_1} \cdot U_{in} \quad (1)$


B:  $\frac{U_B - U_A}{R_2} + \frac{U_B - U_{out}}{R_3} + \frac{U_B}{R_4} = 0$ ;  $U_A = 0 \Rightarrow$

$U_{out} = \left(1 + \frac{R_3}{R_2} + \frac{R_3}{R_4}\right) \cdot U_B = -\frac{R_2}{R_1} \cdot \left(1 + \frac{R_3}{R_2} + \frac{R_3}{R_4}\right) \Rightarrow$


$\frac{U_{out}}{U_{in}} = -\frac{R_2}{R_1} \cdot \left(1 + \frac{R_3}{R_2} + \frac{R_3}{R_4}\right)$

3) Beträkta T2 för DM- och CM-signaler

3

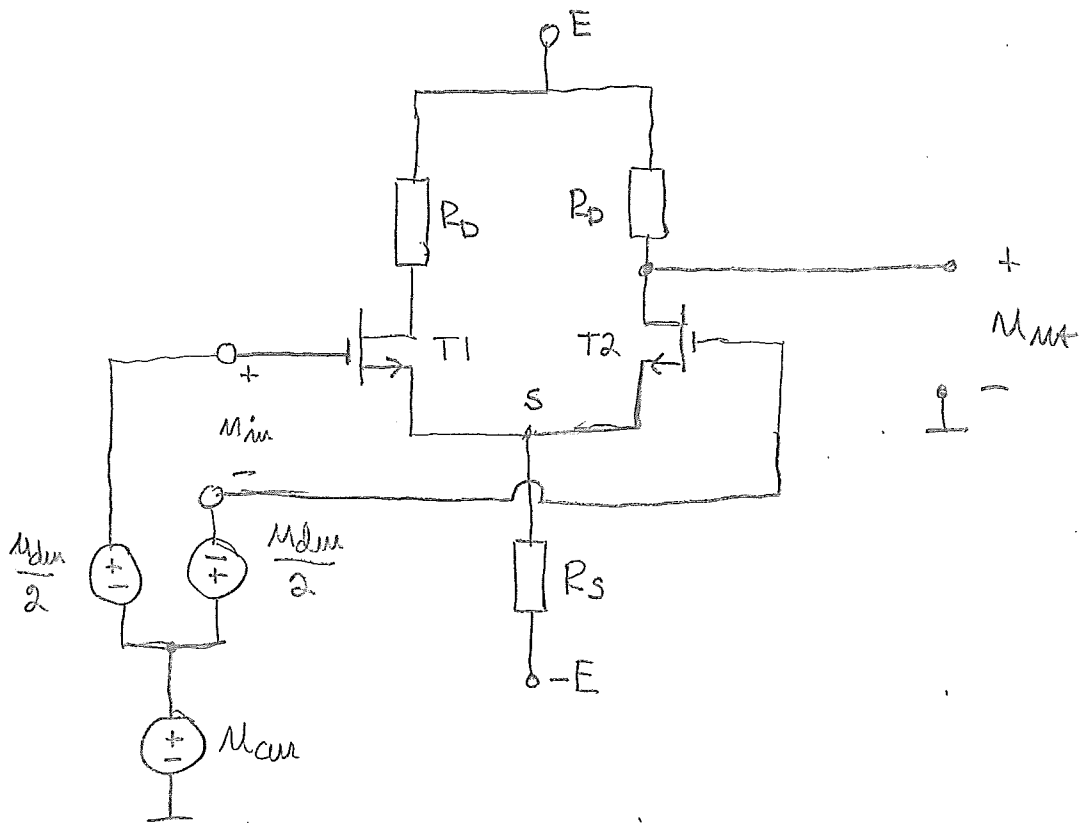

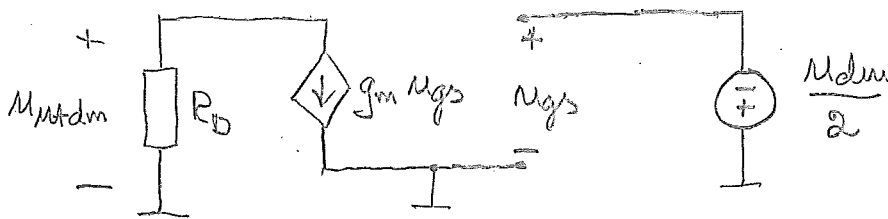DM:  $V_{cm} = 0$  . Småsignalschema  
 $V_S = 0$




$$V_{out-dm} = -g_m V_{gs} \cdot R_D$$

$$V_{gs} = -\frac{V_{dm}}{2} \Rightarrow V_{out} = g_m R_D \cdot \frac{V_{dm}}{2} \Rightarrow$$

$$A_{dm} = \frac{V_{out-dm}}{V_{dm}} = \frac{g_m R_D}{2} = \underline{\underline{40ggr}}$$

CM :  $U_{dm} = 0$

(4)

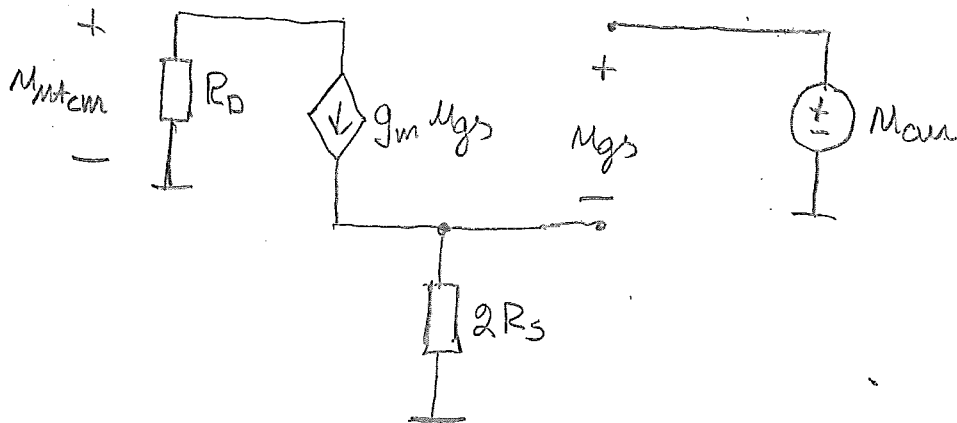

$$U_{utcm} = -g_m U_{gs} \cdot R_D$$

$$U_{cm} = U_{gs} + g_m U_{gs} \cdot 2R_s = (1 + 2g_m R_s) \cdot U_{gs} \Rightarrow$$

$$U_{utcm} = - \frac{g_m R_D}{1 + 2g_m R_s} \cdot U_{cm} \Rightarrow$$


$$A_{cm} = \frac{U_{utcm}}{U_{cm}} = - \frac{g_m R_D}{1 + 2g_m R_s} = -0,729 \Rightarrow$$

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \underline{\underline{54,9 \text{ ggr}}} = \underline{\underline{34,8 \text{ dB}}}$$

---

4

5

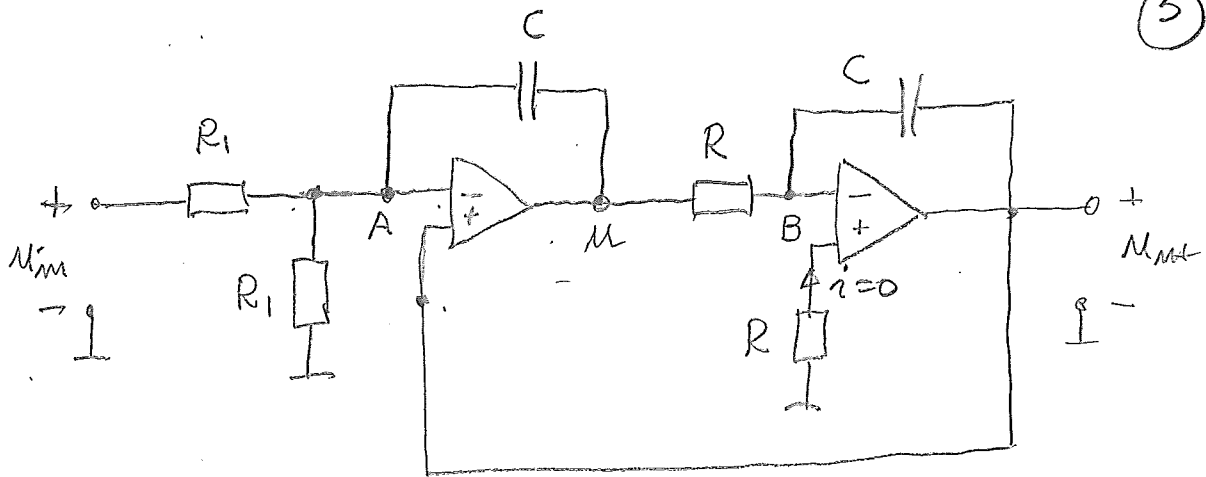

Ideala matkopplade OP  $\Rightarrow$   $\cdot$  inströmmar  $= 0$   
 $\cdot$  lika potential på ingångarna.

$$\Rightarrow U_A = U_{Mst} \quad ; \quad U_B = 0$$

Nodanalys:

$$\underline{A} \quad \frac{U_A - U_{in}}{R_1} + \frac{U_A}{R_1} + \frac{U_A - U}{1/sC} = 0 \quad ; \quad U_A = U_{Mst} \Rightarrow$$

$$(2 + sR_1C) \cdot U_{Mst} = sR_1C \cdot U + U_{in} \quad (1)$$

$$\underline{B} \quad \frac{U_B - U}{R} + \frac{U_B - U_{Mst}}{1/sC} = 0 \quad ; \quad U_B = 0 \Rightarrow$$

$$U = -sRC \cdot U_{Mst} \quad (2) \quad ; \quad \text{sätt in i (1)}$$

$$(2 + sRC) \cdot U_{Mst} = -s^2 R R_1 C^2 \cdot U_{Mst} + U_{in} \Rightarrow$$

$$\frac{U_{Mst}}{U_{in}} = \frac{1}{s^2 R R_1 C^2 + sRC + 2} = \frac{1}{R R_1 C^2} \cdot \frac{1}{s^2 + \frac{1}{RC} s + \frac{2}{R R_1 C^2}}$$

$$\text{Polar: } s^2 + \frac{1}{RC} s + \frac{2}{R R_1 C^2} = 0 \Rightarrow$$

$$s = -\frac{1}{2RC} \pm \sqrt{\frac{1}{4R^2C^2} - \frac{2}{R R_1 C^2}}$$

Maximalt snabbt utan översväng  $\Rightarrow$

(6)

$$\frac{1}{4R^2C^2} = \frac{2}{RR_1C^2} \Rightarrow R_1 = 8R = \underline{\underline{80k\Omega}}$$

Då gäller att

$$\frac{M_{\max}}{M_{\min}} = \frac{1}{RR_1C^2} \cdot \frac{1}{\left(s + \frac{1}{2RC}\right)^2} = 56,6 \cdot 10^6 \cdot \frac{1}{(s + 10638)^2} =$$

$$= \frac{0,5}{\left(1 + \frac{s}{10638}\right)^2} \cdot \text{Dubbelpol } s = -10638 \Rightarrow$$

$$\omega_{\text{TOT}} = 10638 \text{ rad/s} \cdot \sqrt{2^{1/2} - 1} = 6847 \text{ rad/s} \Rightarrow$$

$$\text{Övre gränshfrekvens } f_0 = \frac{6847}{2\pi} \text{ Hz} = 1089,7 \text{ Hz}$$

$$\Rightarrow \text{Stigtiden } t_r = \frac{0,35}{f_0} = \underline{\underline{0,32 \text{ ms}}}$$

---

5

$$R_L = 4\Omega ; E = 12V$$

$$P_L = R_L \cdot \frac{\hat{i}^2}{2} \Rightarrow$$

$$\hat{i} = \sqrt{\frac{2P_L}{R_L}} =$$


$$= \sqrt{\frac{2 \cdot 10W}{4\Omega}} = \underline{2,24A}$$

$$\Rightarrow \overline{i_1} = 2,24A \Rightarrow$$

$$P_{in} = 2P_E = 2 \cdot E \cdot \overline{i_1} = 2 \cdot 12V \cdot \frac{2,24A}{\pi} = \underline{17,08W} \Rightarrow$$

$$\eta = \frac{P_L}{P_{in}} = 0,585 = \underline{58,5\%}$$

7

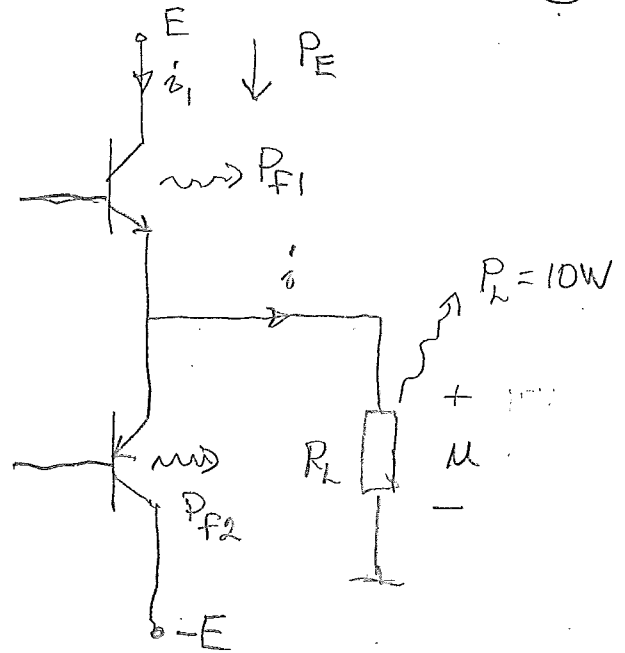


Transistorförlusterna  $P_F = P_{F1} + P_{F2} = P_{in} - P_L = \underline{7,08W}$

Maximal effekt i  $R_L$  erhålls då transistorerna  
bottnar, dvs då  $u_{ce1min} = u_{ce2min} = 0$ .


Då gäller att  $\hat{u} = E = 12V$ , vilket ger

$$P_{Lmax} = \frac{\frac{\hat{u}^2}{2}}{R_L} = \frac{E^2}{2R_L} = \frac{(12V)^2}{2 \cdot 4\Omega} = \underline{18W}$$

6a) Small signal scheme

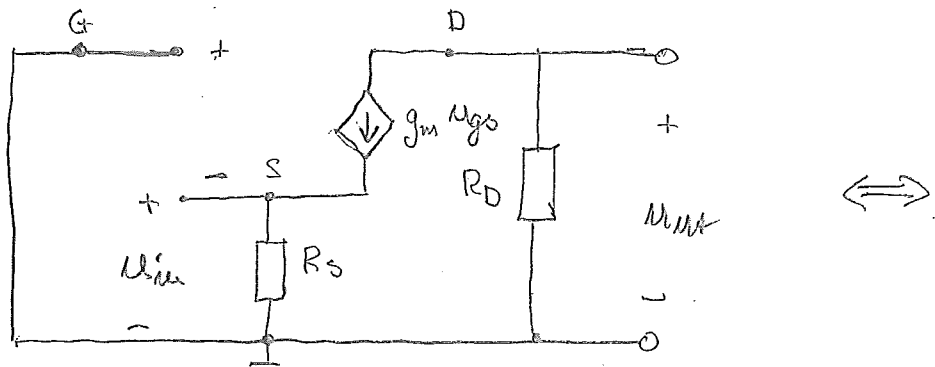

$\frac{U_{out}}{U_{in}}$

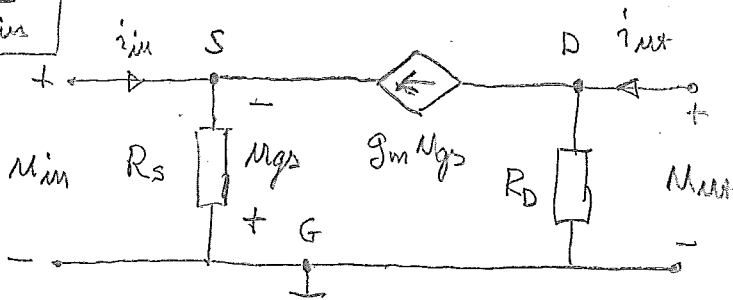

$R_s = 3,36 \Omega$   
 $R_D = 4,76 \Omega$   
 $g_m = 10 \text{ mA/V}$

$U_{out} = -g_m U_{gs} \cdot R_D$  ;  $U_{gs} = -U_{in} \Rightarrow$

$U_{out} = g_m R_D \cdot U_{in} \Rightarrow \frac{U_{out}}{U_{in}} = g_m R_D = \underline{\underline{47,99}}$

$R_{in} \quad R_{in} = \frac{U_{in}}{i_{in}} \Big|_{i_{out} = 0}$

$U_{in} = R_s \cdot (i_{in} + g_m U_{gs})$  ;  $U_{gs} = -U_{in} \Rightarrow$


$U_{in} = R_s \cdot i_{in} - R_s \cdot g_m U_{in} \Rightarrow$

$R_{in} = \frac{U_{in}}{i_{in}} = \frac{R_s}{1 + g_m R_s} = \underline{\underline{97,1 \Omega}}$



(6b.) Småsignal-schema

(9)

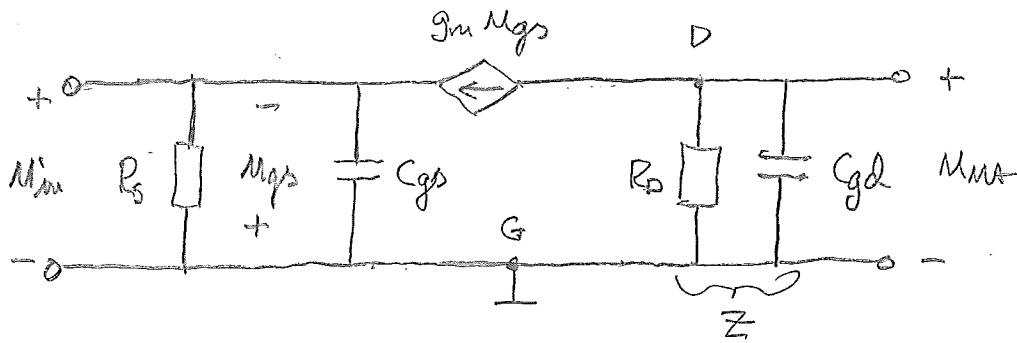

$$M_{ut} = -g_m M_{gs} \cdot Z \quad ; \quad M_{gs} = -M_{in} \quad \Rightarrow$$

$$M_{ut} = -g_m (-M_{in}) \cdot Z = g_m Z \cdot M_{in} \quad \Rightarrow$$

$$\frac{M_{ut}}{M_{in}} = g_m Z = g_m \cdot \frac{R_D \cdot \frac{1}{s C_{gd}}}{R_D + \frac{1}{s C_{gd}}} = \frac{g_m R_D}{1 + s R_D C_{gd}} =$$

$$= \frac{47}{1 + \frac{s}{53,2 \cdot 10^6}} \quad \Rightarrow$$

$$f_0 = \frac{53,2 \cdot 10^6}{2\pi} \text{ Hz} = \underline{\underline{8,47 \text{ MHz}}}$$