

①

09-01-13

a) Varaktor
Varicap - kapacitans diod


b) Elektrolytkondensator

c) Drossel

d) $T_j - T_a = P_T \cdot \theta_{ja}$ där $\theta_{ja} = \theta_{jc} + \theta_{cs} + \theta_{sa}$
 $\theta_{jc} = 1^\circ\text{C/W}$, $\theta_{cs} = 0$, $\theta_{sa} = 2^\circ\text{C/W}$, $T_{j\max} = 175^\circ$
 $T_a = 40^\circ$

$$\underline{P_{T\max}} = \frac{175 - 40}{1 + 2} = \underline{4.5 \text{ Watt}}$$

e)

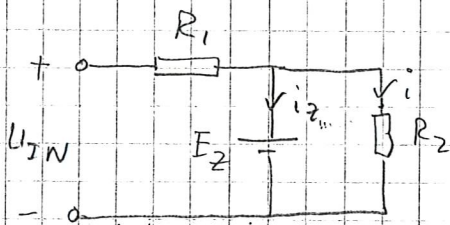

$$U_{IN\max} \Rightarrow i_{Z\max} \Rightarrow P_{Z\max}$$

$$U_{IN\max} = (i + i_{Z\max}) \cdot R_1 + E_Z$$

$$i = E_Z / R_2$$

$$i_{Z\max} = \left[U_{IN\max} - E_Z - \frac{E_Z \cdot R_1}{R_2} \right] / R_1 =$$

$$= \left[12 - 6 - 6 \cdot \frac{20}{80} \right] / 20 = 200 \text{ mA}$$

$$\therefore \underline{P_{Z\max}} = E_Z \cdot i_{Z\max} = 6 \cdot 0.2 = \underline{1.2 \text{ W}}$$

f)

$$P_{\text{Bott}} = 2 \cdot P_T + P_{R_L}; \quad i(t) = 1.2 \cdot \sin \omega t, \quad E = 15 \text{ V}$$

$$R_L = 10 \Omega$$


$$P_{\text{Batt}} = 2 \cdot E \cdot \frac{I}{\pi} \approx 11.46 \text{ W}$$

$$P_{R_L} = \frac{I^2 \cdot R_L}{2} = 7.2 \text{ W}$$

Varje transistors effekt $\underline{P_T} = \frac{11.5 - 7.2}{2} \approx \underline{2.13 \text{ Watt}}$

2

09-01-13

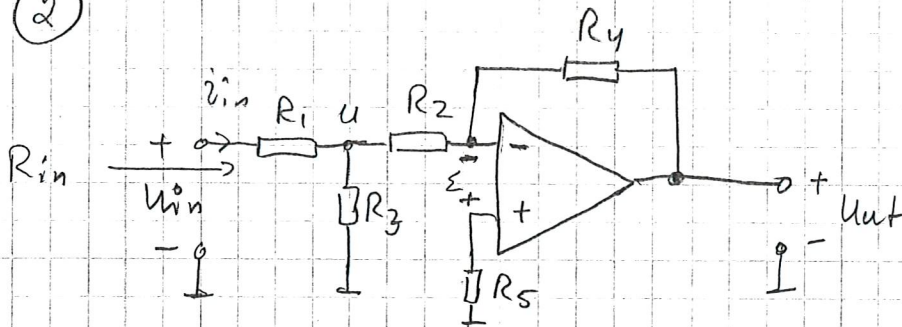

Neg återkoppl. } $\Sigma = 0$
 Ideal op-amp }

$$i_{op} = 0 \Rightarrow u^- = u^+ = 0$$

$$\frac{u_{in} - u}{R_1} + \frac{-u}{R_3} + \frac{-u}{R_2} = 0 \Rightarrow \frac{u_{in}}{R_1} = u \frac{R_2 \cdot R_3 + R_1 \cdot R_2 + R_1 \cdot R_3}{R_1 \cdot R_2 \cdot R_3}$$


$$\frac{u}{R_2} + \frac{u_{out}}{R_4} = 0 \Rightarrow \frac{u_{out}}{u} = - \frac{R_4}{R_2}$$

$$\therefore \frac{u_{out}}{u_{in}} = - \frac{R_4}{R_2} \cdot \frac{R_2 \cdot R_3}{R_2 \cdot R_3 + R_1 \cdot R_2 + R_1 \cdot R_3} = \underline{\underline{- \frac{R_3 \cdot R_4}{R_2 \cdot R_3 + R_1 \cdot R_2 + R_1 \cdot R_3}}}$$

$$\underline{\underline{R_{in}}} = \frac{u_{in}}{i_{in}} = R_1 + \underline{\underline{\frac{R_2 \cdot R_3}{R_2 + R_3}}}$$

③ OP amp $\begin{cases} F = \frac{200.000}{1+s/30} = \frac{F_0}{1+s/w_1} \\ R_{in} = \infty ; R_{ut} = 0 \end{cases}$

09-01-13

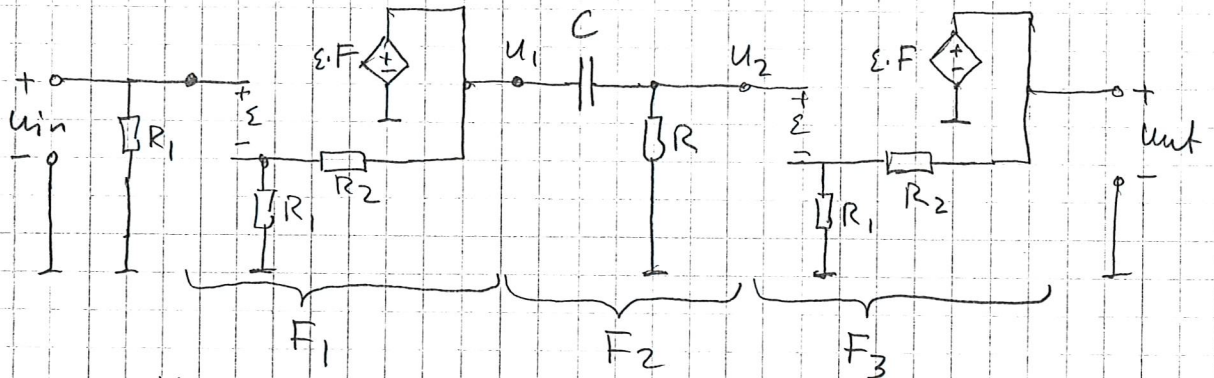


$F_1 = F_3 = \frac{U_1}{U_{in}}$; $U_{in} = \varepsilon + \varepsilon \cdot F \cdot \frac{R_1}{R_1 + R_2}$; $U_1 = \varepsilon \cdot F$

$F_1 = F_3 = \frac{F}{1 + \frac{R_1}{R_1 + R_2} \cdot F} = \frac{F_0}{1 + s/w_1 + \beta \cdot F_0} = \frac{F_0}{1 + \beta \cdot F_0} \cdot \frac{1}{1 + s/w_1 \cdot (1 + \beta F_0)}$

$F_2 = \frac{U_2}{U_1} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} = \frac{s/w_2}{1 + s/w_2}$

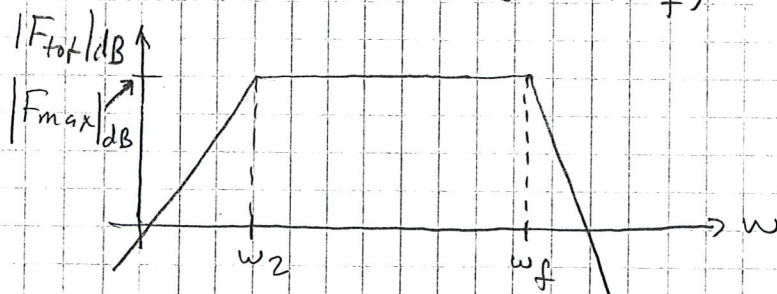$F_{tot} = F_1 \cdot F_2 \cdot F_3 = \left(\frac{F_{of}}{1 + s/w_f} \right)^2 \cdot \frac{s/w_2}{1 + s/w_2}$



$R_1 = 12k\Omega, R_2 = 100k\Omega$
 $R = 10k\Omega, C = 270nF$

$\underline{w_{0_{tot}}} = w_f \sqrt{2^{1/2} - 1} = 30 \left(1 + \frac{12k}{112k} \cdot 2 \cdot 10^5 \right) \cdot \sqrt{2^{1/2} - 1} = 414k \text{ rad/s}$


$\underline{w_u} = w_2 = \frac{1}{RC} = \underline{370 \text{ rad/sek}}$

$F_{max} = F_{of}^2 \cdot 1$ for $w_2 \ll w \ll w_f$

$\underline{F_{max}} = \left(\frac{2 \cdot 10^5}{1 + \frac{12k}{112k} \cdot 2 \cdot 10^5} \right)^2 \approx \underline{8799}$

4

09-01-13

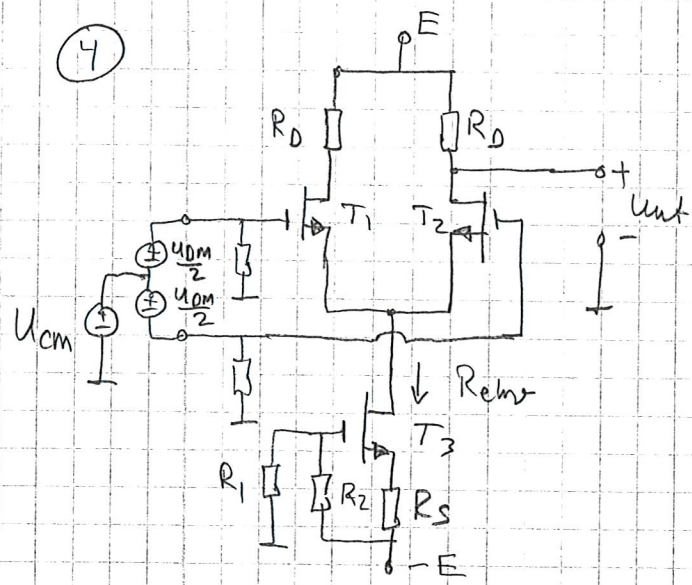

$$CMRR = \left| \frac{F_{DM}}{F_{CM}} \right|$$


$$R_D = 6.8 k\Omega \quad R_S = 1.4 k\Omega$$

$$g_m = 3 \text{ mA/V} \quad (T_1, T_2)$$

$$g_{m3} = 5 \text{ mA/V} \quad (T_3)$$

$$r_{o3} = 30 k\Omega \quad (T_3)$$

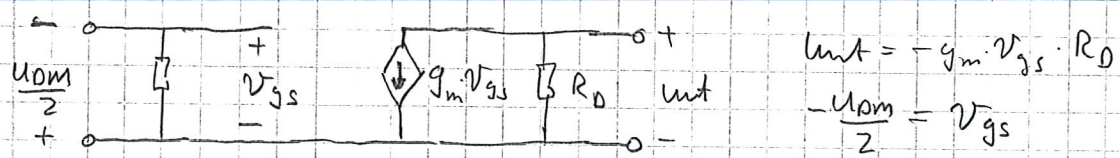F_{DM}: $U_{cm} = 0$, Source $T_1, T_2 =$ virtual jord.




$$U_{out} = -g_m \cdot V_{gs} \cdot R_D$$

$$-\frac{u_{om}}{2} = V_{gs}$$

$$F_{DM} = \frac{U_{out}}{u_{om}} = \frac{g_m \cdot R_D}{2} = \frac{3 \text{ mA/V} \cdot 6.8 k\Omega}{2} = 10.2 \text{ ggr}$$

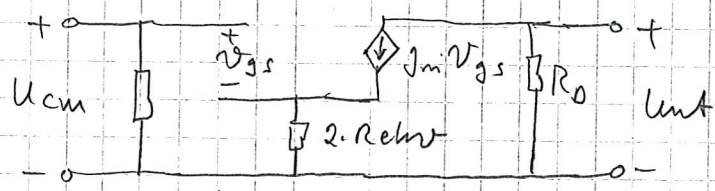
F_{CM}: $U_{om} = 0$ Source T_1, T_2 ser Rehrv in drain T_3



$$U_{out} = -g_m \cdot V_{gs} \cdot R_D$$

$$U_{cm} = V_{gs} + g_m \cdot V_{gs} \cdot 2 \text{ Rehrv}$$
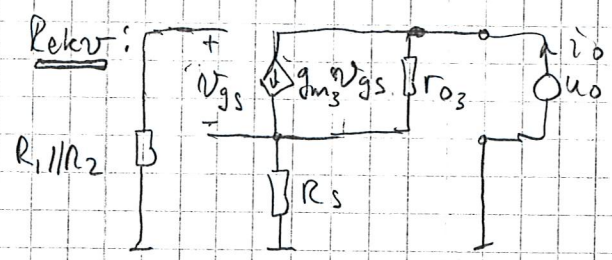
$$F_{CM} = \frac{U_{out}}{U_{cm}} = \frac{-g_m \cdot R_D}{1 + g_m \cdot 2 \cdot \text{Rehrv}}$$



$$U_o = (i_o - g_{m3} \cdot V_{gs}) r_{o3} + i_o \cdot R_S$$

$$-V_{gs} = i_o \cdot R_S$$

$$\text{Rehrv} = \frac{U_o}{i_o} = (1 + g_{m3} \cdot R_S) r_{o3} + R_S =$$

$$= 180 k\Omega$$

$$F_{CM} \approx -18.8 \cdot 10^{-3} \text{ ggr}$$

$$\underline{CMRR} = \frac{10.2}{18.8 \cdot 10^{-3}} \approx \underline{543 \text{ ggr}} \Rightarrow \underline{54.7 \text{ dB}}$$


⑤ Små signalschema: Mellamfrekvens:

09-01-13

Antag C_{gs}, C_{gd}, C_b är avbrutt (ip.F)

C_s och C är kortslutna (μF)

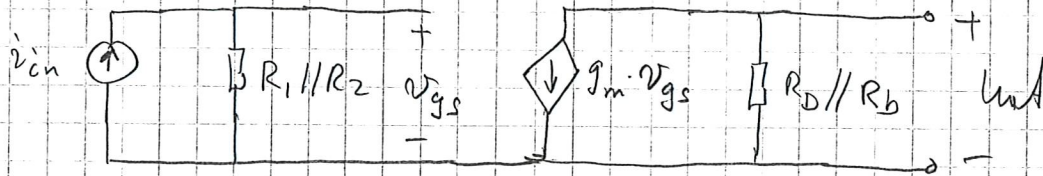$R_s = 12k, R_D = 4.7k, R_1 = 33k, R_2 = 10k, R_b = 3.9k$



$k = 10 \text{ mA/V}^2$
 $V_t = 1.5 \text{ V}$


$V_{gs} = i_{in} \cdot R_1 // R_2$

$U_{out} = -g_m \cdot V_{gs} \cdot R_D // R_b$

$\frac{U_{out}}{i_{in}} = -g_m \cdot R_1 // R_2 \cdot R_D // R_b$

$I_m?$ $g_m = \sqrt{2 \cdot k \cdot I_D}$ Bestäm I_D

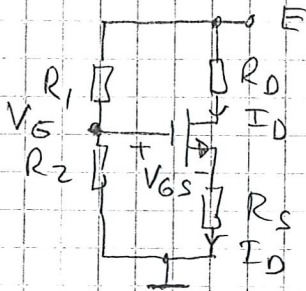Storsignalschema: Antag C_s, C avbrutt; $i_{in} = 0$



$I_D = \frac{k}{2} (V_{GS} - V_t)^2 = \frac{V_G - V_{GS}}{R_s}$

$V_{GS}^2 + \left(\frac{2}{k \cdot R_s} + 2 \cdot V_t \right) V_{GS} + V_t^2 - \frac{2 \cdot V_G}{k \cdot R_s} = 0$

$E = 15 \text{ V}$

$V_G = \frac{E \cdot R_2}{R_1 + R_2} = \frac{15 \cdot 10k}{33k + 10k} \approx 3.5 \text{ Volt}$

$V_{GS}^2 + \left(\frac{2}{10m \cdot 12k} + 2 \cdot 1.5 \right) V_{GS} + 1.5^2 - \frac{2 \cdot 3.5}{10m \cdot 12k} = 0$

$V_{GS}^2 - 2.83 V_{GS} + 1.67 = 0$ $V_{GS} = 1.42 \pm \sqrt{1.42^2 - 1.67} = (0.831)$


$\therefore I_D = \frac{10m}{2} (2 - 1.5)^2 = 1.25 \text{ mA}$

$g_m = \sqrt{2 \cdot 10m \cdot 1.25m} = 5 \text{ mA/V}$

$\frac{U_{out}}{i_{in}} = -5m \cdot \frac{33k \cdot 10k}{43k} \cdot \frac{4.7k \cdot 3.9k}{4.7k + 3.9k} \approx -82 \text{ kV/A}$

⑥

09-01-13

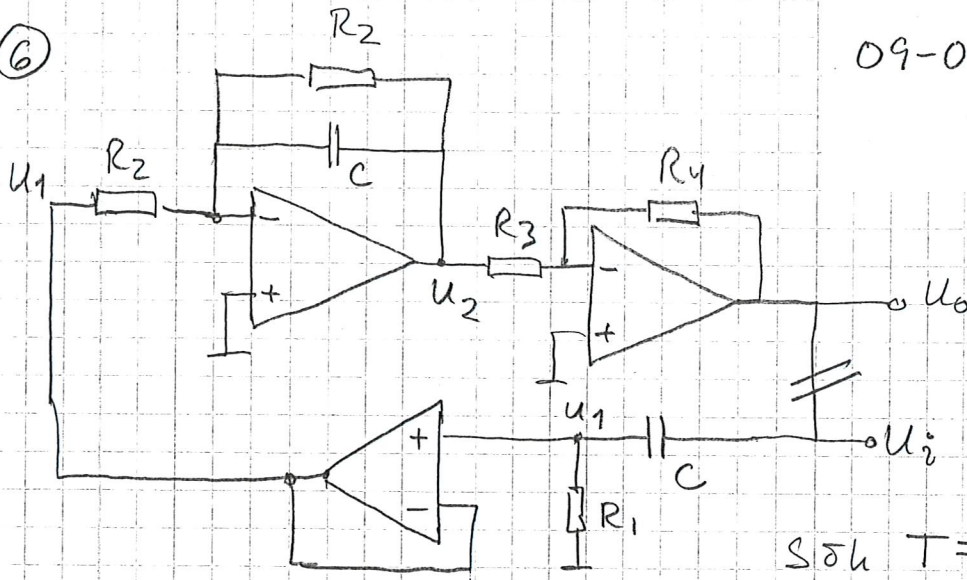

$C = 15 \text{ nF}$
 $R_1 = 5 \text{ k}\Omega$
 $R_2 = 20 \text{ k}\Omega$
 $R_3 = 1 \text{ k}\Omega$

$s \text{ oh } T = \frac{u_o}{u_i}$

Ideale op-ampere } $\epsilon = 0$
 Neg. återkoppling }

$$u_1 = u_i \cdot \frac{R_1}{R_1 + 1/sC} = u_i \cdot \frac{sR_1C}{1 + sR_1C}$$

$$\frac{u_2}{u_1} = - \frac{R_2}{1 + sR_2C} \cdot \frac{1}{R_2}$$

$$\frac{u_o}{u_2} = - \frac{R_4}{R_3}$$

$$T = \frac{u_o}{u_i} \cdot \frac{u_2}{u_1} \cdot \frac{u_1}{u_i} = \frac{R_4}{R_3} \cdot \frac{1}{1 + sR_2C} \cdot \frac{sR_1C}{1 + sR_1C}$$

$$T = \frac{R_4}{R_3} \cdot \frac{sR_1C}{s^2R_1R_2C^2 + s(R_1 + R_2)C + 1}$$

$$T(j\omega) = \frac{R_4}{R_3} \frac{j\omega_0 R_1 C}{-\omega_0^2 R_1 R_2 C^2 + j\omega_0 (R_1 + R_2) C + 1} = 1 \text{ for sinus-oscillation}$$

$\angle T$: $\text{Re}[\text{Nämnare}] = 0 \quad -\omega_0^2 R_1 R_2 C^2 + 1 = 0 \Rightarrow$

$|T|$: Svängningsfrekvens: $\omega_0 = \frac{1}{C\sqrt{R_1 R_2}} = \frac{1}{15 \text{ nF} \sqrt{5 \text{ k}\Omega \cdot 20 \text{ k}\Omega}} = 6.67 \text{ k rad/sek.}$

$f_0 = \frac{\omega_0}{2\pi} = \underline{\underline{1.060 \text{ kHz}}}$

$$\frac{R_4}{R_3} \cdot \frac{j\omega_0 R_1 C}{j\omega_0 (R_1 + R_2) C} = 1 \Rightarrow R_4 = \frac{(R_1 + R_2) \cdot R_3}{R_1} = \frac{5 \text{ k} + 20 \text{ k}}{5 \text{ k}} \cdot 1 \text{ k}$$

$R_4 = \underline{\underline{5 \text{ k}\Omega}}$