
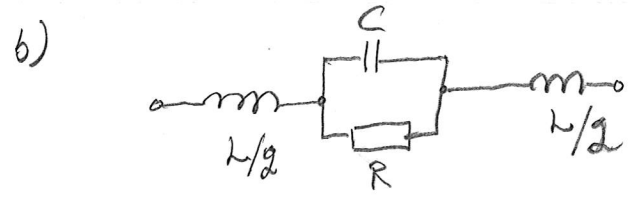


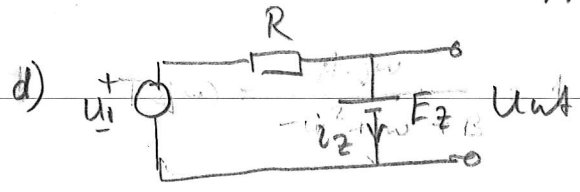- 1 a) • stabil kapacitans  
 • Polykarbonat, Polystyren, Polypropen



L: induktans i tilldelningar  
 R: Läderresistans  
 C: Nominell kapacitans


- c) • spärra oönskade högfrekventa störningar  
 • filter  
 • switchade nät aggregat



$$U_{1min} = E_2 = 10V$$

$$P_{2max} = E_2 \cdot i_{2max} \Rightarrow i_{2max} = \frac{0,5}{10} = 50mA$$
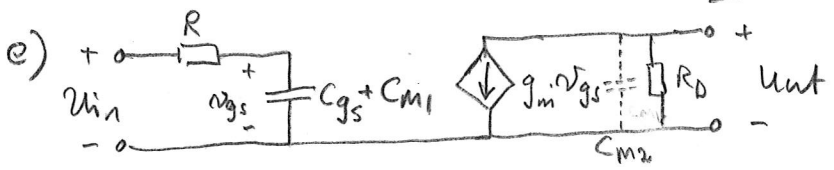
$$U_{1max} = R \cdot i_{2max} + E_2 = 100 \cdot 50m + 10 = 15V$$



$g_m = 10mA/V$   
 $R_D = 10k\Omega$

$$C_{m1} = C_{gd}(1-k) ; C_{m1} = 1p \cdot 101 \approx 100p$$

$$k = -g_m R_D = -100$$

Inverkan av  $C_{m2}$  försummas vid beräkning av  $\omega_0$

$$\omega_0^n = \frac{1}{R(C_{gs} + C_{m1})} \approx 19,9 \text{ Mrad/s}$$


f)  $T(s=j\omega) = \frac{A \cdot j\omega_0}{- \omega^2 + j\omega_0 + B} = 1$  för sinusformad självsväng.

$$B = \omega_0^2 = (2\pi \cdot f_0)^2 = (2\pi \cdot 1k)^2 \approx 39,5 \cdot 10^6 \left(\frac{rad}{s}\right)^2$$

$$A \approx 1$$

Even...  
 stor...

②

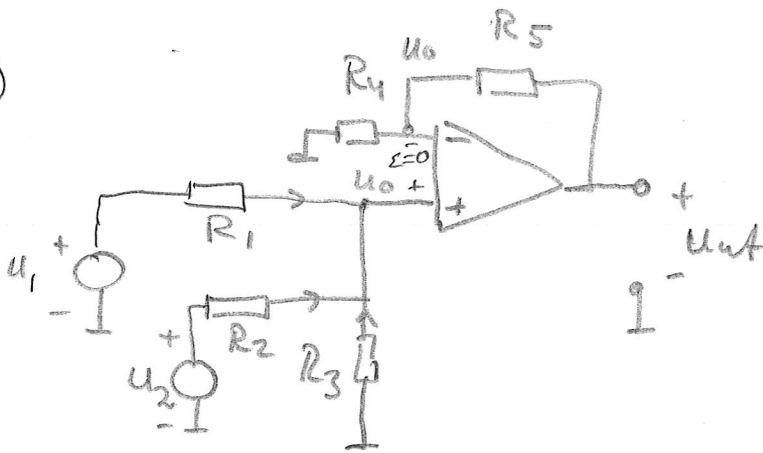

$$\begin{aligned} R_1 &= 1k = R \\ R_2 &= 2k = 2R \\ R_3 &= 2k = 2R \\ R_4 &= 1k = R \\ R_5 &= 3k = 3R \end{aligned}$$

Ideal op-amp  
neg iterkoppling }  $\epsilon = 0$


$$\frac{U_2 - U_0}{R_2} + \frac{0 - U_0}{R_3} + \frac{U_1 - U_0}{R_1} = 0 \Rightarrow \frac{U_2}{2R} + \frac{U_1}{R} = U_0 \left( \frac{1}{2R} + \frac{1}{2R} + \frac{1}{R} \right)$$

$$\frac{-U_0}{R_4} + \frac{U_{out} - U_0}{R_5} = 0 \Rightarrow \frac{U_{out}}{3R} = U_0 \cdot \left( \frac{1}{R} + \frac{1}{3R} \right) \Rightarrow U_{out} = U_0 \cdot 4$$

$$\therefore \frac{U_2}{2} + U_1 = \frac{U_{out}}{4} \quad (2)$$

$$\therefore \boxed{U_{out} = U_2 + 2U_1}$$

③

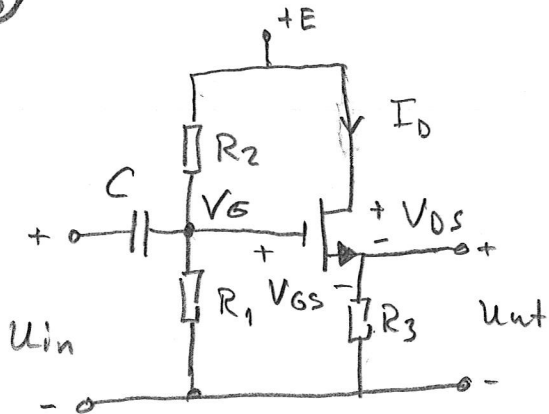

$$I_D = 4 \text{ mA}, \quad k = 2 \text{ mA/V}^2, \quad V_t = 1 \text{ V}$$

$$E = 16 \text{ Volt}$$

Maximalt utstyringsområde  $\Rightarrow$

$$V_{DS} = \frac{E}{2} = 8 \text{ Volt}$$

$$V_{R_3} = E - V_{DS} = 8 \text{ volt} \Rightarrow R_3 = \frac{V_{R_3}}{I_D} = \frac{8}{4 \text{ mA}} = \underline{\underline{2 \text{ k}\Omega}}$$

$$I_D = \frac{k}{2} \cdot (V_{GS} - V_t)^2 \Rightarrow V_{GS} = \sqrt{\frac{2 I_D}{k}} + V_t = \sqrt{\frac{2 \cdot 4 \text{ mA}}{2}} + 1 = 3 \text{ Volt}$$


$$V_G = V_{R_3} + V_{GS} = \frac{E \cdot R_1}{R_1 + R_2} \quad ; \quad 11 = 16 \cdot \frac{R_1}{R_1 + R_2}$$

Välj  $R_1 = \underline{\underline{100 \text{ k}\Omega}}$  (10k-10M  $\Omega$  ok)

$$11(R_1 + R_2) = 16 \cdot R_1 \Rightarrow R_2 = \frac{5 \cdot R_1}{11} \approx 50 \text{ k}\Omega$$

4

181012-4

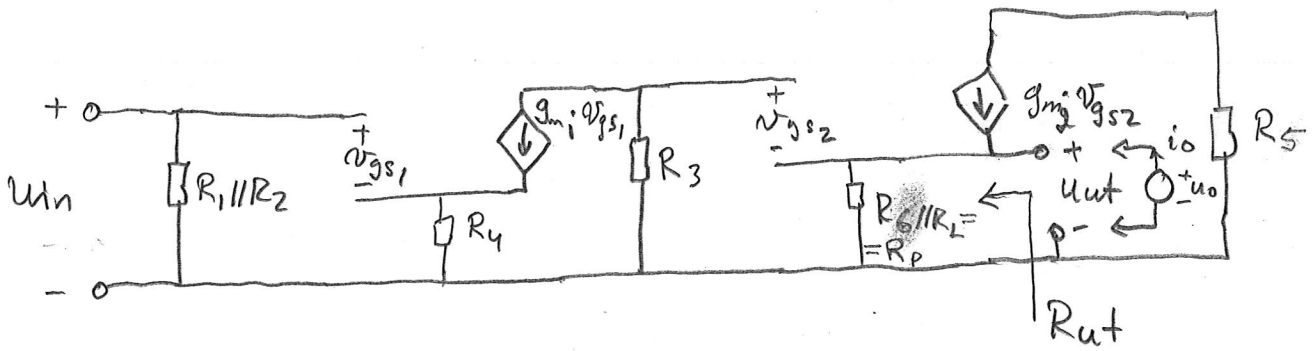

$$U_{in} = v_{gs1} + g_{m1} \cdot v_{gs1} \cdot R_4 = (1 + g_{m1} \cdot R_4) v_{gs1}$$


$$-g_{m1} \cdot v_{gs1} \cdot R_3 = (1 + g_{m2} \cdot R_p) v_{gs2}$$

$$U_{out} = g_{m2} \cdot v_{gs2} \cdot R_p$$

$$\frac{U_{out}}{U_{in}} = \frac{-g_{m2} \cdot R_p}{1 + g_{m2} \cdot R_p} \cdot \frac{g_{m1} \cdot R_3}{1 + g_{m1} \cdot R_4}$$

( $\approx \frac{R_3}{R_4}$  da  $g_{m2} \cdot R_5 \gg 1$   
 $g_{m1} \cdot R_4 \gg 1$ )

$$R_{out} = \frac{U_o}{i_o} \Big|_{U_{in}=0}$$

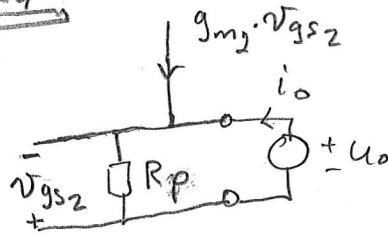


$$\begin{aligned} U_{out} &= -v_{gs2} \\ U_{out} &= (i_o + g_{m2} \cdot v_{gs2}) \cdot R_p \end{aligned} \parallel$$

$$U_{out} (1 + g_{m2} \cdot R_5) = i_o \cdot R_p$$

$$\therefore R_{out} = \frac{R_p}{1 + g_{m2} \cdot R_p} \left( \approx \frac{1}{g_{m2}} \text{ da } g_{m2} \cdot R_p \gg 1 \right)$$

$$R_{in} = R_1 \parallel R_2$$

5

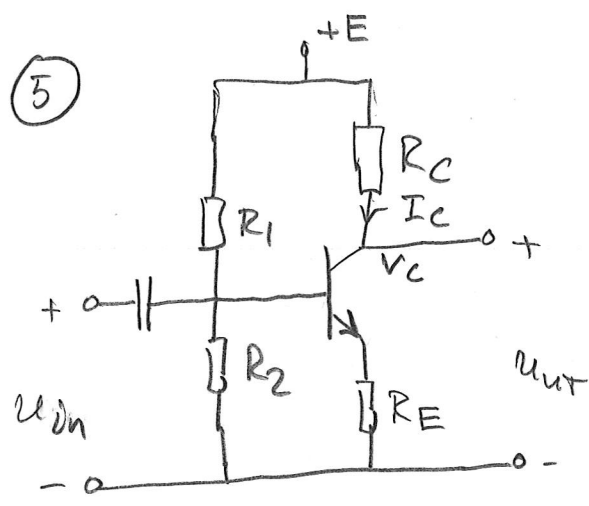

$E = 18V, V_C = 13V$   
 $R_1 = 2.4k\Omega, R_2 = 200\Omega, R_C = 100\Omega$   
 $R_E = 10\Omega$


a)  $I_C = \frac{E - V_C}{R_C} = \frac{18 - 13}{100} = 50mA$

$V_{CE} = E - I_C \cdot (R_C + R_E) = 18 - 0.05(110) = 12.5V$

$P_T = V_{CE} \cdot I_C = 625mW$

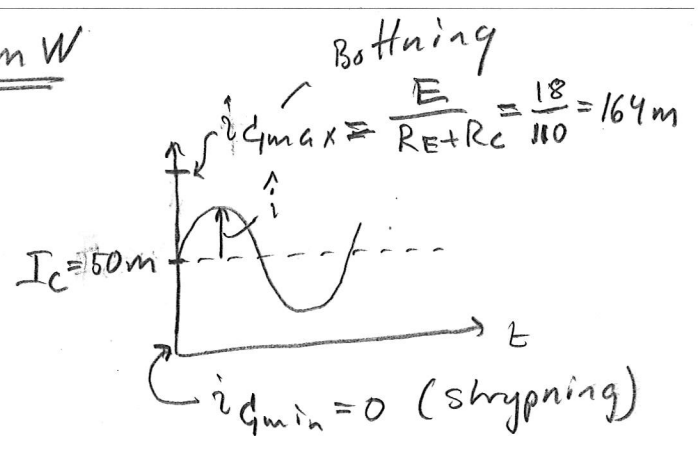b)  $\hat{i}_{max} = 50mA$  for maximal dynamik


$P_{RC_{max}} = \frac{\hat{i}_{max}^2 \cdot R_C}{2} = 125mW$






c) 
$$P_T = \frac{1}{T} \int_0^T [V_{CE} - \hat{i}_{max} \cdot (R_C + R_E) \sin \omega t] \cdot (I_C + \hat{i}_{max} \sin \omega t) dt =$$

$$= V_{CE} \cdot I_C - \frac{\hat{i}_{max}^2 \cdot (R_C + R_E)}{2} \approx \underline{\underline{487mW}}$$

6

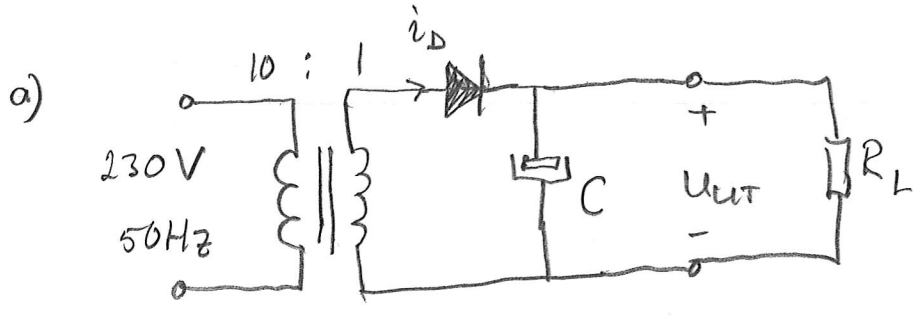

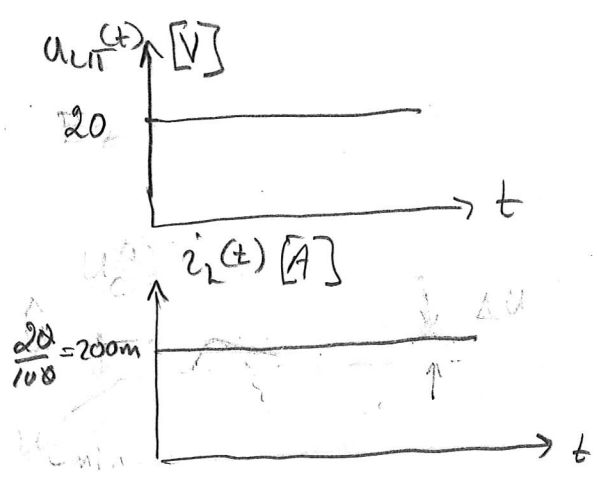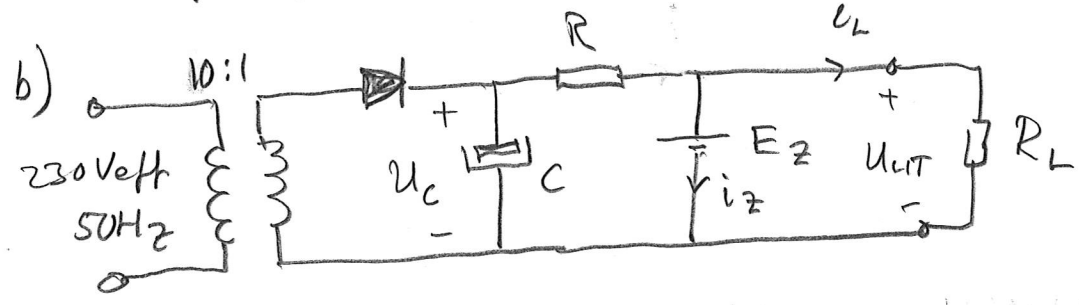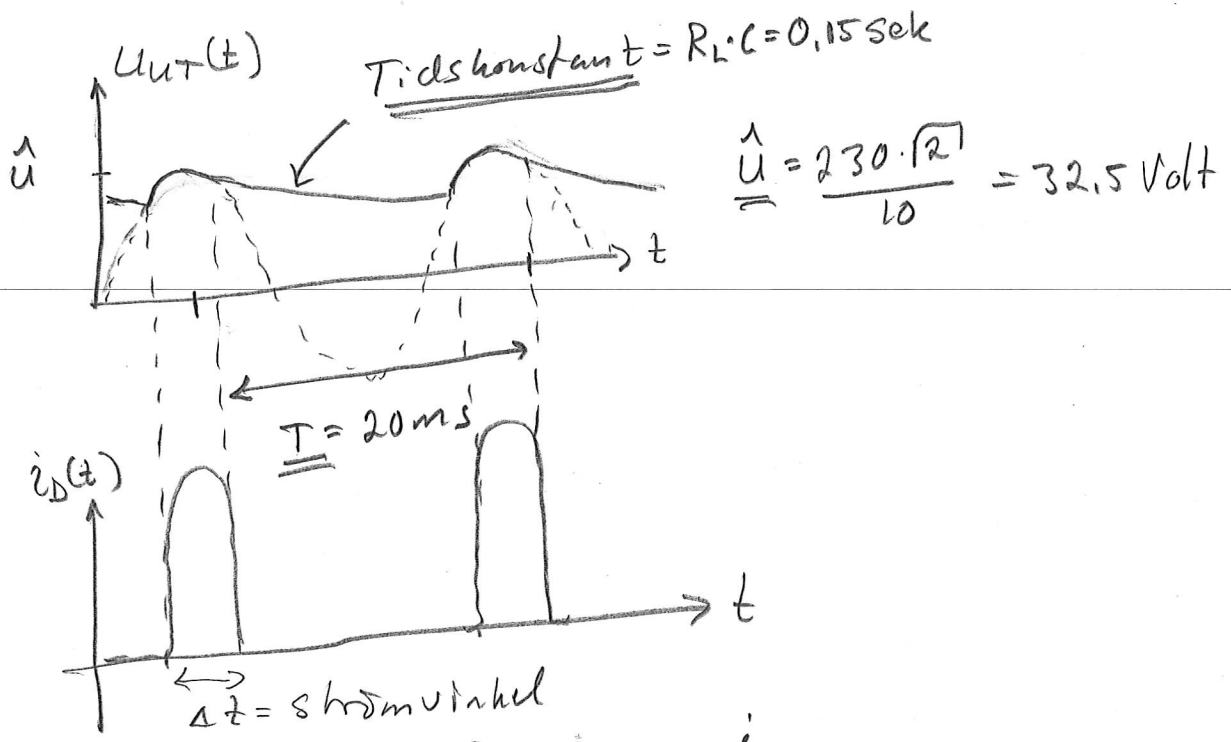$R_L = 100 \Omega$   
 $C = 1500 \mu F$   
 $E_z = 20 V$   
 $r_z = 0$



Med Zener  $U_z = 20 \text{ Volt}$

$U_{out} = E_z = 20 \text{ V}$

$U_{omsp} = R_{omsp} \cdot i_D + E_z = 20 \text{ Volt}$

$i_D = 0$

$i_L = E_z / R_L = 200 \text{ mA}$

$R_{max} = \frac{U - \Delta U - E_z}{E_z / R_L} = \frac{32,5 - 4 - 20}{20/100} = 112,5 \Omega$

$R_{max} = 112,5 \Omega$