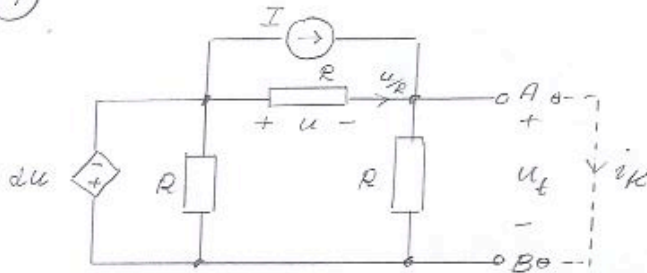


Elektriska kretsar för Z1 23/8 2005

①



Terräng:



KVL →

$$u + u_t + du = 0$$

$$\rightarrow u = -\frac{u_t}{d+1}$$

Ohms lag →  $u_t = R(I + \frac{u}{R}) = RI - \frac{u_t}{d+1} \rightarrow u_t = \frac{RI(d+1)}{d+2}$

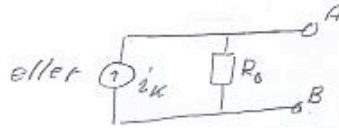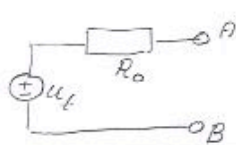
Kortslutning:  $u + du = 0 \rightarrow u = 0, i_k = I + \frac{u}{R} = I$



$$R_0 = \frac{u_t}{i_k} = \frac{R(d+1)}{d+2}$$

②  $u_0(t) = 4 \cos 3t \Rightarrow U_0 = 4 e^{j0^\circ}, \omega = 3, \omega(L_1 + L_2) = 6$

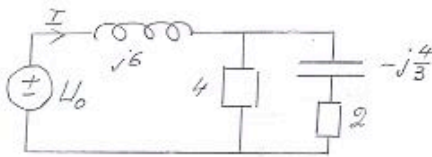$\frac{1}{\omega C} = \frac{4}{3}$ . Ekvivalent krets:



$$4 // (2 - j\frac{4}{3}) = \frac{4(2 - j\frac{4}{3})}{4 + 2 - j\frac{4}{3}} \approx$$


$$\approx \dots \approx 1.46 - j0.56$$

$$Z_{tot} = j6 + 1.46 - j0.56 = 1.46 + j5.44$$

$$I = \frac{U_0}{Z_{tot}} \approx 0.71 e^{-j75.1^\circ}$$

$$i(t) = \text{Re}\{I e^{j\omega t}\} = 0.71 \cos(3t - 75.1^\circ) \text{ A}$$

③ a)

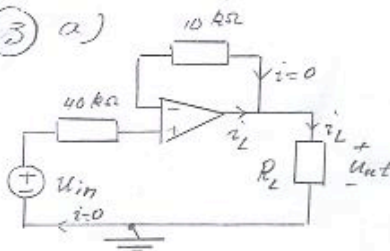

KVL →  $U_{in} = U_{out}$

Ohms lag →  $U_{out} = R_L i_L$


$$\therefore i_L = \frac{U_{out}}{R_L} = \frac{U_{in}}{R_L} = \frac{4}{2 \cdot 10^4} =$$

$$= 2 \cdot 10^{-4} \text{ A} \rightarrow P = R_L i_L^2 =$$

$$= \frac{U_{in}^2}{R_L} = \frac{16}{2 \cdot 10^4} = 8 \cdot 10^{-4} \text{ W}$$

Elektriska kretsar för Z1 23/8 2005

3) b)

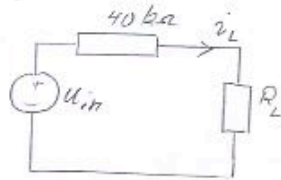

Ohms lag  $\rightarrow i_L = \frac{U_{in}}{R_L + 4 \cdot 10^4} =$   
 $= \frac{4}{6 \cdot 10^4} = \frac{2}{3} \cdot 10^{-4} \text{ A}$   
 $P_2 = R_L i_L^2 = \frac{8}{9} \cdot 10^{-4} \text{ W}; \frac{P_1}{P_2} = 9$

4) a)  $S_1 = P_1 + jQ_1 = 3 \cdot 10^3 + j4 \cdot 10^3$

$S_2 = P_2 + jQ_2 = 2 \cdot 2 \cdot 10^3 (\cos \varphi_2 + j \sin \varphi_2) =$   
 $[\cos \varphi_2 = 0.6; \sin \varphi_2 = \sqrt{1 - \cos^2 \varphi_2} = 0.8] = (1.32 + j1.76) 10^3$

$S_3 = P_3 = 1.5 \cdot 10^3$


$S_{tot} = S_1 + S_2 + S_3 = (3 + 1.32 + 1.5) 10^3 + j(4 + 1.76) 10^3 = \frac{P}{S_{tot}} + j \frac{Q}{S_{tot}}$

dar  $P_{tot} = 5.82 \text{ kW}, Q_{tot} = 5.76 \text{ kVAR}$


b)  $S_{tot} = \frac{1}{2} U_0 I^* = \frac{1}{2} U_0 \left( \frac{U_0}{Z_{tot}} \right)^* = \frac{1}{2} \frac{|U_0|^2}{Z_{tot}^*} \rightarrow Z_{tot}^* = \frac{|U_0|^2}{2 S_{tot}}$

$Z_{tot} = \frac{|U_0|^2}{2 S_{tot}^*} \approx \frac{(220 \sqrt{2})^2}{2 \cdot 5.8 \cdot 10^3 (1-j)} = \dots = \frac{121}{29} (1+j) \approx 4(1+j) \Omega$


5) a)  $|H_1| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_1})^2}}$   $\omega/\omega_1 \ll 1, |H_1| \approx 1, |H_1|_{dB} = 20 \log 1 = 0$   
 $\omega/\omega_1 \gg 1, |H_1| \approx \frac{1}{\omega/\omega_1}, |H_1|_{dB} = 20 \log \left( \frac{1}{\omega/\omega_1} \right)$

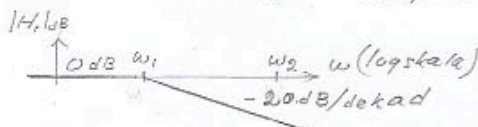

b)  $|H_2| = \frac{\omega/\omega_2}{\sqrt{1 + (\frac{\omega}{\omega_1})^2}}$   $\omega/\omega_1 \ll 1, |H_2| \approx \frac{\omega}{\omega_2}, |H_2|_{dB} = 20 \log \left( \frac{\omega}{\omega_2} \right)$   
 $\omega/\omega_1 \gg 1, |H_2| \approx \frac{\omega/\omega_2}{\omega/\omega_1}, |H_2|_{dB} = 20 \log 10^{-2} = -40$

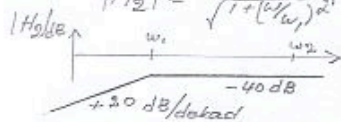

$|H_3| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_1})^2}}$   $\omega/\omega_1 \ll 1, |H_3| \approx 1, |H_3|_{dB} = 20 \log 1 = 0 \text{ dB}$

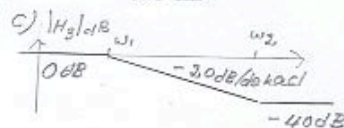

$\omega_1 \ll \omega \ll \omega_2, |H_3|_{dB} \approx 20 \log \frac{1}{\omega/\omega_1}$   
 $\omega/\omega_2 \gg 1, |H_3|_{dB} \approx 20 \log \frac{\omega/\omega_1}{\omega/\omega_2} = -40 \text{ dB}$   
 A.J.