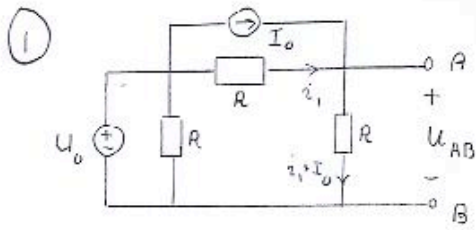


Elektriska kretsar för Z1, 10/1 2006




längd: kVL:

$$U_0 - Ri_1 - R(i_1 + I_0) = 0$$

$$i_1 = \frac{1}{2R}(U_0 - RI_0)$$


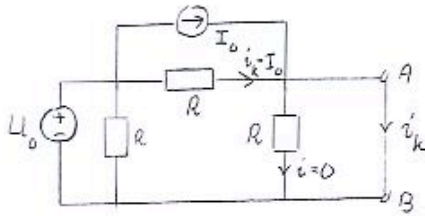
$$U_{AB} = Ri_1 + RI_0 = \frac{1}{2}(RI_0 + U_0)$$



kortslutning: kVL:

$$U_0 - R(i_k - I_0) = 0$$


$$i_k = \frac{1}{2}(RI_0 + U_0)$$

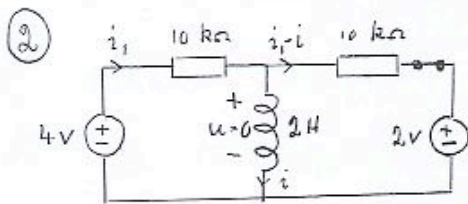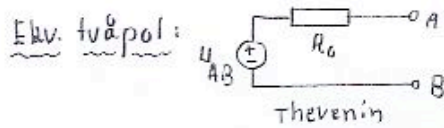

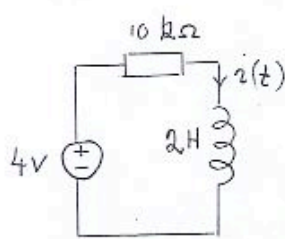a) $t=0$: kVL:

$$\begin{cases} 4 = 10^4 i \\ 2 = -10^4 (i_1 - i) \end{cases}$$

$$2 = -4 + 10^4 i \rightarrow i = 6 \cdot 10^{-4} \text{ A}$$



b) $t \geq 0$: kVL: $4 = 10^4 i + 2 \frac{di}{dt}$

Lösning till homogena ekv: $10^4 i_h = -2 \frac{di_h}{dt}$

$$i_h = C e^{-(10^4/2)t}, C = \text{integrationskonst.}$$

partikulär lösning: $i_p = \text{konst.} = 4 \cdot 10^{-4} \text{ A}$

$$i = i_h + i_p = C e^{-(10^4/2)t} + 4 \cdot 10^{-4}$$


Begynnelsevillkor:

$$i = 6 \cdot 10^{-4} \text{ A för } t=0 \rightarrow C + 4 \cdot 10^{-4} = 6 \cdot 10^{-4} \rightarrow C = 2 \cdot 10^{-4} \rightarrow$$

$$\rightarrow i = 2 \cdot 10^{-4} (2 + e^{-(10^4/2)t}) \text{ A}$$

Elektriska kretsar för Z1, 10/1 2006

3

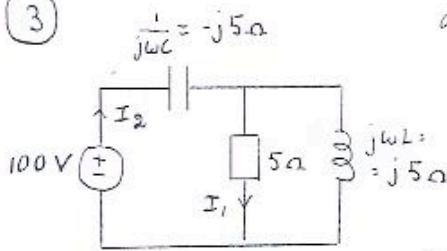


a) Ohms lag: $I_2 = \frac{100}{-j5 + \frac{j5 \cdot 5}{j5 + 5}} =$

$$= \frac{100}{5 - j5 + j5} = 20(1+j) \text{ A} = 20\sqrt{2} e^{j45^\circ} \text{ A}$$

Strömdelning: $I_1 = \frac{j5}{j5+5} I_2 = 20j = 20 e^{j90^\circ} \text{ A}$

b) $i_2 = \text{Re}(I_2 e^{j\omega t}) = 20\sqrt{2} \cos(100t + 45^\circ) \text{ A}$, $i_1 = \text{Re}(I_1 e^{j\omega t}) = 20 \cos(100t + 90^\circ) \text{ A}$

4

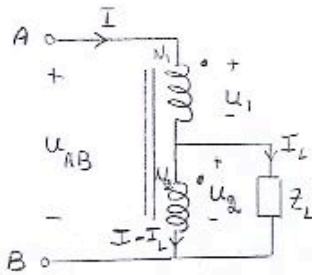


$$\frac{U_1}{U_2} = \frac{N_1}{N_2}, \quad \frac{I}{I_L} = -\frac{N_2}{N_1} \rightarrow I_L = \left(1 + \frac{N_1}{N_2}\right) I$$

$$U_{AB} = U_1 + U_2 = \left(1 + \frac{N_1}{N_2}\right) U_2 = \left(1 + \frac{N_1}{N_2}\right) I_L Z_L$$

$$= \left(1 + \frac{N_1}{N_2}\right) \left(1 + \frac{N_1}{N_2}\right) I Z_L$$

$$Z_{in} = \frac{U_{AB}}{I} = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L$$

5

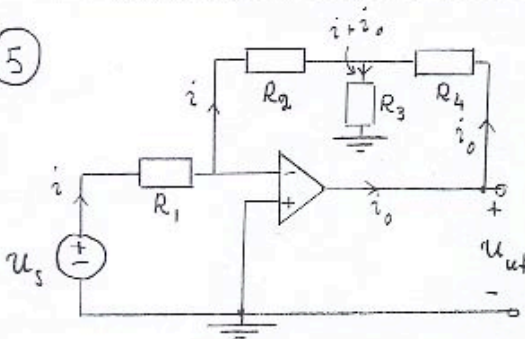

KVL: $U_{ut} - U_s + (R_1 + R_2) i - R_4 i_0 = 0$

$$U_s = R_1 i \rightarrow i = U_s / R_1$$

$$R_2 i + R_3 (i + i_0) = 0 \rightarrow$$

$$\rightarrow i_0 = -\frac{R_2 + R_3}{R_3} i =$$

$$= -\frac{R_2 + R_3}{R_1 R_3} U_s$$

$$\therefore U_{ut} - U_s + \frac{R_1 + R_2}{R_1} U_s + \frac{R_4 (R_2 + R_3)}{R_1 R_3} U_s = 0$$

$$\rightarrow \frac{U_{ut}}{U_s} = 1 - 1 - \frac{R_2}{R_1} - \frac{R_4 (R_2 + R_3)}{R_1 R_3} = -\frac{R_2 R_3 + R_4 R_2 + R_4 R_3}{R_1 R_3}$$

A.J.