

① a) $Z_2 = R_2 = |Z_1| = \underline{\underline{180 \Omega}}$

om Z_2 kan väljas fritt $\Rightarrow Z_2 = \bar{Z}_1 \Rightarrow$

strömmen ökar \Rightarrow effekten i R_2 ökar.

b) Gauss lagar $\Rightarrow \Phi_E = \Phi_{\text{inneslutat}} = -2 \text{ nC}$ negativ
 $\Phi_M = 0$ (alltid) flöde in i området

c) Slew rate & FB-produkt begränsar f_{max} :

$$SR > \left| \frac{dU_{\text{ut}}}{dt} \right|_{\text{max}} = 2\pi f_{\text{max}} \cdot |A_{\text{ul}}| \cdot \hat{u}_{\text{in}}$$


$$\rightarrow f_{\text{max}} < 127 \text{ kHz}$$

$$FB > |A_{\text{ul}}| \cdot f_{\text{max}} \Rightarrow f_{\text{max}} < 60 \text{ kHz}$$

$$\therefore f_{\text{max}} < \underline{\underline{60 \text{ kHz}}}$$

d) $B_{\text{max}} = \frac{\mu_0 I}{2\pi r_i} \quad \text{där} \quad I = \sqrt{\frac{S \cdot 2\pi r_y^2 \cdot \ln\left(\frac{r_y}{r_i}\right)}{R}} \approx 0,42306 \text{ A}$

$\approx 1,0610^{-4} \text{ T}$

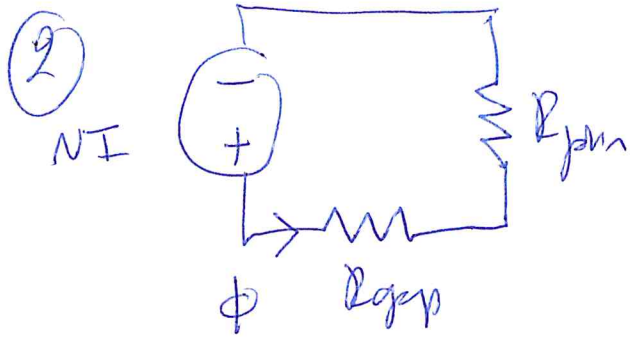


$$\left. \begin{aligned} B_{gpp} &= \frac{\Phi}{A} \\ NI &= R_{tot} \cdot \Phi \end{aligned} \right\} \Rightarrow B_{gpp} = \frac{NI}{A \cdot R_{tot}}$$

$$R_{tot} = R_{gpp} + R_{pnn} = \frac{l}{\mu_0 A} + \frac{\text{omkrets} - l}{\mu_0 \mu_{pnn} \cdot A} \approx 2,852 \cdot 10^6 \text{ 1/H}$$

$$\Rightarrow B_{gpp} \approx \underline{\underline{0,19 \text{ T}}} \quad \text{riktad} \rightarrow$$

③

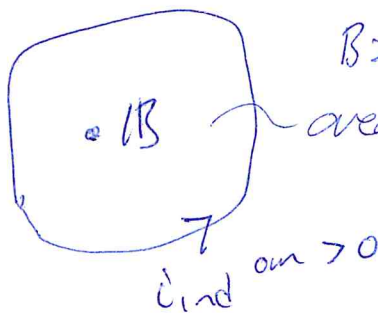

$B > 0 \Rightarrow \odot$

$$R_{slingor} = 20 \text{ } \Omega$$

area = $A = 0,04 \text{ m}^2$; $B = B_0 \cdot \sin^2 \omega t =$

$$= 0,02 \cdot \sin^2(10^3 t) \text{ tesla}$$

$$i_{ind} = \frac{U_{ind}}{R_{slingor}} = - \frac{A}{R_{slingor}} \frac{dB}{dt} = - \frac{AB_0 \omega}{R_{slingor}} 2 \sin \omega t \cos \omega t =$$

$$= - \frac{AB_0 \omega}{R_{slingor}} \cdot \sin(2\omega t)$$


$$\Rightarrow i_{ind \text{ min}} = \underline{\underline{0}}, \quad i_{ind \text{ max}} = \frac{AB_0 \omega}{R_{slingor}} = \underline{\underline{0,04 \text{ T}}}$$

Stämrikt. vid tiden för sig stammax. efter $t > 0$:

$$i_{ind \text{ max}} \text{ inträffar då } 2\omega t = \frac{\pi}{2} \Rightarrow t = \frac{\pi}{4\omega}$$

$$\Rightarrow i_{ind} = - \frac{AB_0 \omega}{R_{slingor}} < 0 \text{ vid denna tid} \Rightarrow i_{ind} \downarrow \text{ medans}$$

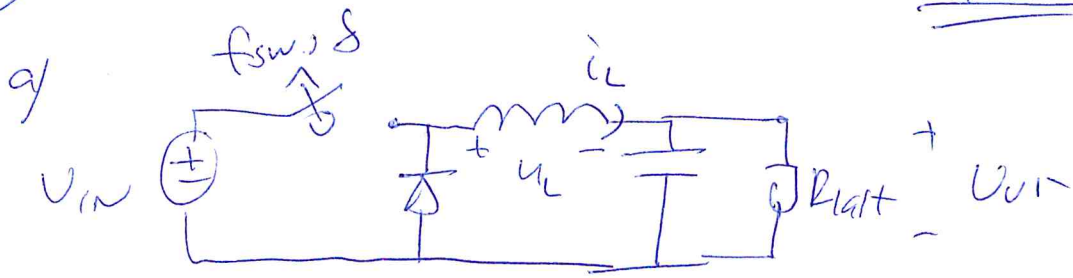④ $V_{in} = 20V$, $V_{out} = 12V \Rightarrow$ step down omv.



$u_L = V_{in} - V_{out}$ när brytaren i TILL-läge.


b) $i_{L,medel} = \frac{V_{out}}{R_{latt}} = 0,4 \text{ A}$

c) $\Delta i_L = \frac{u_L \cdot \delta \cdot T}{L} = \frac{(V_{in} - V_{out}) \cdot \delta \cdot T}{L} \approx 0,2909 \text{ A}$

↑
tex, TILL-läge

↑
 $\delta = \frac{V_{out}}{V_{in}} = 0,6$

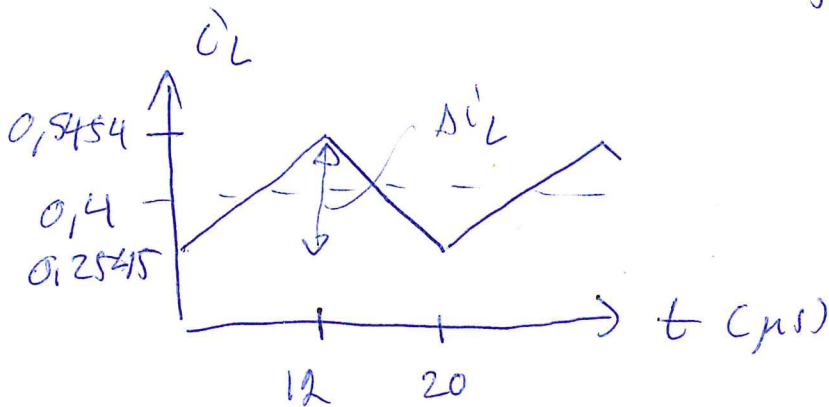$T = \frac{1}{f_{sw}} = 2 \cdot 10^{-5} \text{ s}$



Brytaren sluten $0 \rightarrow 12 \mu\text{s}$
 -| - öppen $12 \rightarrow 20 \mu\text{s}$


c) Tex. ESR hos kondensatorer, vill upp/urladat. av kond.

$$\textcircled{5} \quad a) \quad \sqrt{I_D} = \underbrace{\sqrt{\frac{\mu}{2}}}_{0,316} \cdot U_{GS} = \underbrace{\sqrt{\frac{\mu}{2}}}_{0,474} \cdot U_T$$

$$\Rightarrow \underline{\mu = 0,120 \text{ A/V}^2}, \quad \underline{U_T = 1,5 \text{ V}}$$

$$b) \quad \left. \begin{aligned} \frac{R_2}{R_1 + R_2} U_{DD} - U_{GS} - R_S I_{DQ} &= 0 \\ I_{DQ} &= \frac{\mu}{2} (U_{GS} - U_T)^2 = 9,468 \text{ A} \end{aligned} \right\} \Rightarrow \underline{R_2 = 82 \text{ k}\Omega}$$
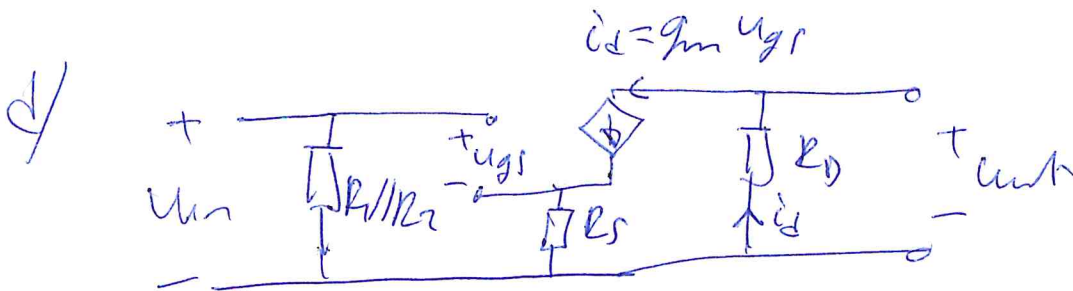
$$c) \quad P_{\text{transistor}} = U_{DSQ} \cdot I_{DQ} = (U_{DD} - R_D I_{DQ} - R_S I_{DQ}) \cdot I_{DQ} \\ \approx \underline{66 \text{ mW}}$$




$$R_{\text{out}} = R_D = \underline{330 \Omega}$$

$$e) \quad \left. \begin{aligned} u_{\text{out}} &= -g_m u_{gs} R_D \\ u_{\text{in}} &= u_{gs} + g_m u_{gs} R_S \end{aligned} \right\} \Rightarrow A_u = \frac{u_{\text{out}}}{u_{\text{in}}} = -\frac{g_m R_D}{1 + g_m R_S}$$

$$g_m = \mu (U_{GS} - U_T) = 812 \text{ A/V}$$

$$\Rightarrow A_u \approx 7,3 \text{ g\u00e4nger} \Rightarrow U_{ut} = A_u \cdot U_{in} = -2,19 \cdot \cos(2\pi \cdot 12 \cdot 10^3 t) \text{ Volt}$$
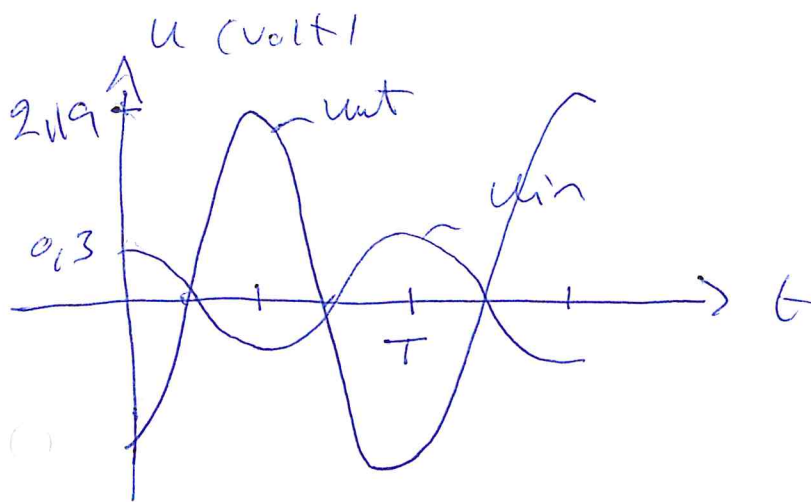
$$0,3 \cdot \cos(2\pi \cdot 12 \cdot 10^3 t)$$




$$T = \frac{1}{12 \cdot 10^3} \approx 83 \mu\text{s}$$

f) Om R_L ansluts $\Rightarrow U_{ut} = (R_L // R_D) \cdot g_m \cdot U_{gs}$

$$\Rightarrow A_u = -\frac{g_m \cdot (R_L // R_D)}{1 + g_m R_S} \Rightarrow |A_u| \text{ minimer ty}$$

$$R_L // R_D < R_D$$

$\therefore \hat{U}_{ut}$ minimer.

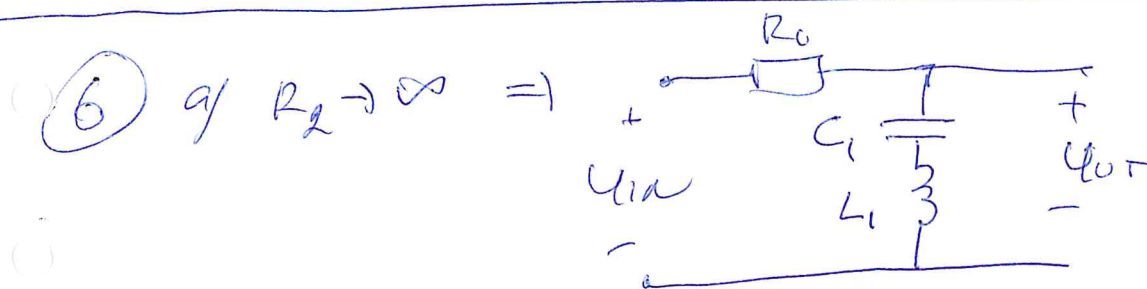

$$\omega_r = \frac{1}{\sqrt{L C_1}} \Rightarrow f_r = \frac{\omega_r}{2\pi} \approx 19,3 \text{ kHz}$$

$$I_{\text{max}} \text{ d\u00e4 } \omega = \omega_r \quad (Z_{\text{tot}} = R_0 \text{ d\u00e4}) \Rightarrow I_{\text{max}} = \frac{U_{in}}{R_0} = \underline{\underline{0,02 \text{ A}}}$$

Bandspassfilter: $U_{ut} \approx 0$ d\u00e4 $\omega = \omega_r$

$U_{ut} \approx U_{in}$ d\u00e4 $\omega \ll \omega_r$ & $\omega \gg \omega_r$

\uparrow kond. 'b\u00f6tt'
 \uparrow indukt. 'b\u00f6tt'

b/ Resonans inträffar ej om ω_r imaginär.

$$Z_{tot} = R_0 + j\omega L_1 + \frac{R_2 \frac{1}{j\omega C_1}}{R_2 + \frac{1}{j\omega C_1}} = \dots =$$

$$= R_0 + j\omega L_1 + \frac{R_2}{1 + (\omega R_2 C_1)^2} - \frac{j\omega R_2 C_1}{1 + (\omega R_2 C_1)^2}$$

$$\text{Im } Z_{tot} = 0 \Rightarrow \omega = \frac{1}{C_1 R_2} \sqrt{\frac{C_1}{L_1} R_2^2 - 1}$$

$$\Rightarrow \omega \text{ imaginär om } R_2 < \sqrt{\frac{L_1}{C_1}} \approx 82,5 \Omega$$

\therefore Resonans saknas om $R_2 < \underline{\underline{82 \Omega}}$

Högpåss filter \circ ($|U_{ut}| \approx |U_{in}|$ höga ω (induktans "avbrott")

$$|U_{ut}| \approx \frac{R_2}{R_1 + R_2} |U_{in}| \text{ låga } \omega$$

(kond "avbrott",
ström genom R_2 ,
ind. "kontakter")